

# Computer Architecture

## Week 2: Logic Gates and Arithmetic



Fenerbahçe University

# Professor & TAs

Prof: Dr. Vecdi Emre Levent

Office: 311

Email: [emre.levent@fbu.edu.tr](mailto:emre.levent@fbu.edu.tr)

TA: Arş. Gör. Uğur Özbalkan

Office: 311


Email: [ugur.ozbalkan@fbu.edu.tr](mailto:ugur.ozbalkan@fbu.edu.tr)

# Course Plan


- Logic Gates and Arithmetic

# Switch

## Conductor and insulator

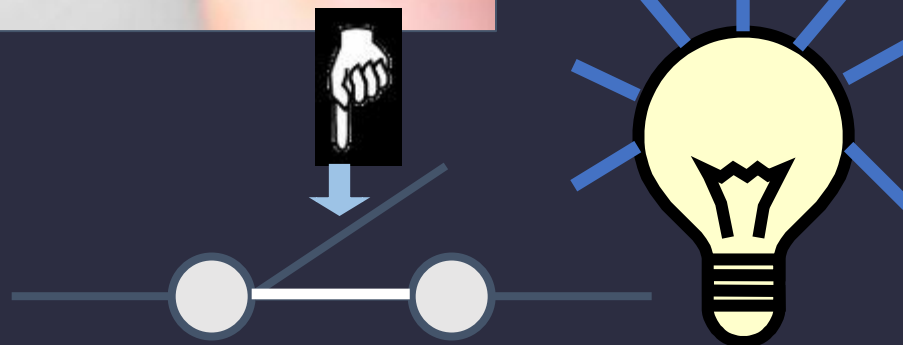


# Switches to Gates

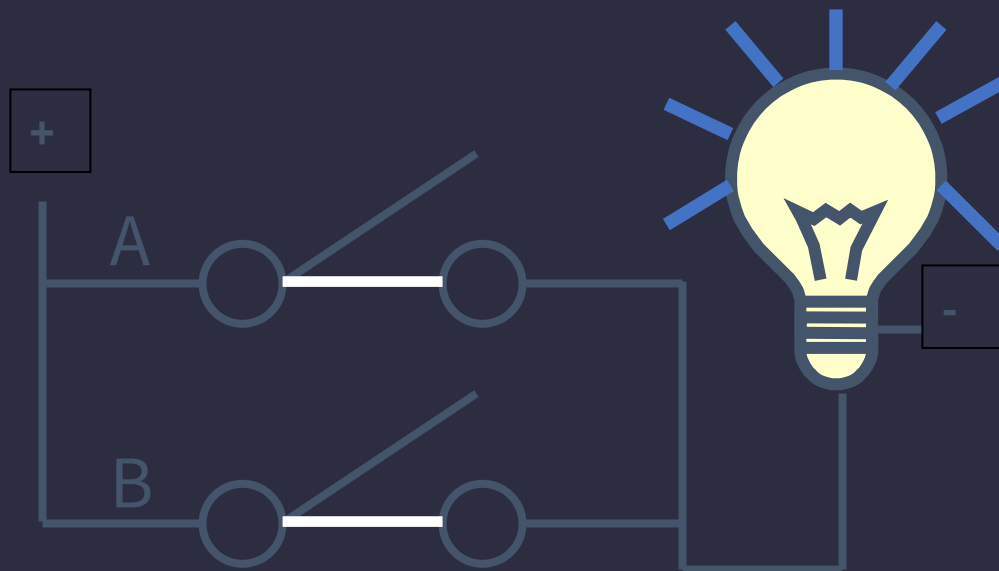

Truth Table


A	B	Light
OFF	OFF	OFF
OFF	ON	ON
ON	OFF	ON
ON	ON	ON

# Switches to Gates

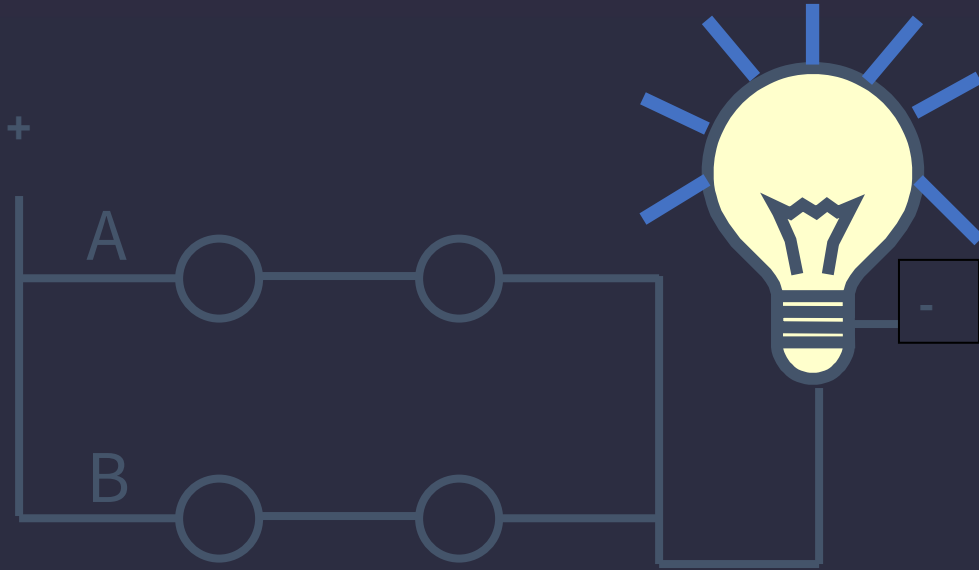

Truth Table


A	B	Light
OFF	OFF	OFF
OFF	ON	ON
ON	OFF	ON
ON	ON	ON

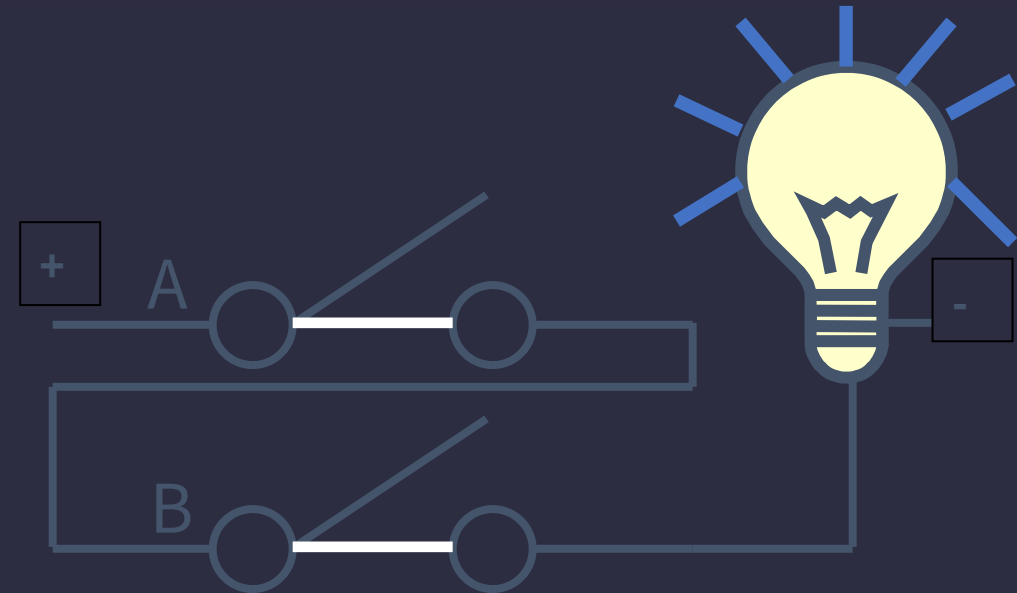

Truth Table

A	B	Light
OFF	OFF	OFF
OFF	ON	OFF
ON	OFF	OFF
ON	ON	ON


# Switches to Gates

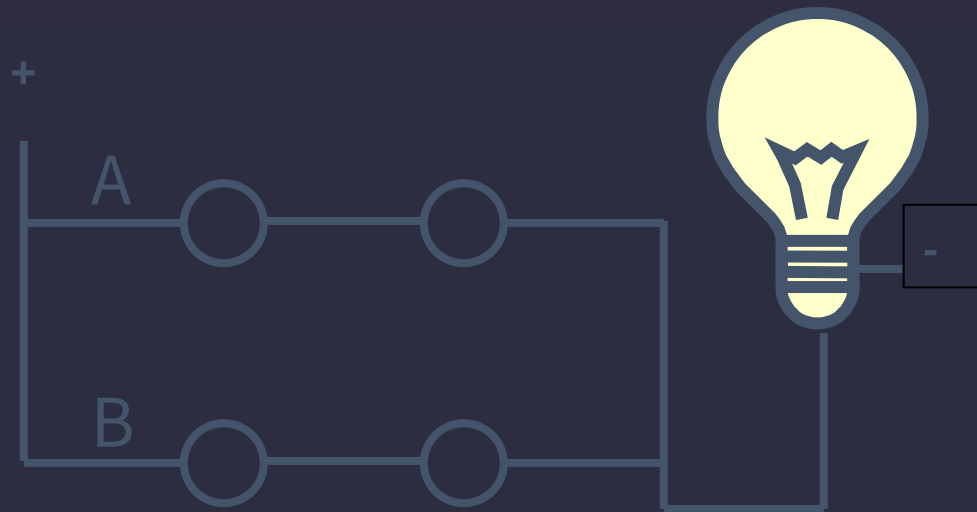

## • OR

Truth Table


A	B	Light
OFF	OFF	OFF
OFF	ON	ON
ON	OFF	ON
ON	ON	ON

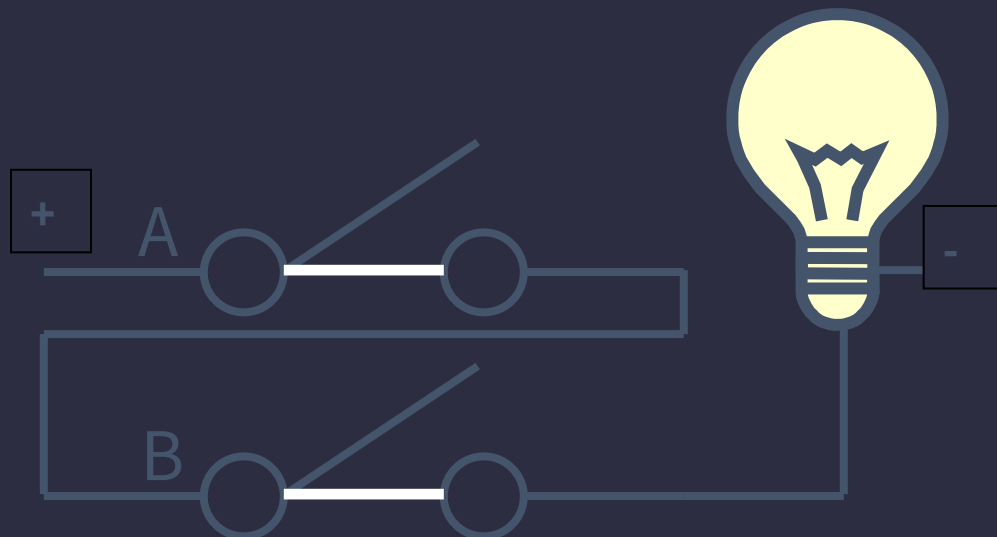

## • AND

A	B	Light
OFF	OFF	OFF
OFF	ON	OFF
ON	OFF	OFF
ON	ON	ON

# Switches to Gates

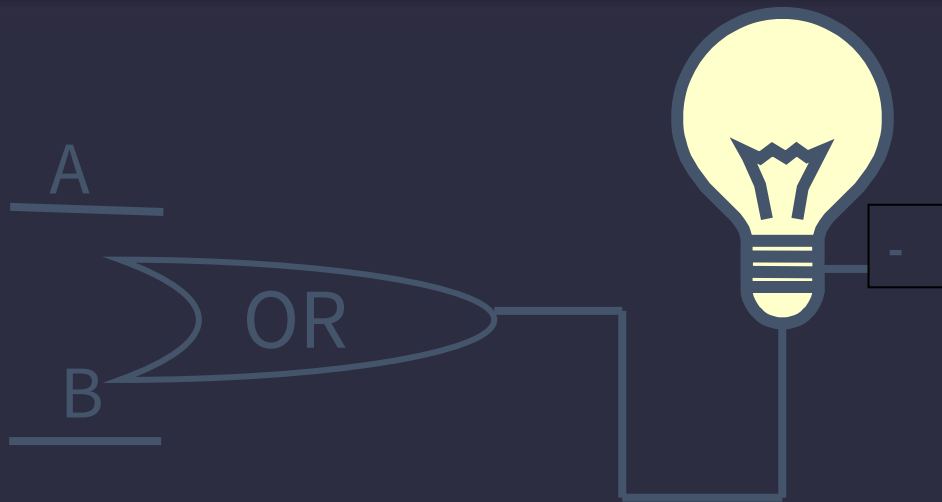

- OR

Truth Table

A	B	Light
OFF	OFF	OFF
OFF	ON	ON
ON	OFF	ON
ON	ON	ON



- AND

A	B	Light
OFF	OFF	OFF
OFF	ON	OFF
ON	OFF	OFF
ON	ON	ON

# Switches to Gates

- Binary
  - There are two symbols: true and false
  - Fundamental for logic design

# Logic Gates

- NOT:



A	Out
0	1
1	0

- AND:



A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

- OR:



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1


## Logic Gates

They are using for building logic functions

Commonly using gates:  
AND, OR, NOT

# Logic Gates

NOT:

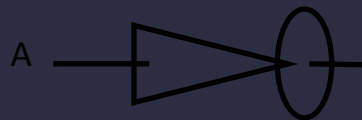

A	Out
0	1
1	0

AND:



A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

OR:



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1


XOR:



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

# Logic Gates

NOT:

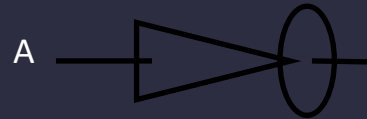

A	Out
0	1
1	0

AND:



A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

OR:



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

XOR:



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

NAND:



A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

NOR:



A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

XNOR:



A	B	Out
0	0	1
0	1	0
1	0	0
1	1	1

# Logic Gates

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

## Truth Table to Function

a	b	c	out	minterm
0	0	0	0	$\bar{a} \bar{b} \bar{c}$
0	0	1	1	$\bar{a} \bar{b} c$
0	1	0	0	$\bar{a} b \bar{c}$
0	1	1	1	$\bar{a} b c$
1	0	0	0	$a \bar{b} \bar{c}$
1	0	1	1	$a \bar{b} c$
1	1	0	0	$a b \bar{c}$
1	1	1	0	$a b c$

1. Write minterms
2. Write sum of products of elements which minterm column is 1

# Truth Table to Function

a	b	c	out	minterm
0	0	0	0	$\bar{a} \bar{b} \bar{c}$
0	0	1	1	$\bar{a} \bar{b} c$
0	1	0	0	$\bar{a} b \bar{c}$
0	1	1	1	$\bar{a} b c$
1	0	0	0	$a \bar{b} \bar{c}$
1	0	1	1	$a \bar{b} c$
1	1	0	0	$ab \bar{c}$
1	1	1	0	$abc$

1. Write minterms
2. Write sum of products of elements which minterm column is 1
  - So,  $out = \bar{a}\bar{b}c + \bar{a}bc + a\bar{b}c$

# Logical Expressions

- NOT:

- $\text{out} = \bar{a} = !a = \neg a$

- AND:

- $\text{out} = a \cdot b = a \& b = a \wedge b$

- OR:

- $\text{out} = a + b = a | b = a \vee b$

- XOR:

- $\text{out} = a \oplus b = a\bar{b} + \bar{a}b$

## NAND:

- $\text{out} = \overline{a \cdot b} = !(a \& b) = \neg (a \wedge b)$

## NOR:

- $\text{out} = \overline{a + b} = !(a | b) = \neg (a \vee b)$

## XNOR:

- $\text{out} = \overline{a \oplus b} = ab + \bar{a}\bar{b}$

# Logical Expressions

$$a + 0 = a$$

$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a \cdot 0 = 0$$

$$a \cdot 1 = a$$


$$a \cdot \bar{a} = 0$$
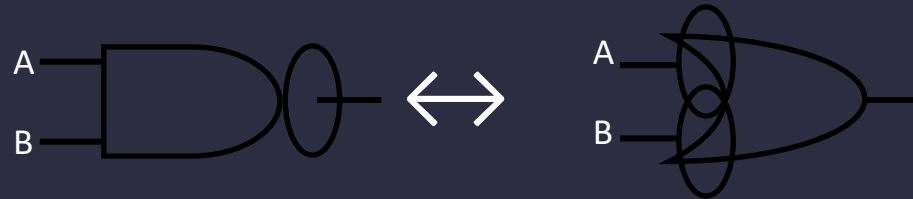
# Logical Expressions

$$\overline{(a + b)} = \bar{a} \cdot \bar{b}$$



$$\overline{(a \cdot b)} = \bar{a} + \bar{b}$$



$$a + a \cdot b = a$$

$$a(b+c) = ab + ac$$

$$\overline{a(b + c)} = \bar{a} + \bar{b} \cdot \bar{c}$$

# Minimization Example

$$a + 0 = a$$

$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a \cdot 0 = 0$$

$$a \cdot 1 = a$$

$$a \cdot \bar{a} = 0$$

$$a + a b = a$$

$$a(b+c) = ab + ac$$

$$\overline{(a + b)} = \bar{a} \bullet \bar{b}$$

$$\overline{(ab)} = \bar{a} + \bar{b}$$

$$a(b + c) = \bar{a} + \bar{b} \bullet \bar{c}$$

Minimize the function below

$$\begin{aligned}(a+b)(a+c) &= (a+b)a + (a+b)c \\ &= aa + ba + ac + bc \\ &= a + a(b+c) + bc \\ &= a + bc\end{aligned}$$

# Minimization Example

$$a + 0 = a$$

$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a \cdot 0 = 0$$

$$a \cdot 1 = a$$

$$a \cdot \bar{a} = 0$$

$$a + a \cdot b = a$$

$$a(b+c) = ab + ac$$

$$\overline{(a + b)} = \bar{a} \cdot \bar{b}$$

$$\overline{(ab)} = \bar{a} + \bar{b}$$

$$a(b + c) = \bar{a} + \bar{b} \cdot \bar{c}$$

Minimize the function below

$$\begin{aligned}(a+b)(a+c) &= (a+b)a + (a+b)c \\ &= aa + ba + ac + bc \\ &= a + a(b+c) + bc \\ &= a + bc\end{aligned}$$

Required logic gates

Before	After
2 OR, 1 AND	1 OR, 1 AND

# Equality Check with Truth tables

Example:  $(a+b)(a+c) = a + bc$

<b>a</b>	<b>b</b>	<b>c</b>					
<b>0</b>	<b>0</b>	<b>0</b>					
<b>0</b>	<b>0</b>	<b>1</b>					
<b>0</b>	<b>1</b>	<b>0</b>					
<b>0</b>	<b>1</b>	<b>1</b>					
<b>1</b>	<b>0</b>	<b>0</b>					
<b>1</b>	<b>0</b>	<b>1</b>					
<b>1</b>	<b>1</b>	<b>0</b>					
<b>1</b>	<b>1</b>	<b>1</b>					

## Equality Check with Truth tables

Example:  $(a+b)(a+c) = a + bc$

a	b	c	a+b	a+c	Sol	bc	Sağ
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

# Karnaugh Maps

How to reach most optimum circuit?

- Algebraic minimizations
- Karnaugh Map
- Computer aided minimization softwares (Totally that way in 2021)

# Karnaugh Maps

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

## ◆ Sum of Minterms

■  $out = \overline{a}bc + \overline{a}bc + a\overline{b}c + a\overline{b}c$

# Karnaugh Maps

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

		ab			
		00	01	11	10
c	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

## ◆ Sum of Minterms

- $out = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + a\bar{b}c$

## ◆ Kmaps are usefull for detecting which inputs are relevant for output

## ◆ When creating Kmap table, only 1 bit can change on row and columns

# Karnaugh Maps

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

		ab			
		00	01	11	10
c	0	0	0	0	1
	1	1	1	0	1

## Sum of Minterms

- $out = \bar{a}\bar{b}c + \bar{a}bc + a\bar{b}c + a\bar{b}c$

## Kmap minimization

- Group ones with twos power group
- Eliminate unnecessary inputs
- ◆  $out = a\bar{b} + \bar{a}c$

# Karnaugh Maps

	ab			
c	00	01	11	10
0	0	1	1	1
1	0	0	1	0

	ab			
c	00	01	11	10
0	1	1	1	1
1	0	0	1	0

◆ Minterms can be used different groups

- $out = b\bar{c} + a\bar{c} + ab$

◆ Minterms can be grouped by two's power

- $out = \bar{c} + ab$

# Karnaugh Maps

	ab			
cd	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	1	0	0	1
10	0	0	0	0

- $out = \bar{b}d$

	ab			
cd	00	01	11	10
00	1	0	0	1
01	0	0	0	0
11	0	0	0	0
10	1	0	0	1

- $out = \bar{b} \bar{d}$

# Karnaugh Maps

		ab			
		00	01	11	10
cd	00	0	0	0	0
	01	1	x	x	x
	11	1	x	x	1
	10	0	0	0	0

- X (“Don’t care”) can be evaluated zero or one.
  - If all X’s are 1,
  - $out = d$

		ab			
		00	01	11	10
cd	00	1	0	0	x
	01	0	x	x	0
	11	0	x	x	0
	10	1	0	0	1


- If all X’s are 0,
- And only right top X is 1, then
- $out = \bar{b} \bar{d}$

# Karnaugh Maps

		ab			
c		00	01	11	10
	0	0	0	0	1
	1	1	1	0	1

$$= a\bar{b} + \bar{a}c$$


# Multiplexer

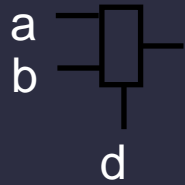

- Multiplexer kendisine verilen girişleri seçerek dışarı çıkarır
  - Eğer  $d=0$ ,  $out = a$
  - Eğer  $d=1$ ,  $out = b$

a	b	d	out
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


# Multiplexer

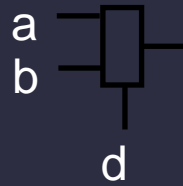

- Doğruluk tablosu oluşturun  
$$\text{out} = \bar{a}bd + a\bar{b}\bar{d} + ab\bar{d} + abd$$

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

# Multiplexer

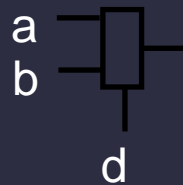


- KMap

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

	ab			
d	00	01	11	10
0				
1				

# Multiplexer

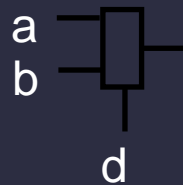


- KMap

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

	ab	00	01	11	10
d	0	0	0	1	1
	1	0	1	1	0

# Multiplexer

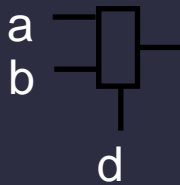


a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


- Minimized Equation

	ab	00	01	11	10
d	0	0	0	1	1
1	0	0	1	1	0

- $out = a\bar{d} + bd$

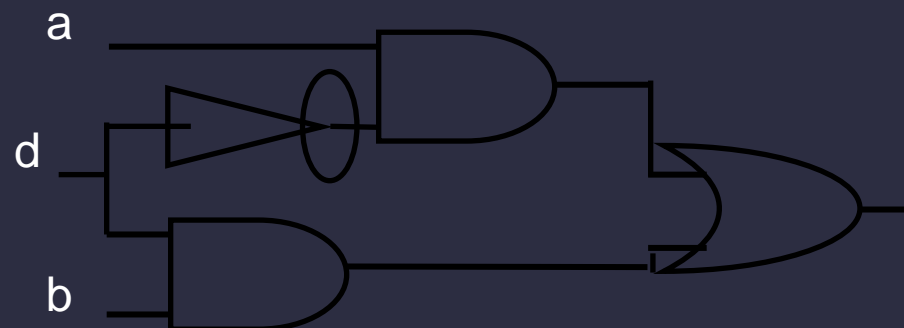


# Transistors

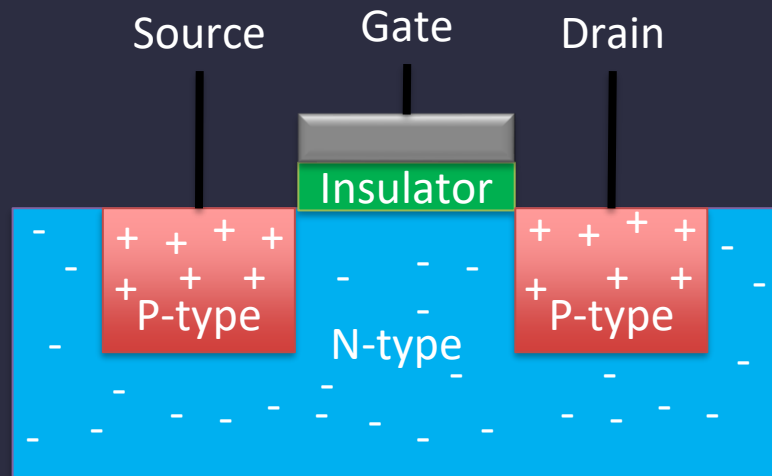

P-Transistor

Closed

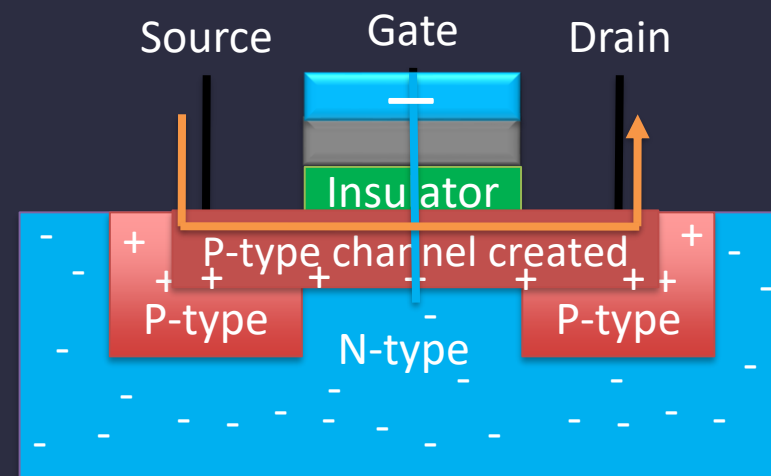


P-Transistor


Open

# CMOS Notation

N-Type

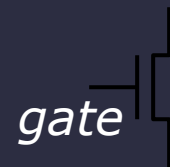

*Closed*

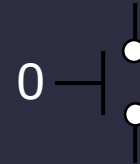


*Open*



P-Type



*Closed*

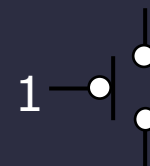


*Open*



Electric flow controls with gate input.

# NOT Gate


NOT

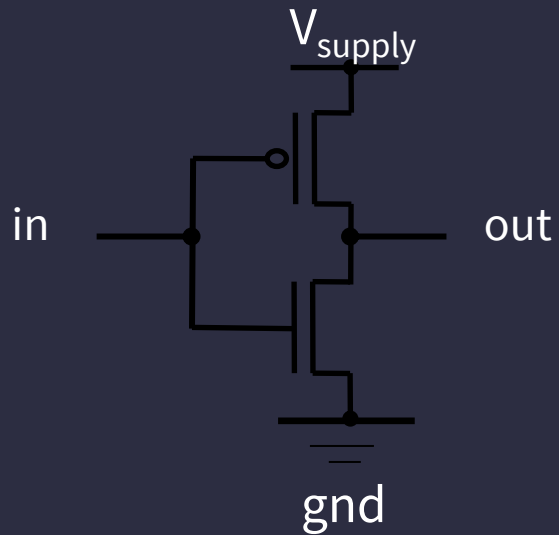

Truth Table

In	Out
0	1
1	0

# NOR Gate

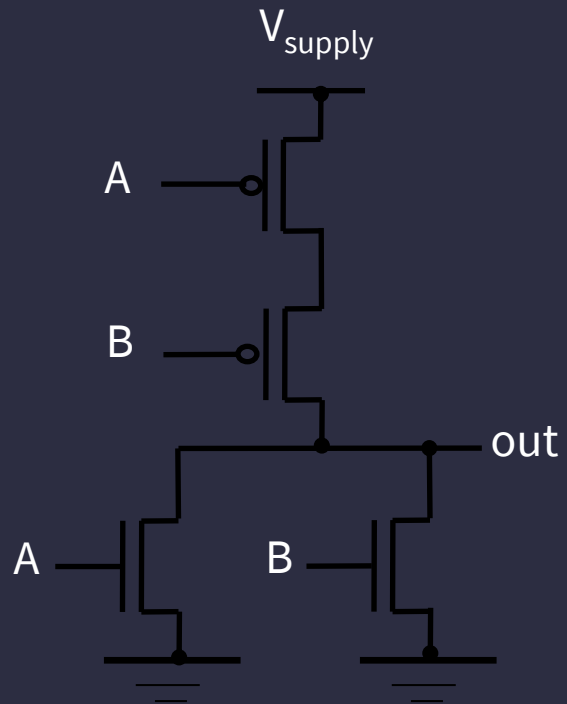

NOR



Truth Table

A	B	out
0	0	1
0	1	0
1	0	0
1	1	0

# Logic Gates


- NOT:



- AND:



- OR:

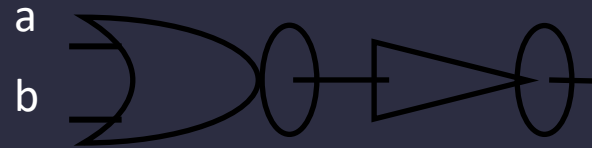

- Generally ASIC designs builds combinations of NAND gates

# Number Representations

## Binary

- There are two symbols: **true** and **false**; **1** and **0**
- It is fundamental of digital systems

# Number Representations

## Binary

- There are two symbols: **true** and **false**; **1** and **0**
- It is fundamental of digital systems

## Base 10 Representation

- Example. 6 3 7       $6 \cdot 10^2 + 3 \cdot 10^1 + 7 \cdot 10^0 = \mathbf{637}$

- Other Bases

- Base 2 — Binary
- Base 8 — Octal
- Base 16 — Hexadecimal

$$1 \cdot 2^9 + 1 \cdot 2^6 + 1 \cdot 2^5 + 1 \cdot 2^4 + 1 \cdot 2^3 + 1 \cdot 2^2 + 1 \cdot 2^0 = \mathbf{637}$$

$$1 \cdot 8^3 + 1 \cdot 8^2 + 7 \cdot 8^1 + 5 \cdot 8^0 = \mathbf{637}$$

$$2 \cdot 16^2 + 7 \cdot 16^1 + \mathbf{d} \cdot 16^0 = \mathbf{637}$$

$$2 \cdot 16^2 + 7 \cdot 16^1 + \mathbf{13} \cdot 16^0 = \mathbf{637}$$


# Number Representations

## Conversion between bases
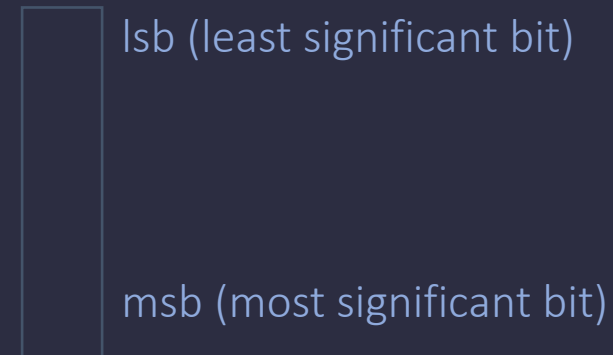
### Base conversion via repetitive division

- Divide by base, write remainder, move left with quotient
- Example: Base 10 to 8 (octal)

- $637 \div 8 = 79$  remainder 5 lsb
- $79 \div 8 = 9$  remainder 7
- $9 \div 8 = 1$  remainder 1
- $1 \div 8 = 0$  remainder 1 msb



- $637 = 0o\ 1175$

# Number Representations

Convert a base 10 number to a base 2 number

Base conversion via repetitive division

- Divide by base, write remainder, move left with quotient
- $637 \div 2 = 318$  remainder 1
- $318 \div 2 = 159$  remainder 0
- $159 \div 2 = 79$  remainder 1
- $79 \div 2 = 39$  remainder 1
- $39 \div 2 = 19$  remainder 1
- $19 \div 2 = 9$  remainder 1
- $9 \div 2 = 4$  remainder 1
- $4 \div 2 = 2$  remainder 0
- $2 \div 2 = 1$  remainder 0
- $1 \div 2 = 0$  remainder 1

637 = 10 0111 1101 (can also be written as 0b10 0111 1101)

msb

lsb

# Number Representations

Convert a base 10 number to a base 16 number

Base conversion via repetitive division

- Divide by base, write remainder, move left with quotient
- $657 \div 16 = 41$  remainder 1
- $41 \div 16 = 2$  remainder 9
- $2 \div 16 = 0$  remainder 2



Thus,  $657 = 0x291$

# Number Representations

Convert a base 10 number to a base 16 number

Base conversion via repetitive division

- Divide by base, write remainder, move left with quotient
- $637 \div 16 = 39$  remainder 13
- $39 \div 16 = 2$  remainder 7
- $2 \div 16 = 0$  remainder 2

	lsb	<u>dec</u> = <u>hex</u>	= <u>bin</u>
		10 = 0xa	= 1010
		11 = 0xb	= 1011
		12 = 0xc	= 1100
		13 = 0xd	= 1101
		14 = 0xe	= 1110
		15 = 0xf	= 1111
	msb		

$637 = 0x\ 2\ 7\ 13 = ?$

Thus,  $637 = 0x27d$



# Number Representations Summary

- Base 10 – Decimal

$$\begin{array}{ccc} \underline{6} & \underline{3} & \underline{7} \\ 10^2 & 10^1 & 10^0 \end{array}$$

$$6 \cdot 10^2 + 3 \cdot 10^1 + 7 \cdot 10^0 = 637$$

- Base 2 — Binary

$$\begin{array}{cccccccccccc} \underline{1} & \underline{0} & \underline{0} & \underline{1} & \underline{1} & \underline{1} & \underline{1} & \underline{1} & \underline{0} & \underline{1} \\ 2^9 & 2^8 & 2^7 & 2^6 & 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0 \end{array}$$

$$1 \cdot 2^9 + 1 \cdot 2^6 + 1 \cdot 2^5 + 1 \cdot 2^4 + 1 \cdot 2^3 + 1 \cdot 2^2 + 1 \cdot 2^0 = 637$$

- Base 8 — Octal

$$\text{0o } \begin{array}{ccc} \underline{1} & \underline{1} & \underline{7} & \underline{5} \\ 8^3 & 8^2 & 8^1 & 8^0 \end{array}$$

$$1 \cdot 8^3 + 1 \cdot 8^2 + 7 \cdot 8^1 + 5 \cdot 8^0 = 637$$

- Base 16 — Hexadecimal

$$\text{0x } \begin{array}{ccc} \underline{2} & \underline{7} & \underline{d} \\ 16^2 & 16^1 & 16^0 \end{array}$$

$$2 \cdot 16^2 + 7 \cdot 16^1 + d \cdot 16^0 = 637$$

$$2 \cdot 16^2 + 7 \cdot 16^1 + 13 \cdot 16^0 = 637$$

# Binary Addition

- Addition works the same way regardless of base
  - Add the digits in each position
  - Propagate the carry

Unsigned binary addition is pretty easy

- Combine two bits at a time
- Along with a carry

How do we do arithmetic in binary?

$$\begin{array}{r} 1 \\ 183 \\ + 254 \\ \hline 437 \end{array}$$


Carry-in      Carry-out

$$\begin{array}{r} 111 \\ 001110 \\ + 011100 \\ \hline 101010 \end{array}$$


# Binary Addition

- Binary addition requires
  - Add of *two bits* PLUS *carry-in*
  - Also, *carry-out* if necessary

# 1-bit Adder

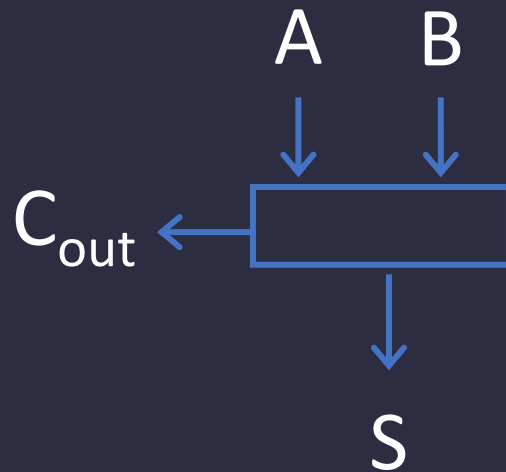

A	B	C <sub>out</sub>	S
0	0		
0	1		
1	0		
1	1		

## Half Adder

- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry
- No carry-in

What is the equation for  $C_{out}$ ?

a)  $A + B$


b)  $AB$

c)  $A \oplus B$

d)  $A + !B$

e)  $!A!B$

# 1-bit Adder

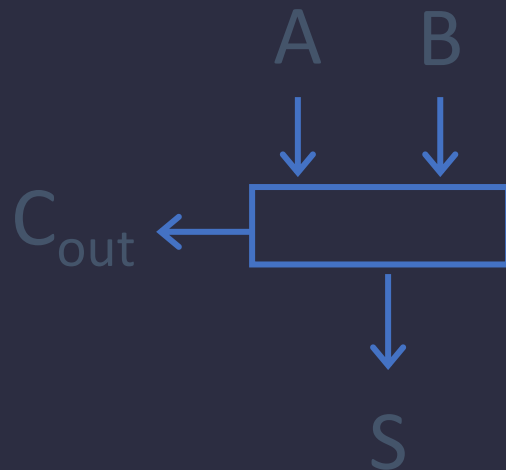


A	B	C <sub>out</sub>	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

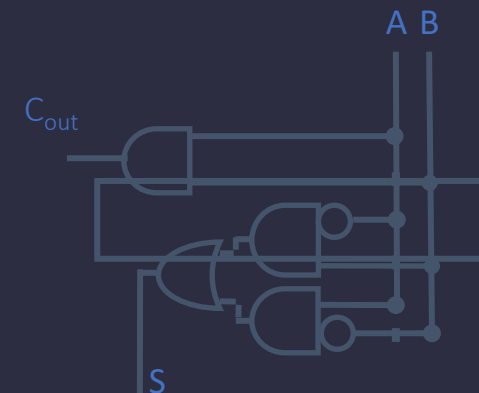
## Half Adder

- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry
- No carry-in

- $S = \bar{A}B + A\bar{B}$
- $C_{out} = AB$



# 1-bit Adder

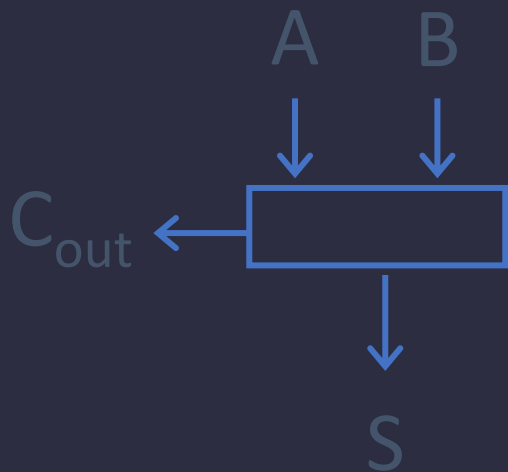


A	B	C <sub>out</sub>	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

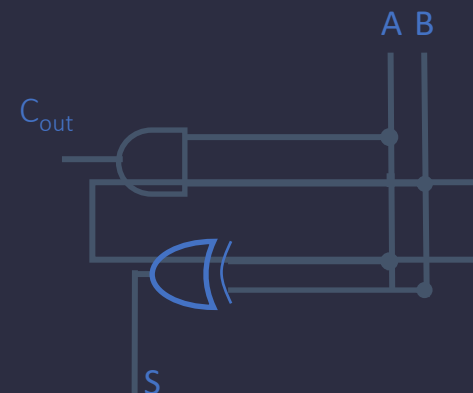
## Half Adder

- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry
- No carry-in

- $S = \bar{A}B + A\bar{B} = A \oplus B$
- $C_{out} = AB$



# 1-bit Adder with Carry

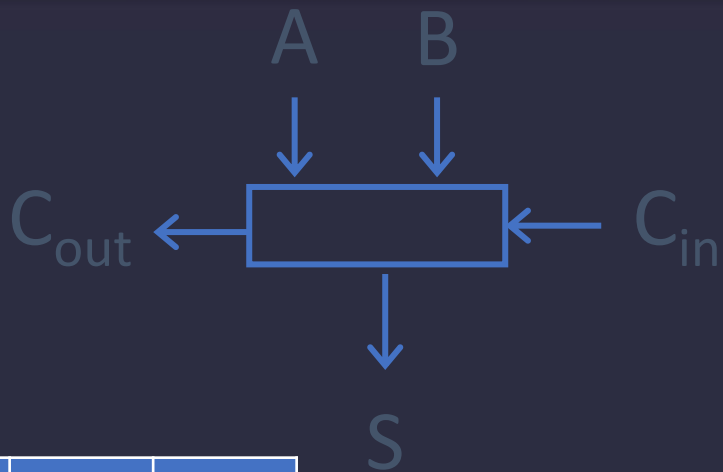


A	B	C <sub>in</sub>	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

## Full Adder


- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded

$$S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$
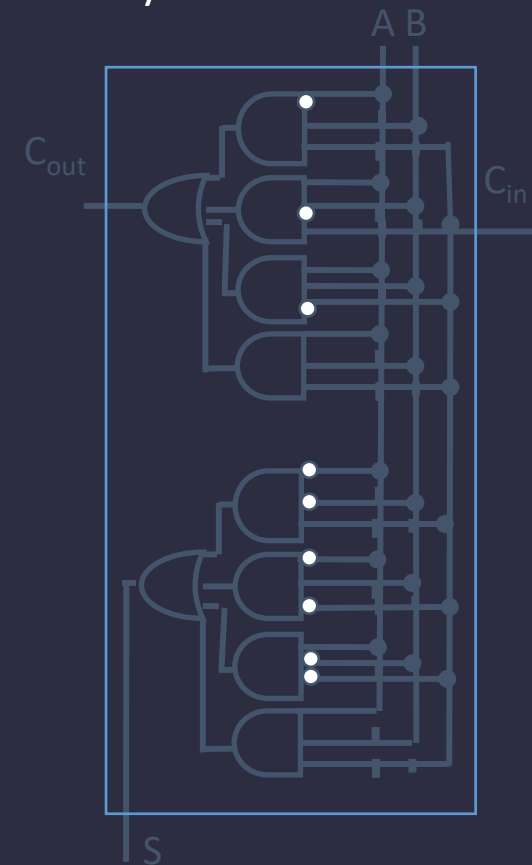
$$C_{out} = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$



# 1-bit Adder with Carry

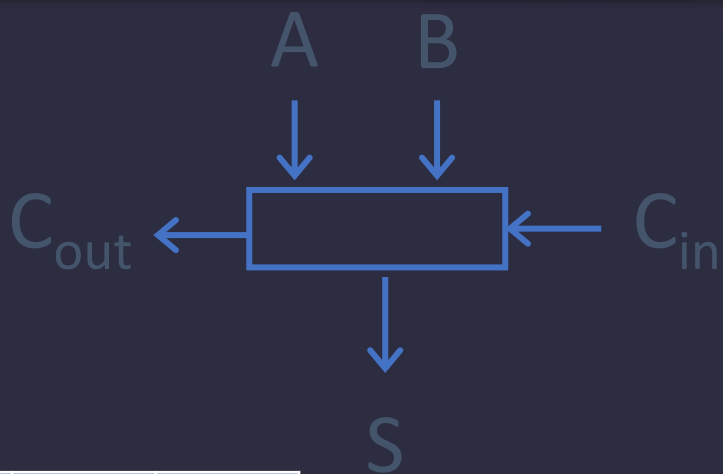

A	B	C <sub>in</sub>	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


## Full Adder

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded

$$S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$


$$C_{out} = \overline{A}BC + \overline{A}\overline{B}C + A\overline{B}\overline{C} + ABC$$

$$C_{out} = AB + AC + BC$$

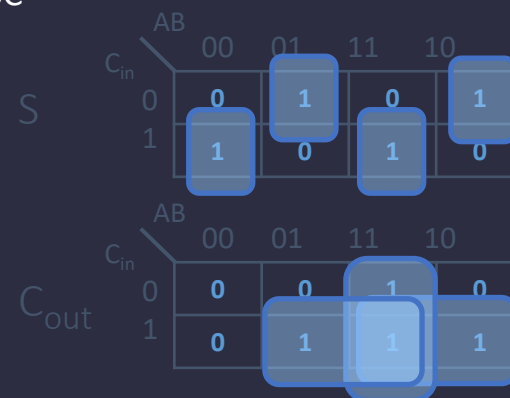

AB \ C <sub>in</sub>	00	01	11	10
0	0	1	0	1
1	1	0	1	0


AB \ C <sub>in</sub>	00	01	11	10
0	0	0	1	0
1	0	1	1	1

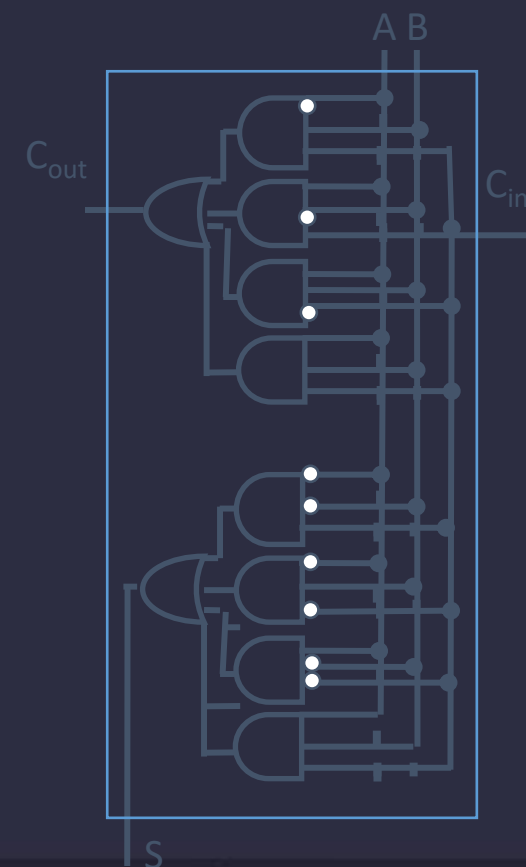


## 4-bit Adder
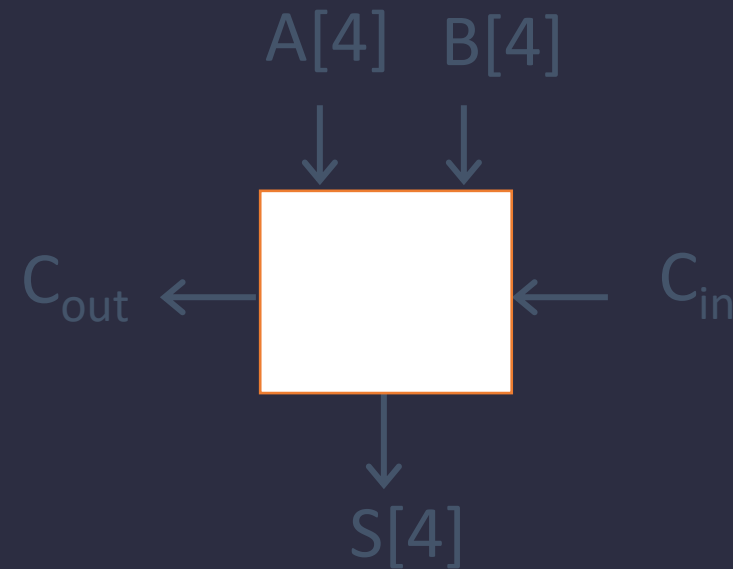
### 4-Bit Full Adder

- Adds two 4-bit numbers and carry in
- Computes 4-bit result and carry out
- Can be cascaded




## 4-bit Adder

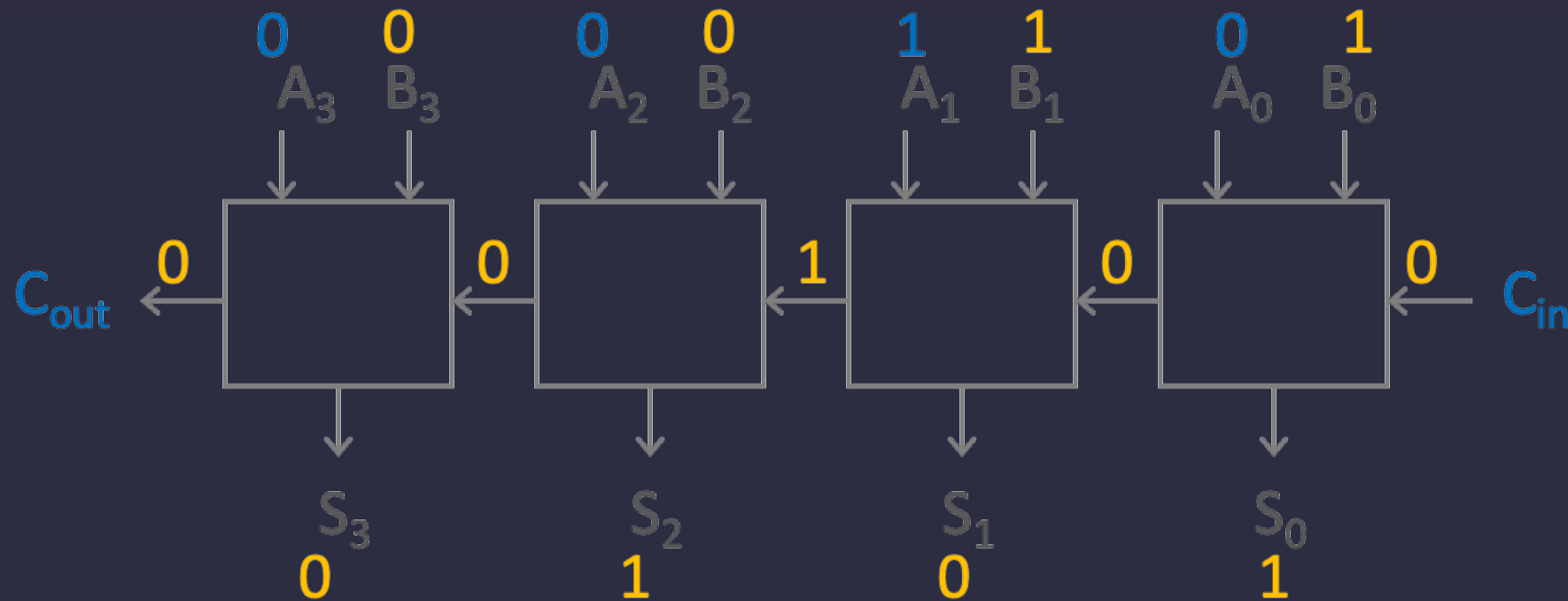

- Adds two 4-bit numbers, along with carry-in
- Computes 4-bit result and carry out
- Carry-out = overflow indicates result does not fit in 4 bits

## 4-bit Adder

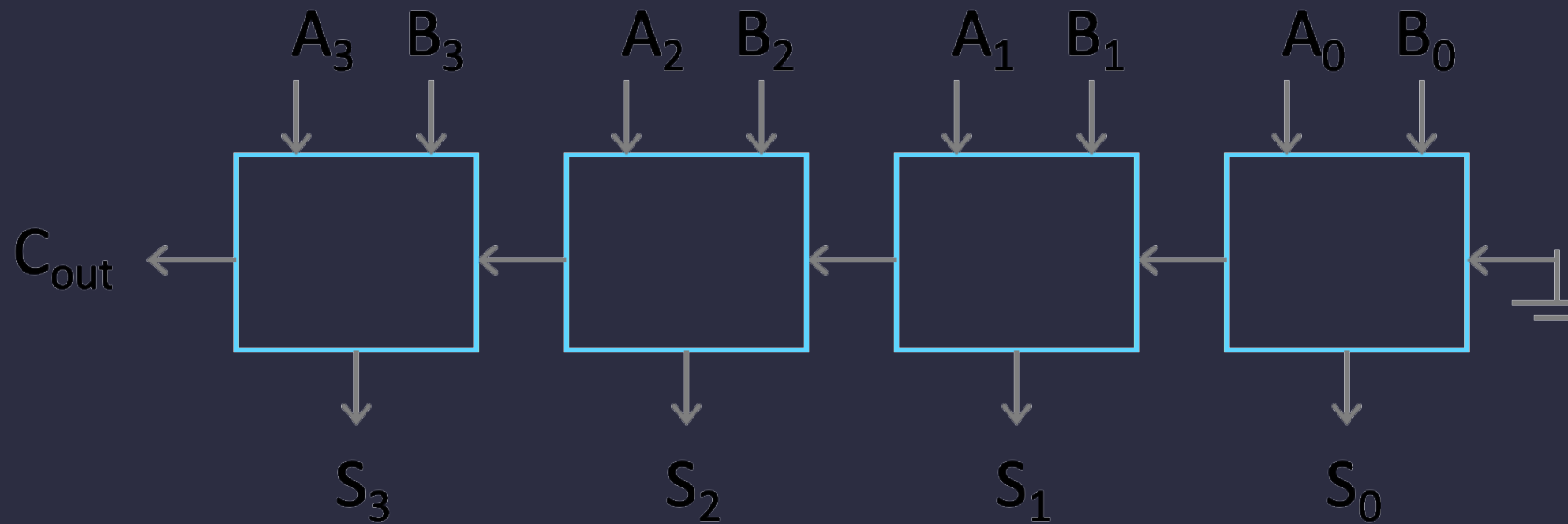

- Adds two 4-bit numbers, along with carry-in
- Computes 4-bit result and carry out
- Carry-out = overflow indicates result does not fit in 4 bits

# 1<sup>st</sup> Attempt: Sign/Magnitude Representation

- First Attempt: Sign/Magnitude Representation

- 1 bit for sign (0=positive, 1=negative)       $\underline{0}111 = 7$
- N-1 bits for magnitude       $\underline{1}111 = -7$

## Problem?

- Two zero's: +0 different than -0       $\underline{0}000 = +0$
- Complicated circuits       $\underline{1}000 = -0$
- $-2 + 1 = ???$

## Second Attempt: One's complement

- Second Attempt: One's complement

- Leading 0's for positive and 1's for negative
- Negative numbers: complement the positive number

$$\underline{0}111 = 7$$

$$\underline{1}000 = -7$$

- Problem?

- Two zero's still: +0 different than -0
- -1 if offset from two's complement
- Complicated circuits
  - Carry is difficult

$$\underline{0}000 = +0$$

$$\underline{1}111 = -0$$

# Two's Complement Representation

What is used: Two's Complement Representation

Nonnegative numbers are represented as usual

- $0 = 0000$ ,  $1 = 0001$ ,  $3 = 0011$ ,  $7 = 0111$

Leading 1's for negative numbers

To negate any number:

- complement *all* the bits (i.e. flip all the bits)
- then add 1
- $-1: 1 \Rightarrow 0001 \Rightarrow 1110 \Rightarrow 1111$
- $-3: 3 \Rightarrow 0011 \Rightarrow 1100 \Rightarrow 1101$
- $-7: 7 \Rightarrow 0111 \Rightarrow 1000 \Rightarrow 1001$
- $-8: 8 \Rightarrow 1000 \Rightarrow 0111 \Rightarrow 1000$
- $-0: 0 \Rightarrow 0000 \Rightarrow 1111 \Rightarrow 0000$  (this is good,  $-0 = +0$ )

# Two's Complement

Non-negatives  
(as usual):

+0 = 0000  
+1 = 0001  
+2 = 0010  
+3 = 0011  
+4 = 0100  
+5 = 0101  
+6 = 0110  
+7 = 0111  
+8 = 1000

Negatives (two's complement)

flip

then add 1

$\bar{0} = 1111$	-0 = 0000
$\bar{1} = 1110$	-1 = 1111
$\bar{2} = 1101$	-2 = 1110
$\bar{3} = 1100$	-3 = 1101
$\bar{4} = 1011$	-4 = 1100
$\bar{5} = 1010$	-5 = 1011
$\bar{6} = 1001$	-6 = 1010
$\bar{7} = 1000$	-7 = 1001
$\bar{8} = 0111$	-8 = 1000

# Two's Complement vs. Unsigned

$$-1 = 1111 = 15$$

$$-2 = 1110 = 14$$

$$-3 = 1101 = 13$$

$$-4 = 1100 = 12$$

$$-5 = 1011 = 11$$

$$-6 = 1010 = 10$$

$$-7 = 1001 = 9$$

$$-8 = 1000 = 8$$

$$+7 = 0111 = 7$$

$$+6 = 0110 = 6$$

$$+5 = 0101 = 5$$

$$+4 = 0100 = 4$$

$$+3 = 0011 = 3$$

$$+2 = 0010 = 2$$

$$+1 = 0001 = 1$$

$$0 = 0000 = 0$$

4 bit  
Two's  
Complement  
-8 ... 7

4 bit  
Unsigned  
Binary  
0 ... 15

## 2s Complement

Calculate the following twos complement number value in decimal base

11010

11010

00101 (flip)

+1

---

-6 = 00110

# Two's Complement Facts

## Signed two's complement

Negative numbers have leading 1's

zero is unique:  $+0 = -0$

wraps from largest positive to largest negative

## N bits can be used to represent

unsigned: range  $0 \dots 2^N - 1$

eg: 8 bits  $\Rightarrow 0 \dots 255$

signed (two's complement):  $-(2^{N-1}) \dots (2^{N-1} - 1)$

E.g.: 8 bits  $\Rightarrow (1000\ 000) \dots (0111\ 1111)$

$-128 \dots 127$

# Sign Extension & Truncation

## Extending to larger size

- $1111 = -1$
- $1111\ 1111 = -1$
- $0111 = 7$
- $0000\ 0111 = 7$

## Truncate to smaller size

- $0000\ 1111 = 15$
- BUT,  $0000\ 1111 = 1111 = -1$

# Two's Complement Addition

- Addition with two's complement signed numbers
- Addition as usual. Ignore the sign. It just works!
- Examples
  - $1 + -1 = 0001 + 1111 = 0000$  (0)
  - $-3 + -1 = 1101 + 1111 = 1100$  (-4)
  - $-7 + 3 = 1001 + 0011 = 1100$  (-4)
  - $7 + (-3) = 0111 + 1101 = 0100$  (4)

## Clicker Question

Which of the following has problems?

- a)  $7 + 1 = 1000$  overflow
- b)  $-7 + -3 = 1\ 0110$  overflow
- c)  $-7 + -1 = 1000$  fine
- d) Only (a) and (b) have problems
- e) They all have problems

-1 =	1111	= 15
-2 =	1110	= 14
-3 =	1101	= 13
-4 =	1100	= 12
-5 =	1011	= 11
-6 =	1010	= 10
-7 =	1001	= 9
-8 =	1000	= 8
+7 =	0111	= 7
+6 =	0110	= 6
+5 =	0101	= 5
+4 =	0100	= 4
+3 =	0011	= 3
+2 =	0010	= 2
+1 =	0001	= 1
0 =	0000	= 0

# Overflow

## When can **overflow** occur?

- adding a negative and a positive?
  - Overflow *cannot occur* (Why?)
  - Always subtract larger magnitude from smaller
- adding two positives?
  - Overflow *can occur* (Why?)
  - Precision: Add two positives, and get a negative number!
- adding two negatives?
  - Overflow *can occur* (Why?)
  - Precision: add two negatives, get a positive number!

## Rule of thumb:

- Overflow happens iff  
carry into msb  $\neq$  carry out of msb

# Overflow

## When can **overflow** occur?

- adding a negative and a positive?
  - Overflow *cannot occur* (Why?)
  - Always subtract larger magnitude from smaller
- adding two positives?
  - Overflow *can occur* (Why?)
  - Precision: Add two positives, and get a negative number!
- adding two negatives?
  - Overflow *can occur* (Why?)
  - Precision: add two negatives, get a positive number!


## Rule of thumb:

- Overflow happens iff  
carry into msb  $\neq$  carry out of msb

A	B	C <sub>in</sub>	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Wrong  
Sign

Wrong  
Sign

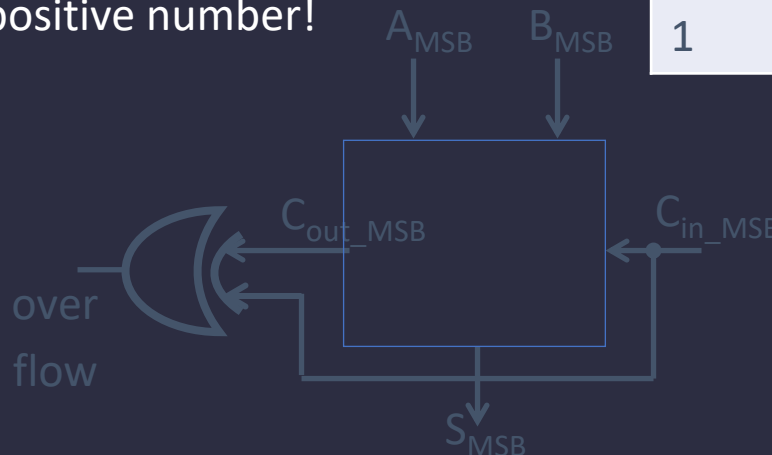

# Youtube Overflow



**YouTube**

Shared publicly · Dec 1, 2014

We never thought a video would be watched in numbers greater than a 32-bit integer ( $=2,147,483,647$  views), but that was before we met PSY. "Gangnam Style" has been viewed so many times we had to upgrade to a 64-bit integer ( $9,223,372,036,854,775,808$ )!

Hover over the counter in PSY's video to see a little math magic and stay tuned for bigger and bigger numbers on YouTube.



# Binary Subtraction

Why create a new circuit?


Just use addition using two's complement math

How?
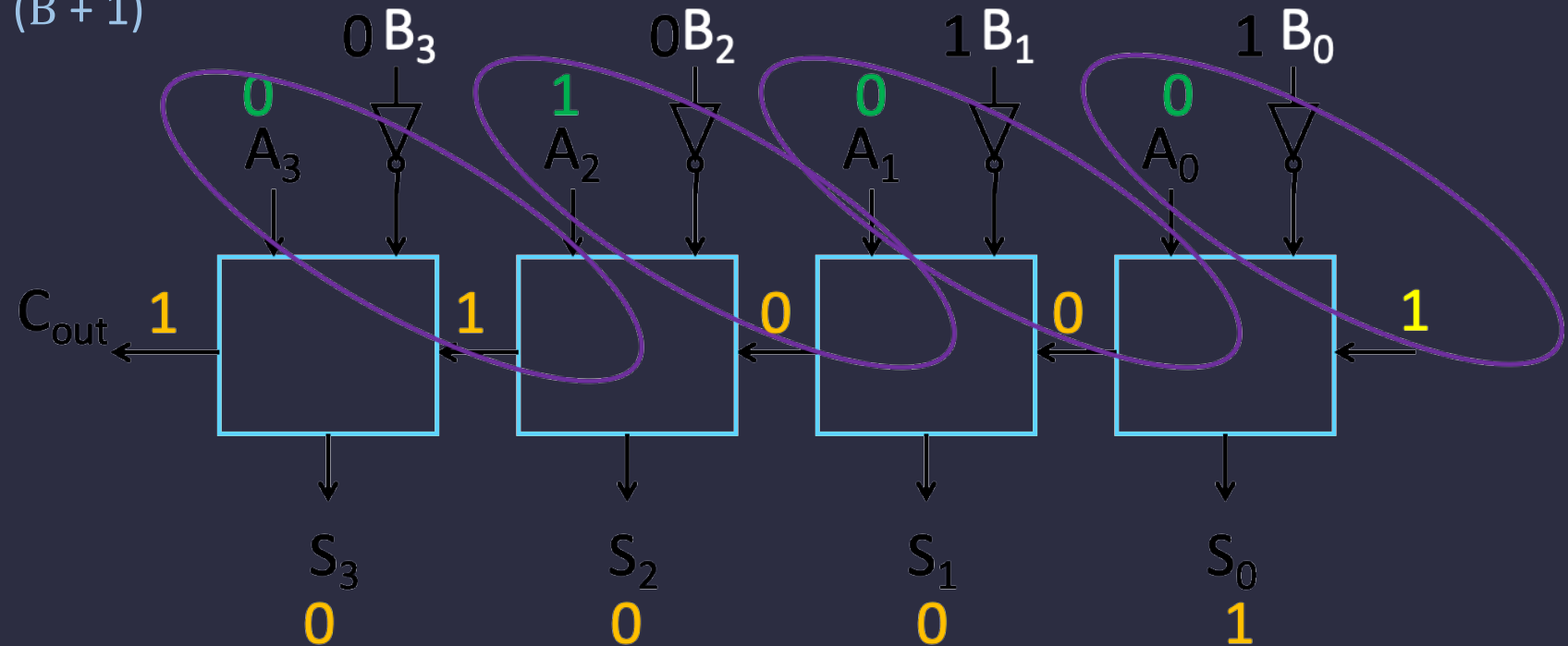
# Binary Subtraction


- Two's Complement Subtraction

- Subtraction is simply addition, where one of the operands has been negated
    - Negation is done by inverting all bits and adding one
- $$A - B = A + (-B) = A + (\bar{B} + 1)$$



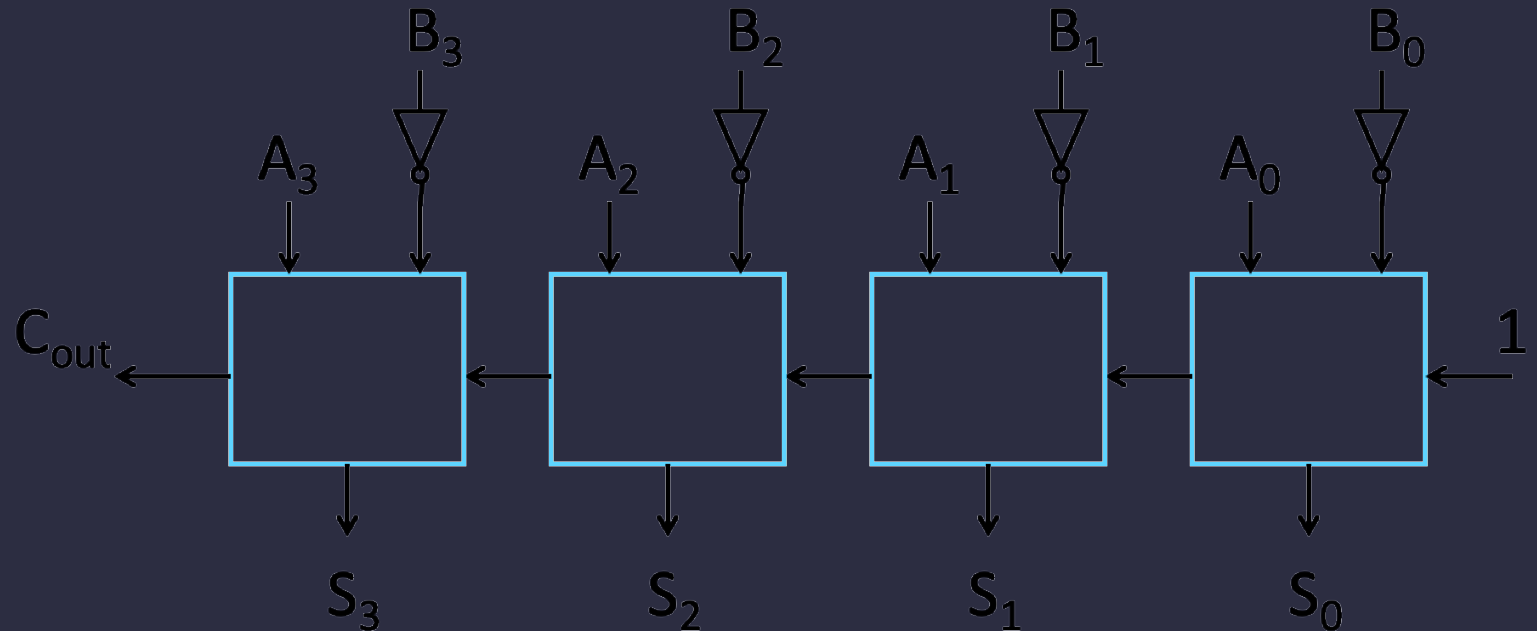
# Binary Subtraction

- Two's Complement Subtraction
  - Subtraction is simply addition, where one of the operands has been negated
    - Negation is done by inverting all bits and adding one
$$A - B = A + (-B) = A + (\bar{B} + 1)$$




# Two's Complement Adder
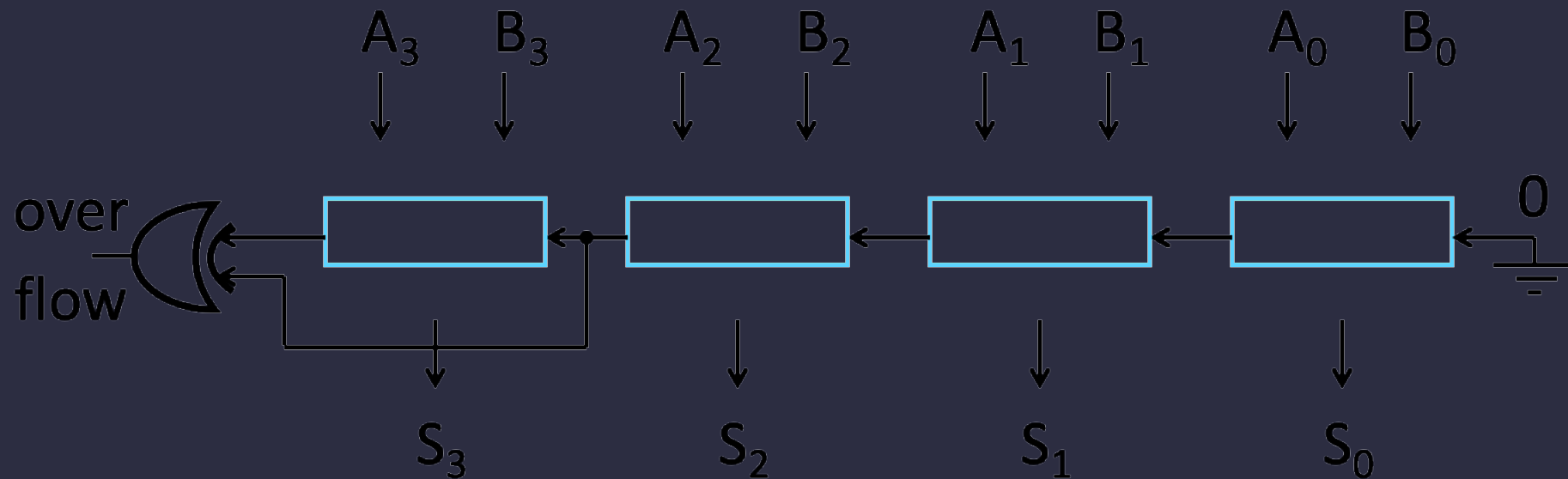
## Two's Complement Adder with overflow detection




# Two's Complement Adder
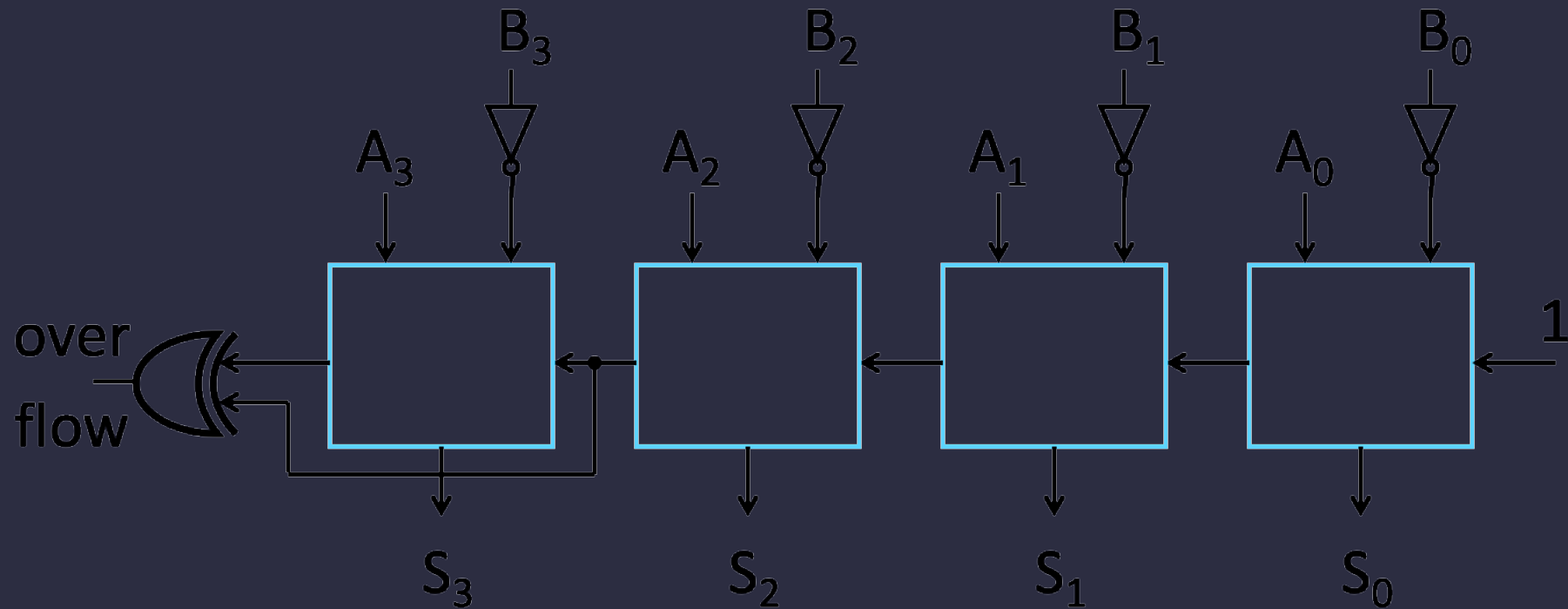
## Two's Complement Adder with overflow detection




# Two's Complement Adder
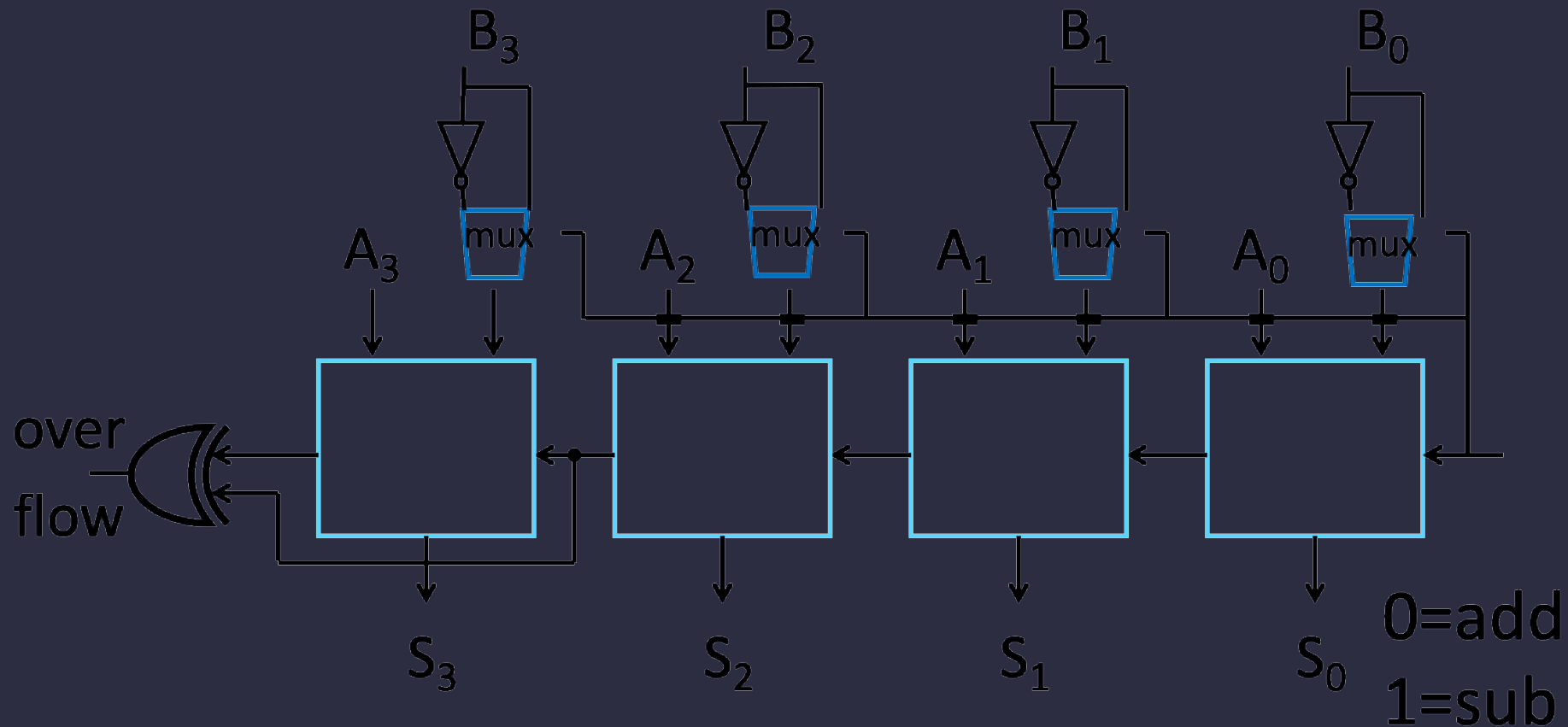
## Two's Complement Adder with overflow detection




# Two's Complement Adder
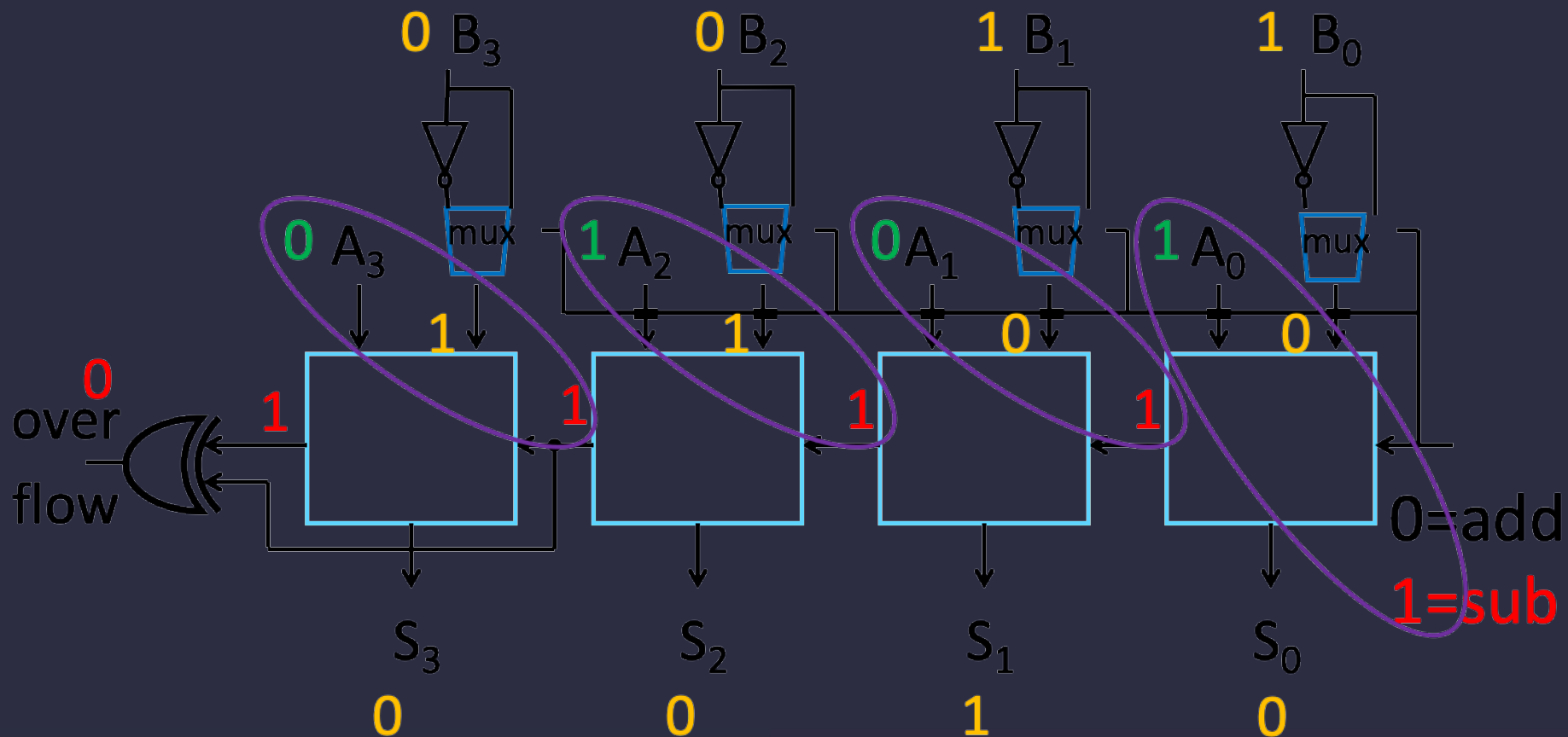
## Two's Complement Adder with overflow detection




# Two's Complement Adder
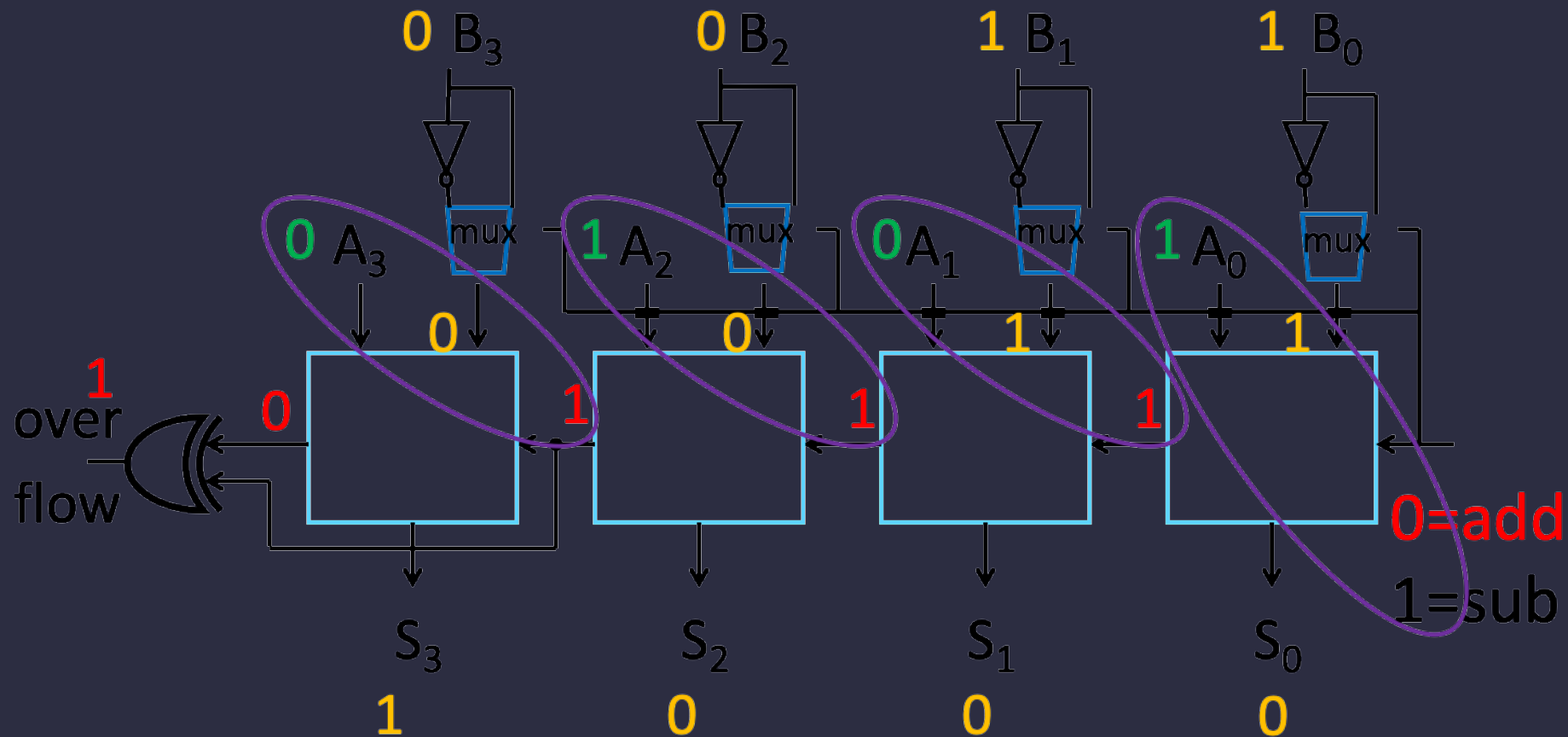
## Two's Complement Adder with overflow detection




# Two's Complement Adder
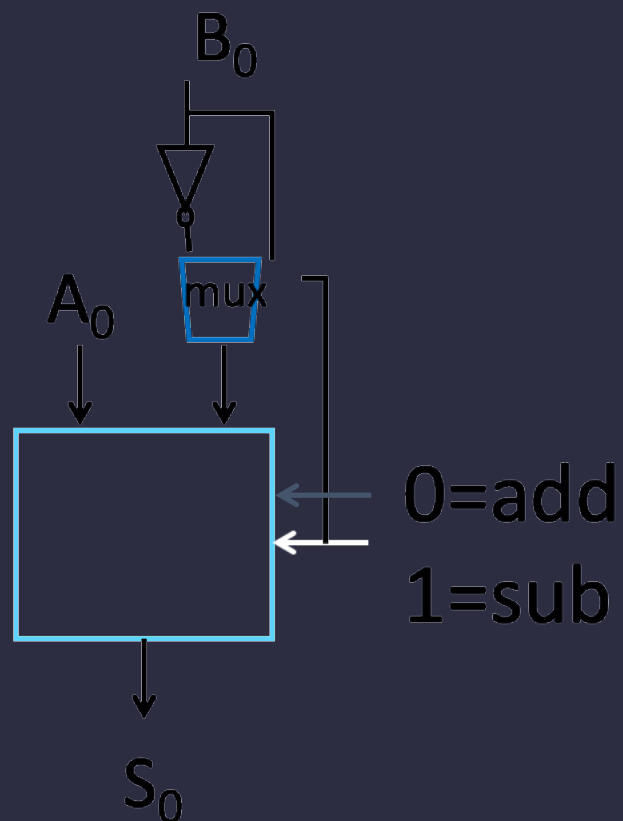
## Two's Complement Adder with overflow detection



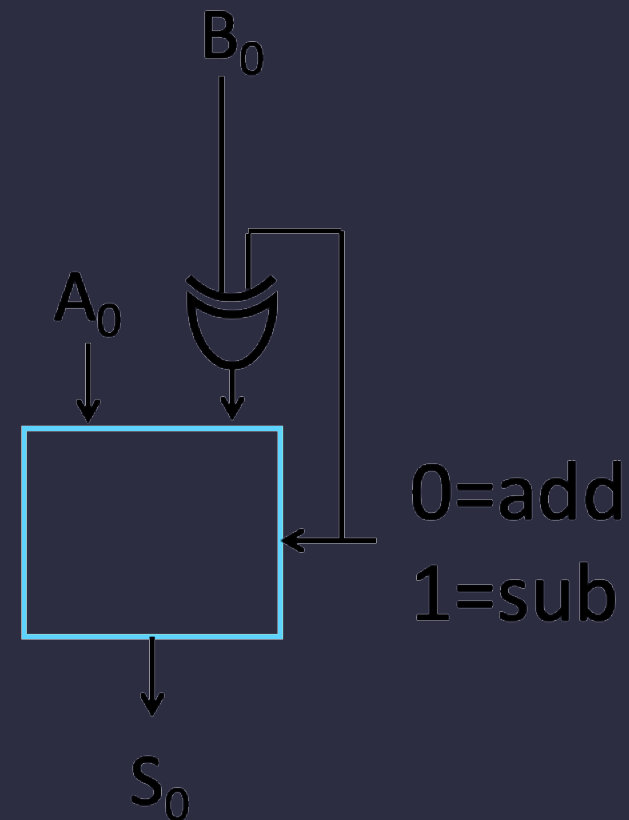Before: 2 inverters, 2 AND gates, 1 OR gate



After: 1 XOR gate