

# Computer Architecture

## Week 3: Combinational and Sequential Circuits



Fenerbahçe University



## Professor and TAs

Prof: Dr. Vecdi Emre Levent

Office: 311

Email: [emre.levent@fbu.edu.tr](mailto:emre.levent@fbu.edu.tr)

TA: Arş. Gör. Uğur Özbalkan


Office: 311

Email: [ugur.ozbalkan@fbu.edu.tr](mailto:ugur.ozbalkan@fbu.edu.tr)

# Course Plan

- Combinational and Sequential Circuits


# Big Picture: Building a Processor

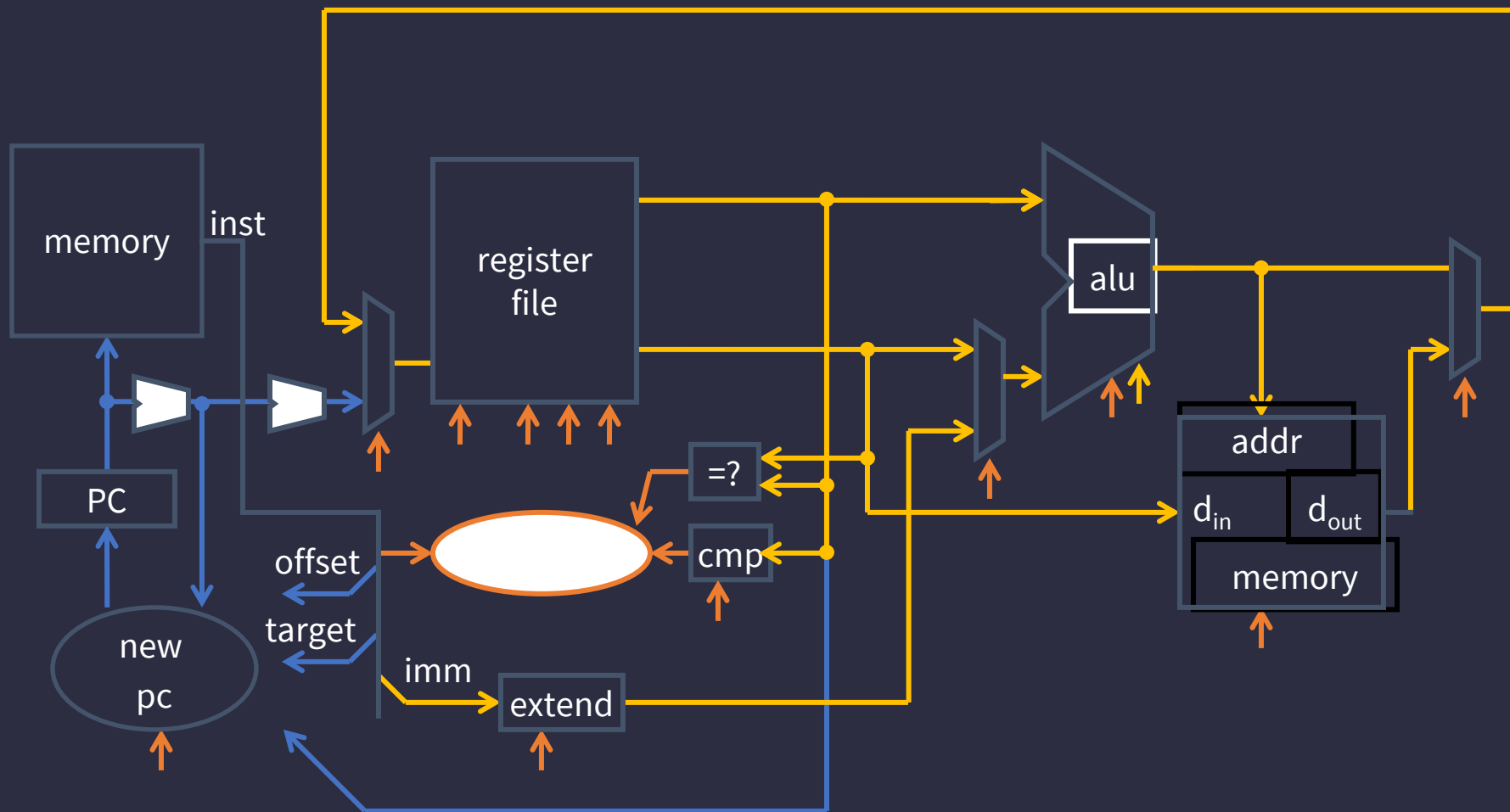

A single cycle processor

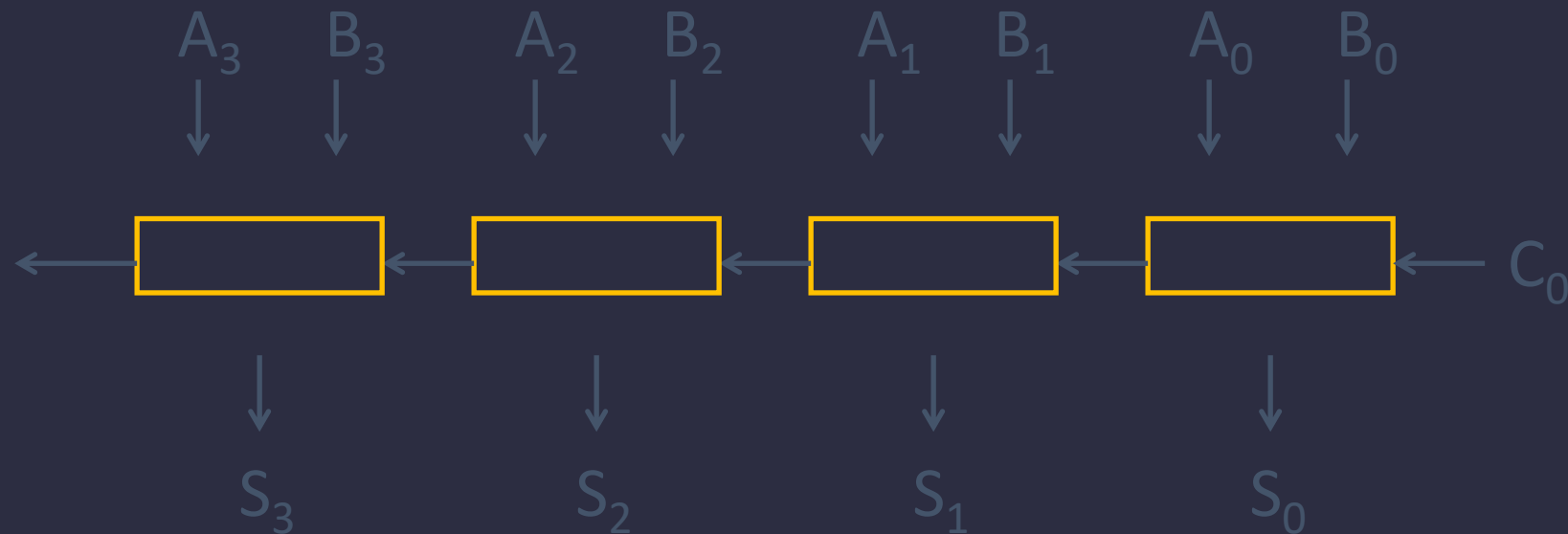
# Review

- We can generalize 1-bit Full Adders to 32 bits, 64 bits ...



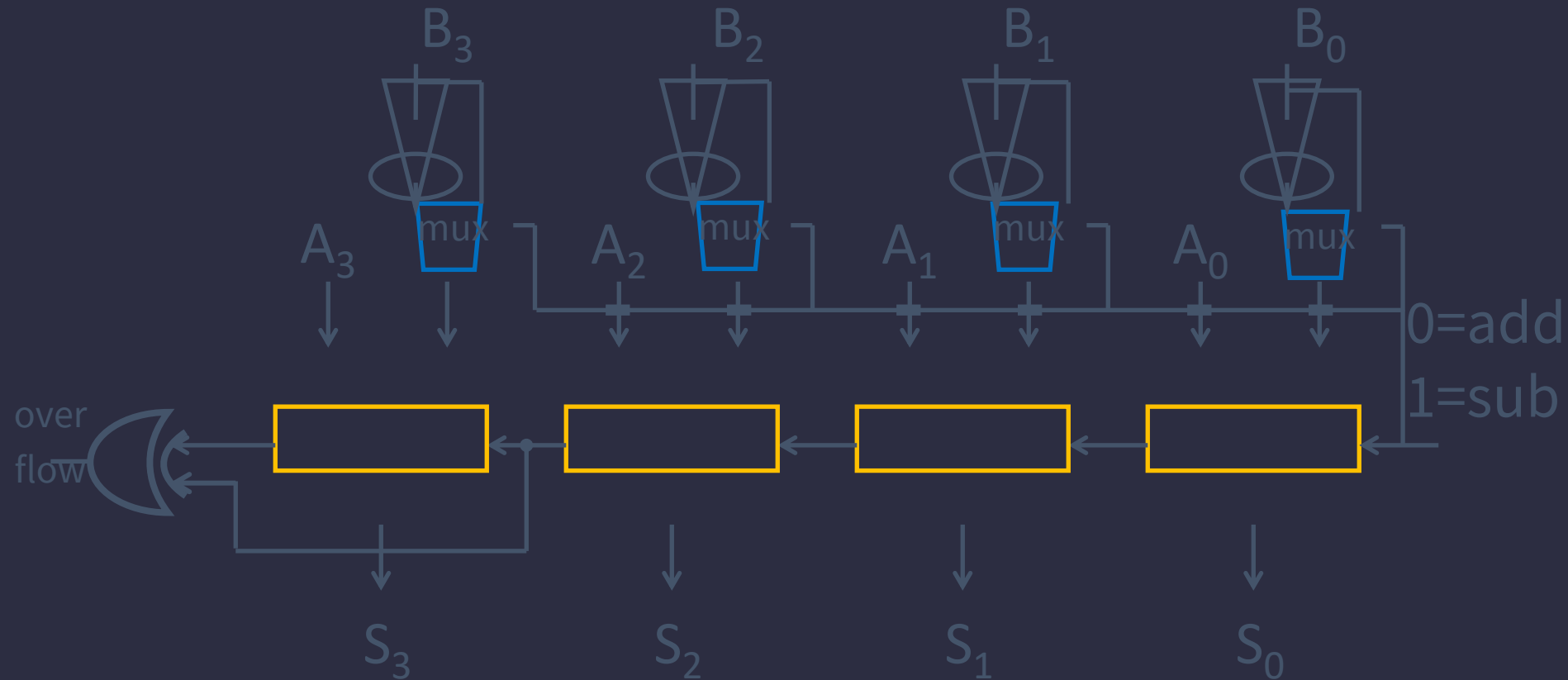
# Review

- We can generalize 1-bit Full Adders to 32 bits, 64 bits ...



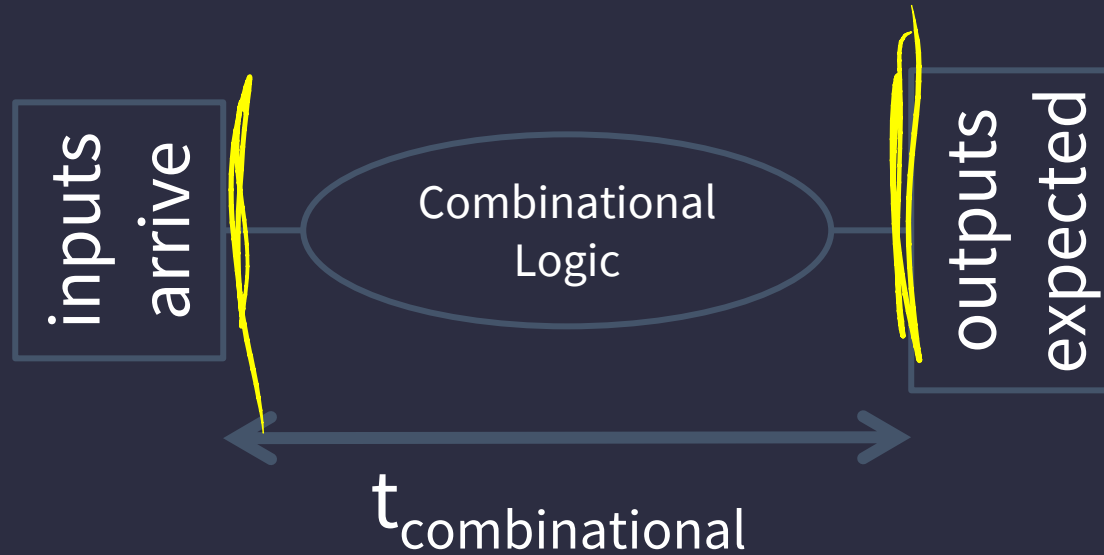
# Performance

Speed of a circuit is affected by the number of gates in series (on the *critical path* or the *deepest level of logic*)



# 4-bit Ripple Carry Adder

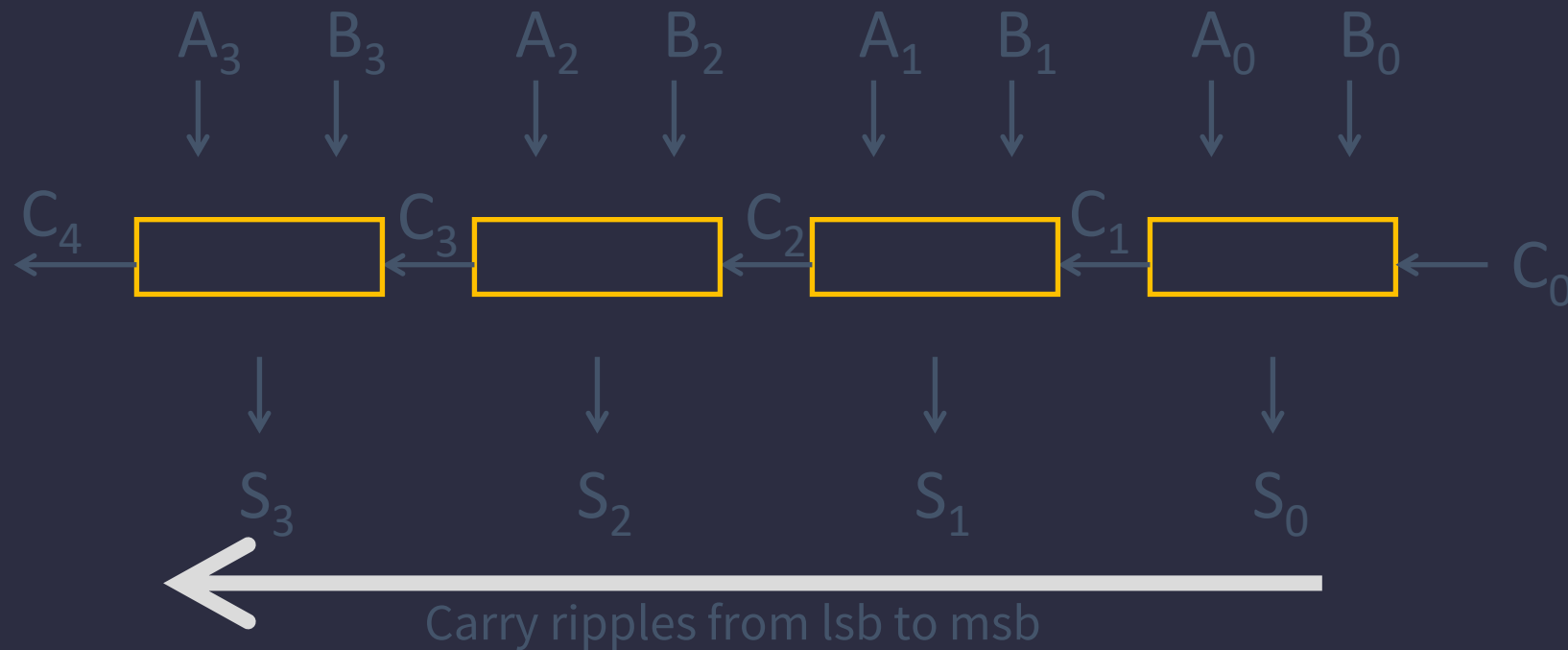

- First full adder, 2 gate delay
- Second full adder, 2 gate delay



# Stateful Components

Until now is combinational logic

- Output is computed when inputs are present
- System has no internal state
- Nothing computed in the present can depend on what happened in the past!



Need a way to record data

Need a way to build stateful circuits

Need a state-holding device

# Goals for Today

## State

- How do we store *one* bit?
- Attempts at storing (and changing) one bit
  - Set-Reset Latch
  - D Latch
  - D Flip-Flops
  - Master-Slave Flip-Flops
- Register: storing more than one bit, N-bits


## Basic Building Blocks

- Decoders and Encoders

# Goal

How do we store store *one* bit?


# First Attempt: Unstable Devices

 

# First Attempt: Unstable Devices


Does not work!

- Unstable
- Oscillates wildly!

 



## Second Attempt: Bistable Devices

- Stable and unstable equilibria?

 


A Simple Device

In stable state,  $\bar{A} = B$

  


How do we change the state?

# Third Attempt: Set-Reset Latch

 

# Third Attempt: Set-Reset Latch

 

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0


S	R	Q	$\bar{Q}$
0	0		
0	1		
1	0		
1	1		

Set-Reset (S-R) Latch

Stores a value Q and its complement



# Third Attempt: Set-Reset Latch

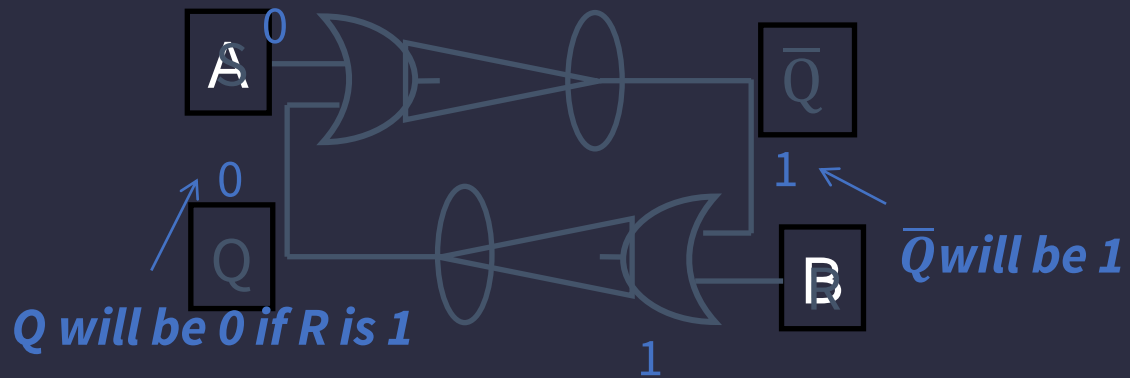


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

S	R	Q	$\bar{Q}$
0	0		
0	1	0	1
1	0		
1	1		

Set-Reset (S-R) Latch

Stores a value Q and its complement

# Third Attempt: Set-Reset Latch

 

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Set-Reset (S-R) Latch  
Stores a value Q and its complement


S	R	Q	Q̄
0	0		
0	1	0	1
1	0	1	0
1	1		

What are the values for Q and Q̄?

- a) 0 and 0
- b) 0 and 1
- c) 1 and 0
- d) 1 and 1

iClicker Question

# Third Attempt: Set-Reset Latch

 


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1		

Set-Reset (S-R) Latch

Stores a value  $Q$  and its complement

# Third Attempt: Set-Reset Latch

 

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0


S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	?	?

## Set-Reset (S-R) Latch

Stores a value Q and its complement

What happens when S,R changes from 1,1 to 0,0?

# Third Attempt: Set-Reset Latch

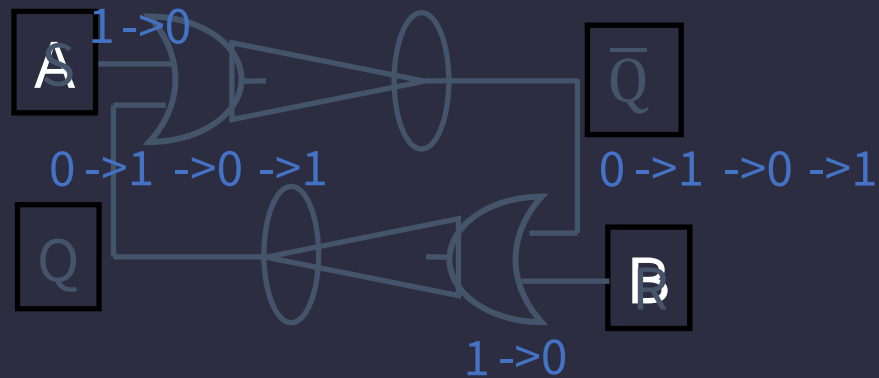

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	forbidden	



## Set-Reset (S-R) Latch

Stores a value  $Q$  and its complement

What happens when  $S, R$  changes from 1,1 to 0,0?

$Q$  and  $\bar{Q}$  become unstable and will oscillate wildly between values 0,0 to 1,1 to 0,0 to 1,1 ...

# Third Attempt: Set-Reset Latch

  

S	R	Q	$\bar{Q}$	
0	0	Q	$\bar{Q}$	hold
0	1	0	1	reset
1	0	1	0	set
1	1	forbidden		

Set-Reset (S-R) Latch

Stores a value Q and its complement

## Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit.



But, SR Latch has a forbidden state.

## Next Goal

How do we avoid the forbidden state of S-R Latch?



# Fourth Attempt: (Unclocked) D Latch

  

## Data (D) Latch

- Easier to use than an SR latch
- No possibility of entering an undefined state

## When D changes, Q changes

- ... immediately (...after a delay of 2 Ors and 2 NOTs)

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

D	Q	$\bar{Q}$
0	0	1
1	1	0

## Need to control when the output changes


## Next Goal

How do we coordinate state changes to a D Latch?
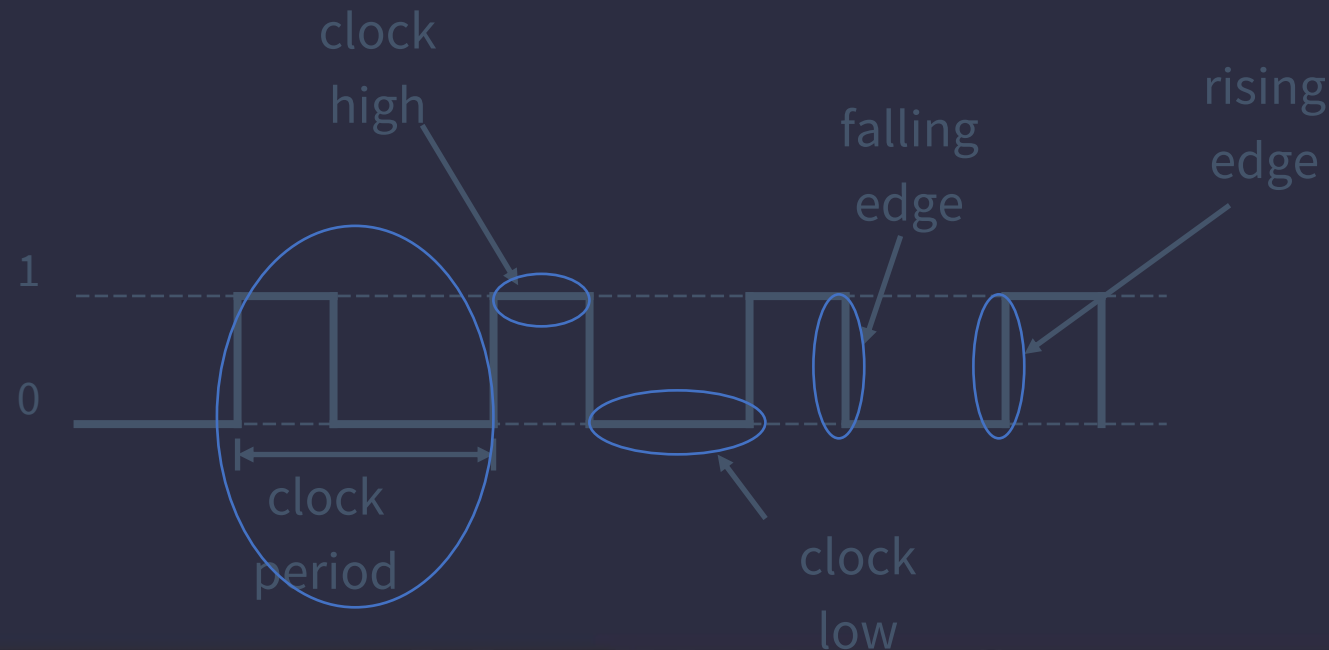
## Aside: Clocks

Clock helps coordinate state changes

- Usually generated by an oscillating crystal
- Fixed period
- Frequency =  $1/\text{period}$



# Clock Disciplines

## Level sensitive

- State changes when clock is high (or low)



## Edge triggered

- State changes at clock edge

positive edge-triggered




negative edge-triggered



# Clock Methodology

## Clock Methodology

- Negative edge, synchronous

 


Edge-Triggered  $\rightarrow$  signals must be stable near falling edge

“near” = before and after

$t_{\text{setup}}$   $t_{\text{hold}}$


## Round 2: D Latch (1)

 

C = 1, D Latch *transparent*:  
set/reset (according to D)

C = 0, D Latch *opaque*:  
keep state (ignore D)

S	R	Q	$\bar{Q}$	
0	0	Q	$\bar{Q}$	hold
0	1	0	1	reset
1	0	1	0	set
1	1	forbidden		

 


- Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- C enables changes

C	D	Q	$\bar{Q}$	
0	0	Q	$\bar{Q}$	No Change
0	1	Q	$\bar{Q}$	
1	0	0	1	Reset
1	1	1	0	Set
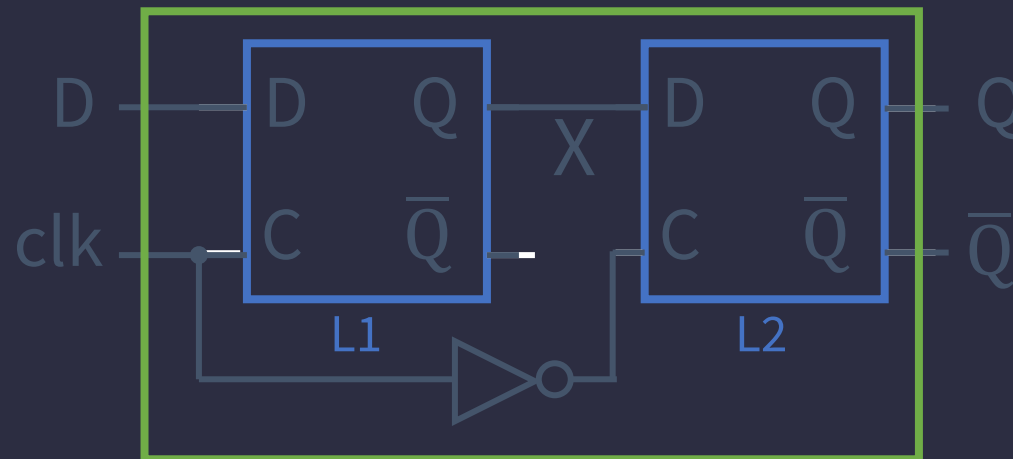
# Round 3: D Flip-Flop

- Edge-Triggered
- Data captured when clock high
- Output changes only on falling edges




# Round 3: D Flip-Flop

**Clock = 1:** L1 *transparent*

L2 *opaque*

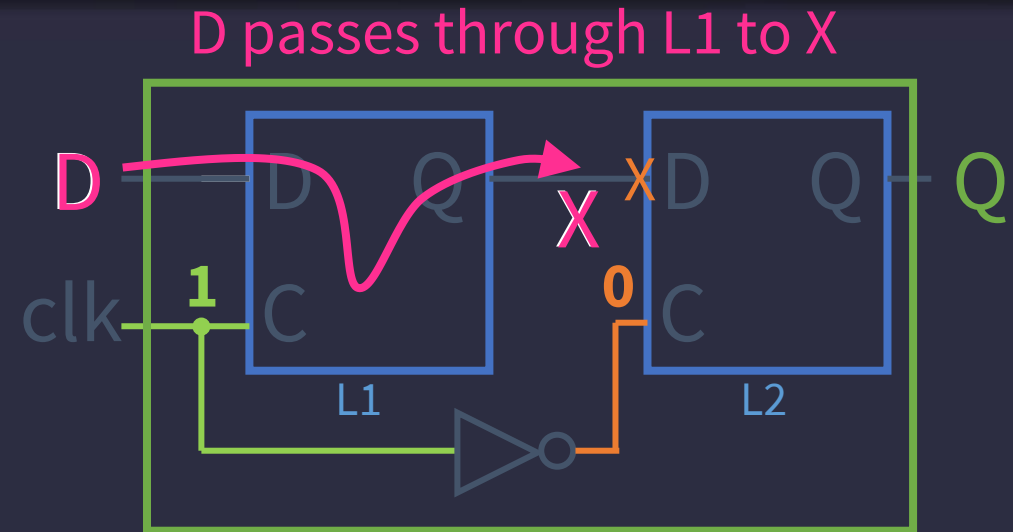
When **CLK** rises ( $0 \rightarrow 1$ ),  
now **X** can change,  
**Q** does not change



**Clock = 0:** L1 *opaque*


L2 *transparent*

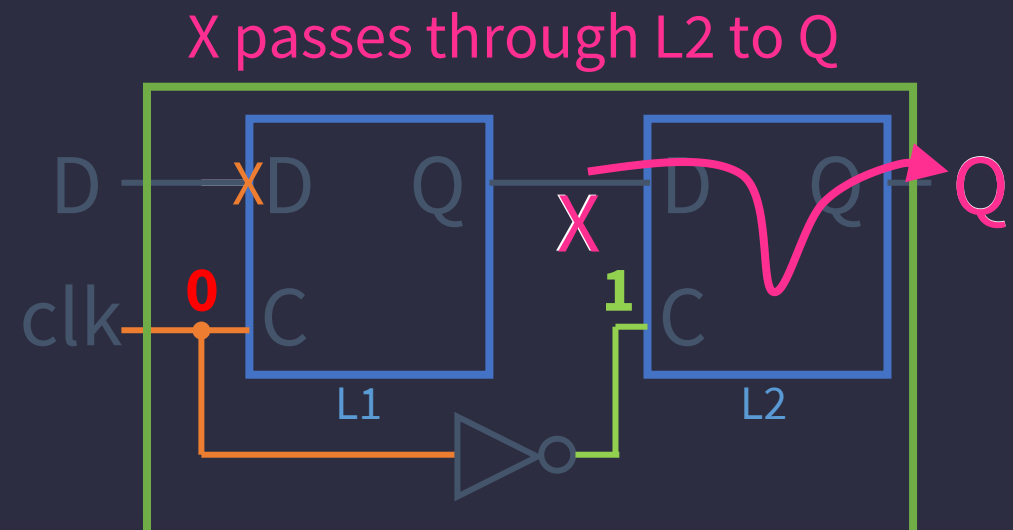When **CLK** falls ( $1 \rightarrow 0$ ),  
**Q** gets **X**, **X** cannot change






# Example

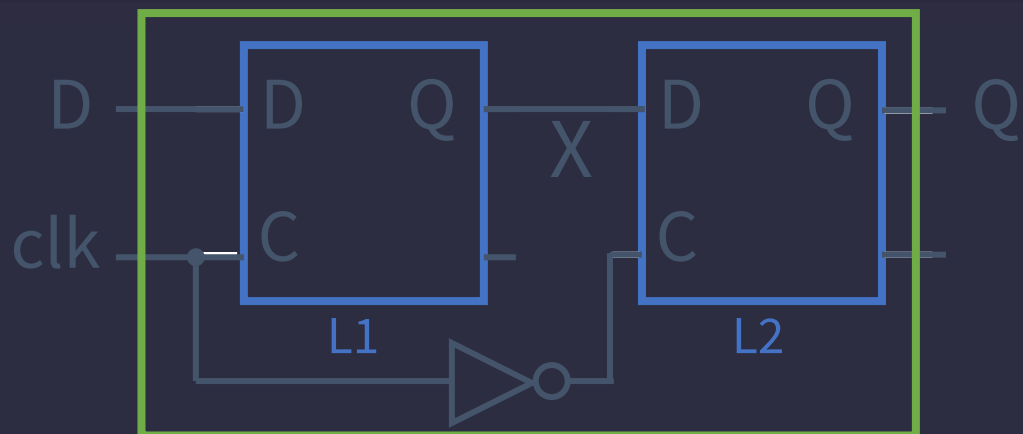



$A = 1, B = 0$

 

# Edge-Triggered D Flip-Flop
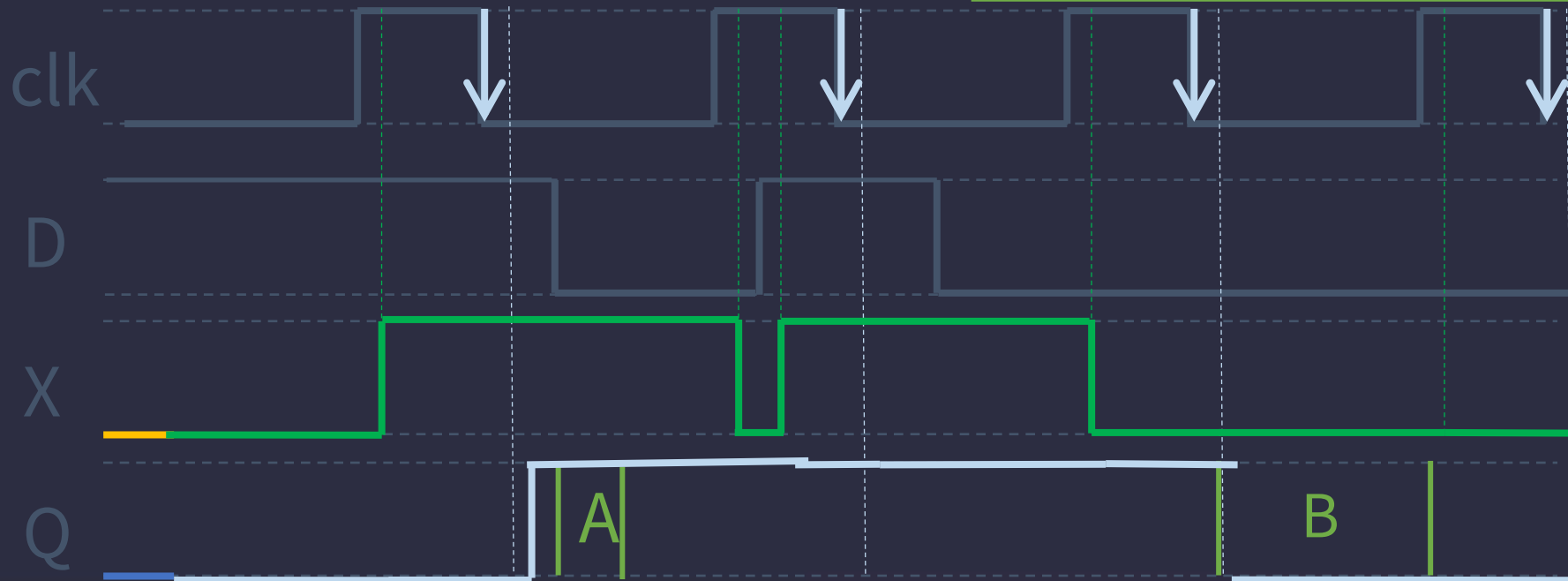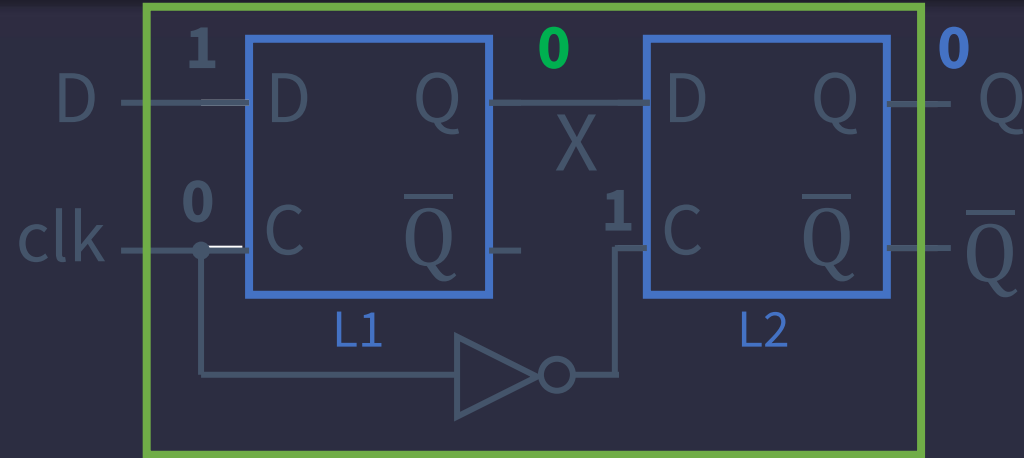
## D Flip-Flop

- Edge-Triggered
- Data captured when clock is high
- Output changes only on falling edges






## Next Goal

How do we store more than one bit,  $N$  bits?


# Registers
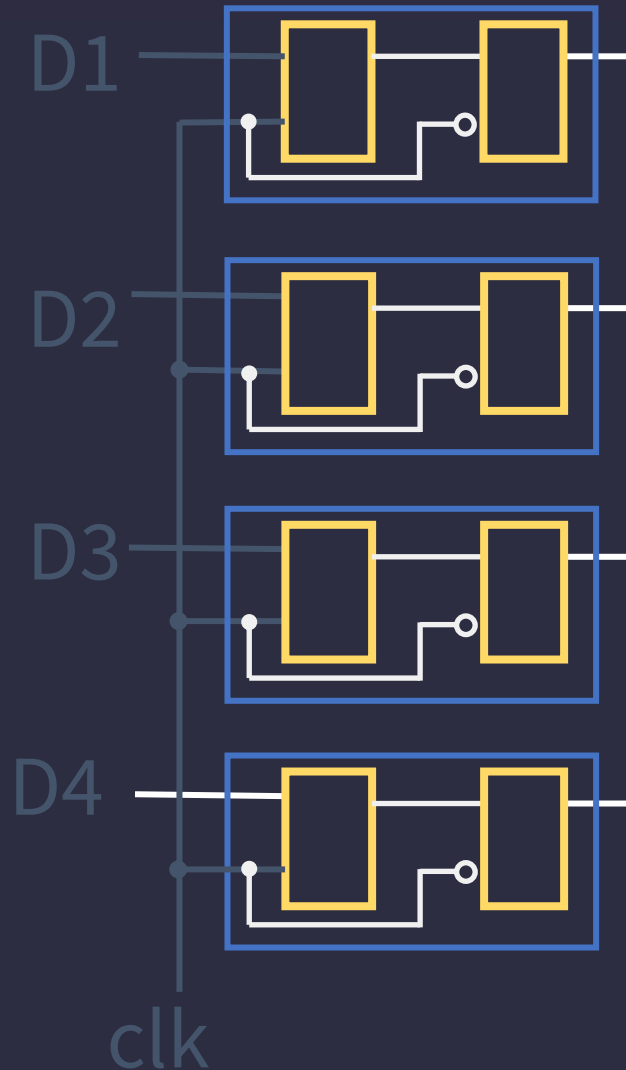
## Register


- D flip-flops in parallel
- shared clock
- extra clocked inputs: write\_enable, reset, ...



# An Example: What will this circuit do?

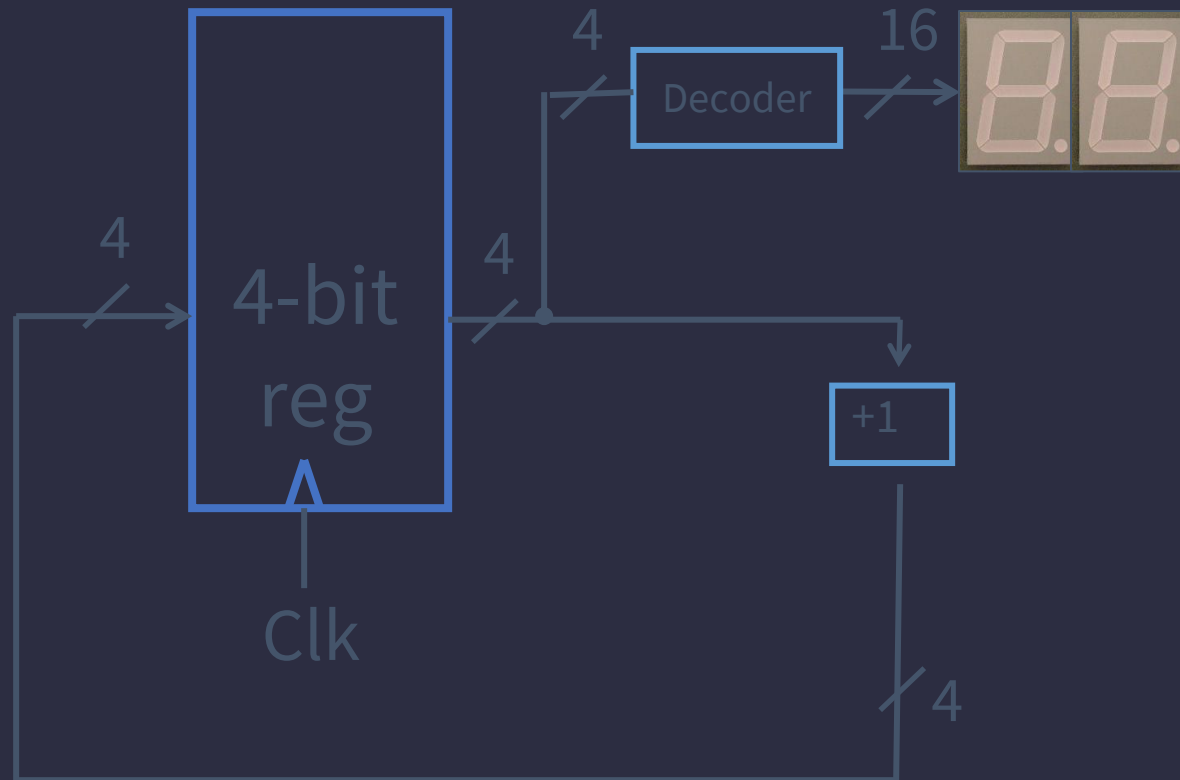

# An Example: What will this circuit do?

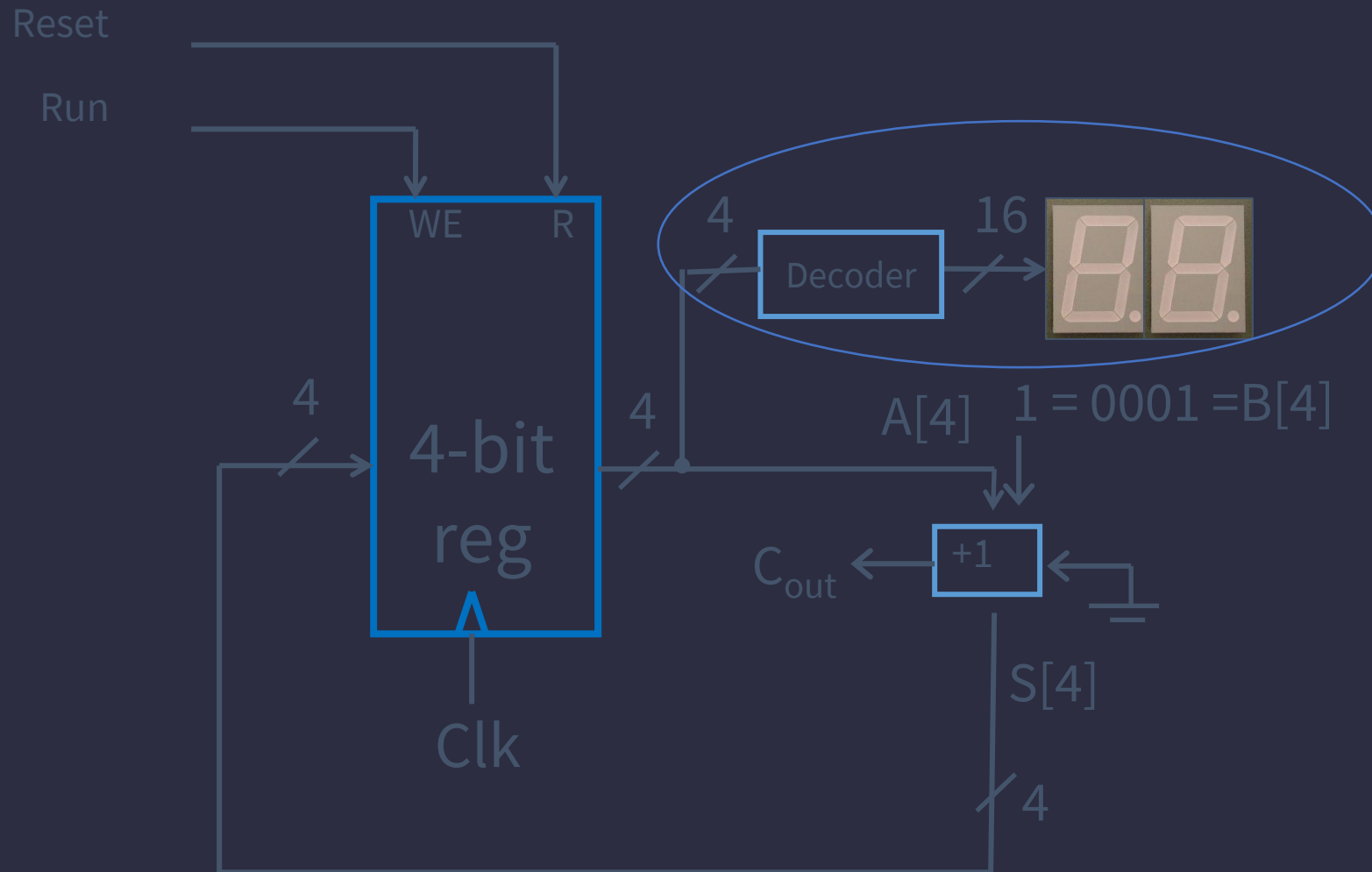

# Decoder Example: 7-Segment LED

## 7-Segment LED


- photons emitted when electrons fall into holes



# Decoder Example: 7-Segment LED
 
## 7-Segment LED

- photons emitted when electrons fall into holes



$d_0$  1 2 3 4 5 6 7  
 5 = 0 1 1 0 1 0 1 1




# Decoder Example: 7-Segment LED Decoder

3 inputs

- encode 0 – 7 in binary

7 outputs

- one for each LED



 


# 7 Segment LED Decoder Implementation

b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0	1	1	1	0	1	1	1
0	0	1	1	0	0	0	0	0	1
0	1	0	0	1	1	1	0	1	1
0	1	1	1	1	0	1	0	1	1
1	0	0	1	0	0	1	1	0	1
1	0	1	1	1	0	1	1	1	0
1	1	0	1	1	1	1	1	1	0
1	1	1	1	0	0	0	0	1	1



# Basic Building Blocks We have Seen

 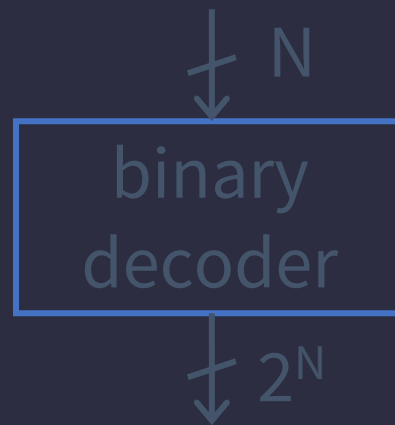 

# Encoders

