

Computer Architecture

Week 4: Finite State Machine



Fenerbahçe University



Professor & TAs

Prof: Dr. Vecdi Emre Levent

Office: 311

Email: emre.levent@fbu.edu.tr

TA: Arş. Gör. Uğur Özbalkan

Office: 311

Email: ugur.ozbalkan@fbu.edu.tr



Course Plan

- Finite State Machine

Stateful Components

Combinational logic

- Output computed directly from inputs
- System has no internal state
- Nothing depends on the past!



Need:

- To record data
- To build stateful circuits
- A state-holding device

Sequential Logic & Finite State Machines

Finite State Machines

An electronic machine which has

- external inputs
- externally visible outputs
- internal state

Output and next state depend on

- inputs
- current state

Abstract Model of FSM

Machine is

$$M = (S, I, O, \delta)$$

S : Finite set of states

I : Finite set of inputs


O : Finite set of outputs

δ : State transition function

Next state depends on present input *and* present state



Automata Model

Finite State Machine

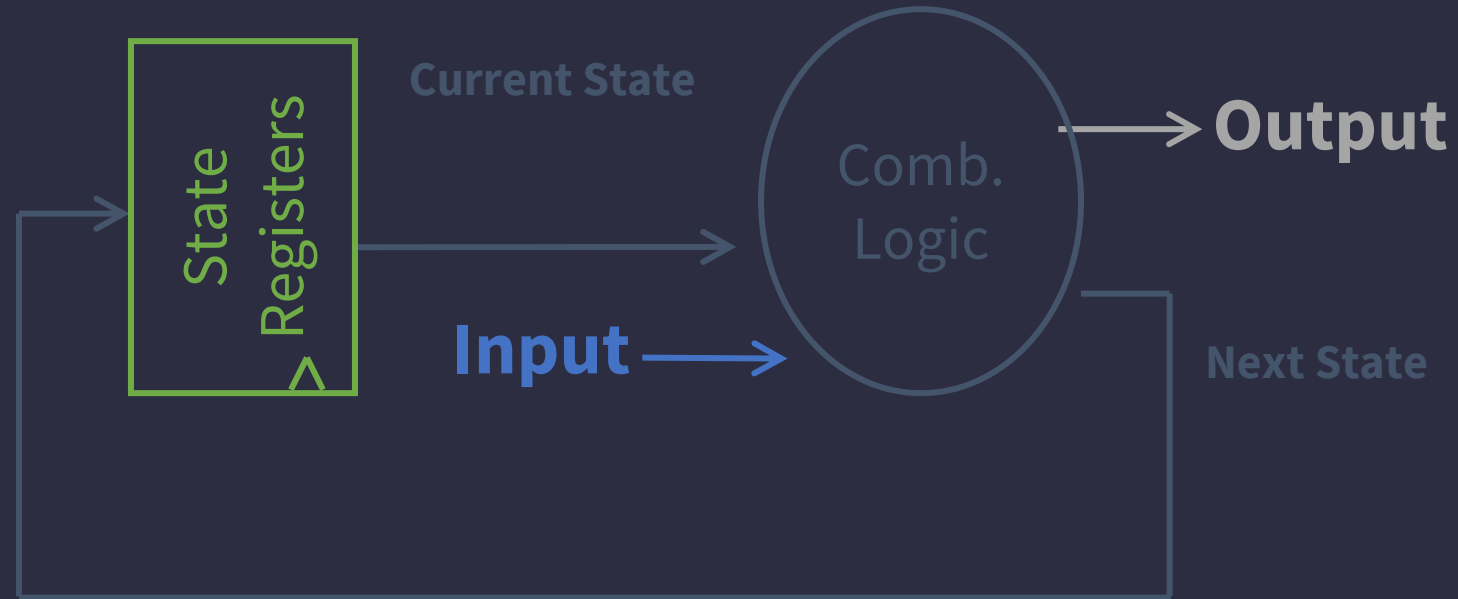

- inputs from external world
- outputs to external world
- internal state
- combinational logic

FSM Example

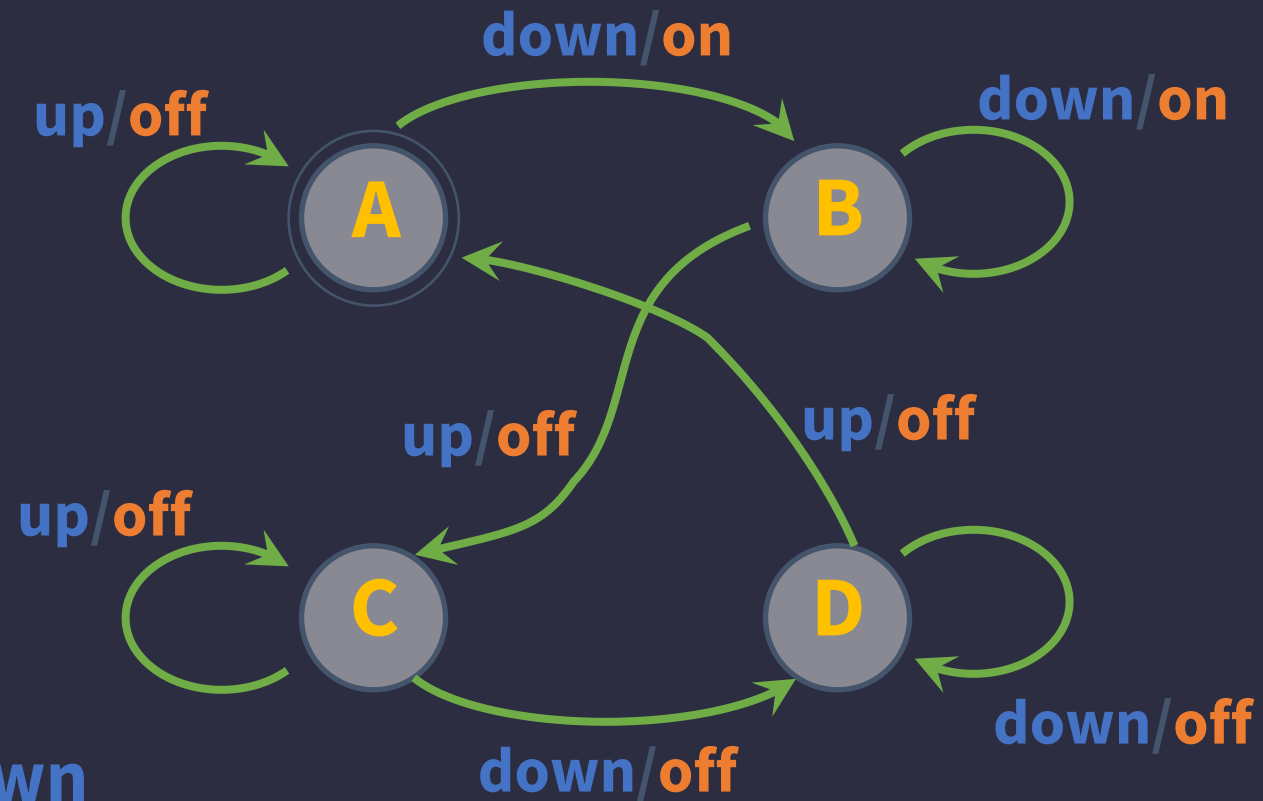
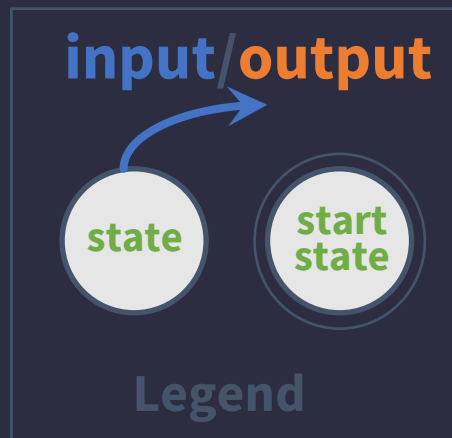


Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

FSM Example

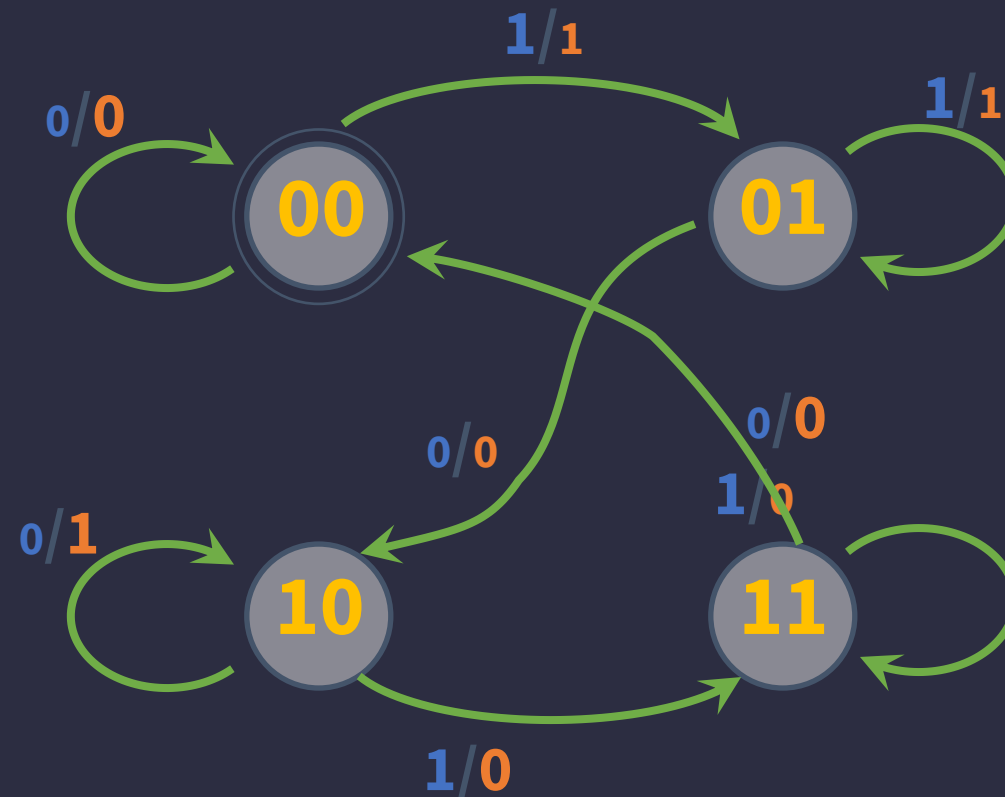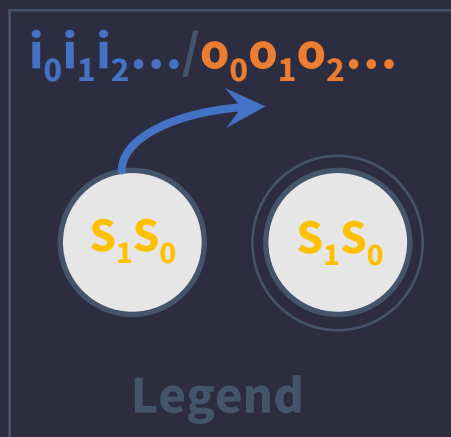


Input: **0**=up or **1**=down

Output: **1**=on or **0**=off

States: **00**=A, **01**=B, **10**=C, or **11**=D

Mealy Machine


General Case: Mealy Machine

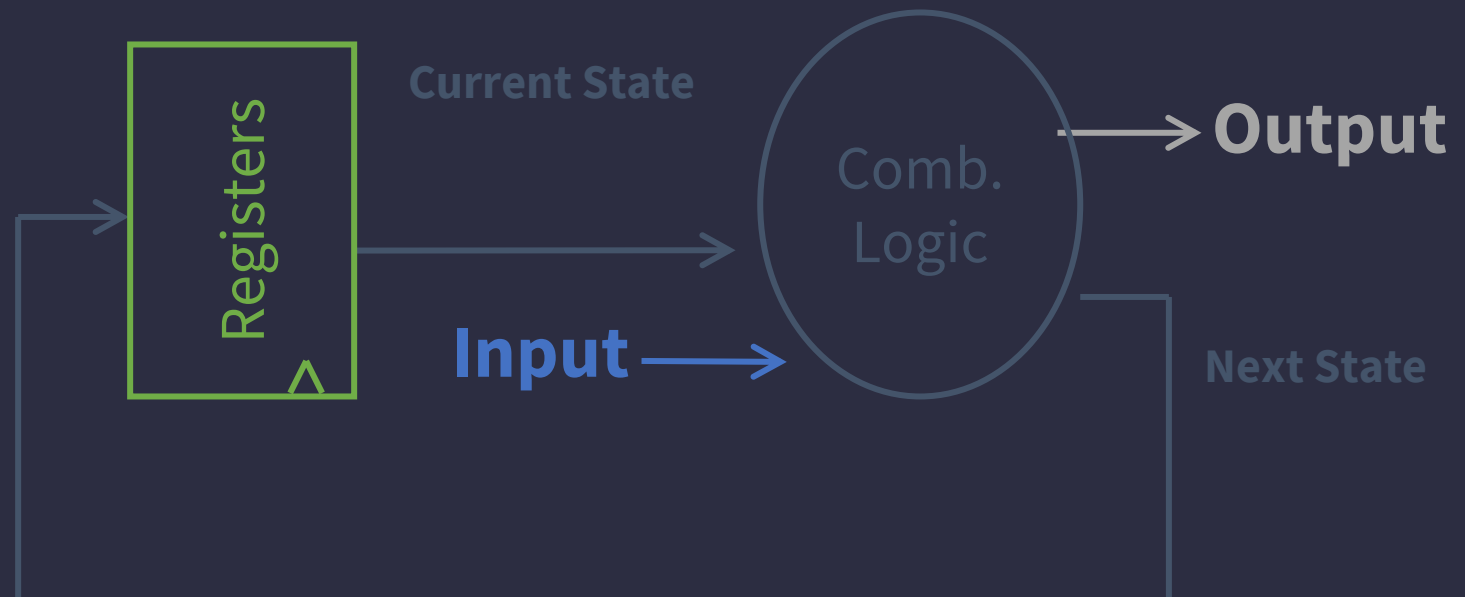

Outputs and next state depend on both current state and input



Moore Machine

Special Case: Moore Machine

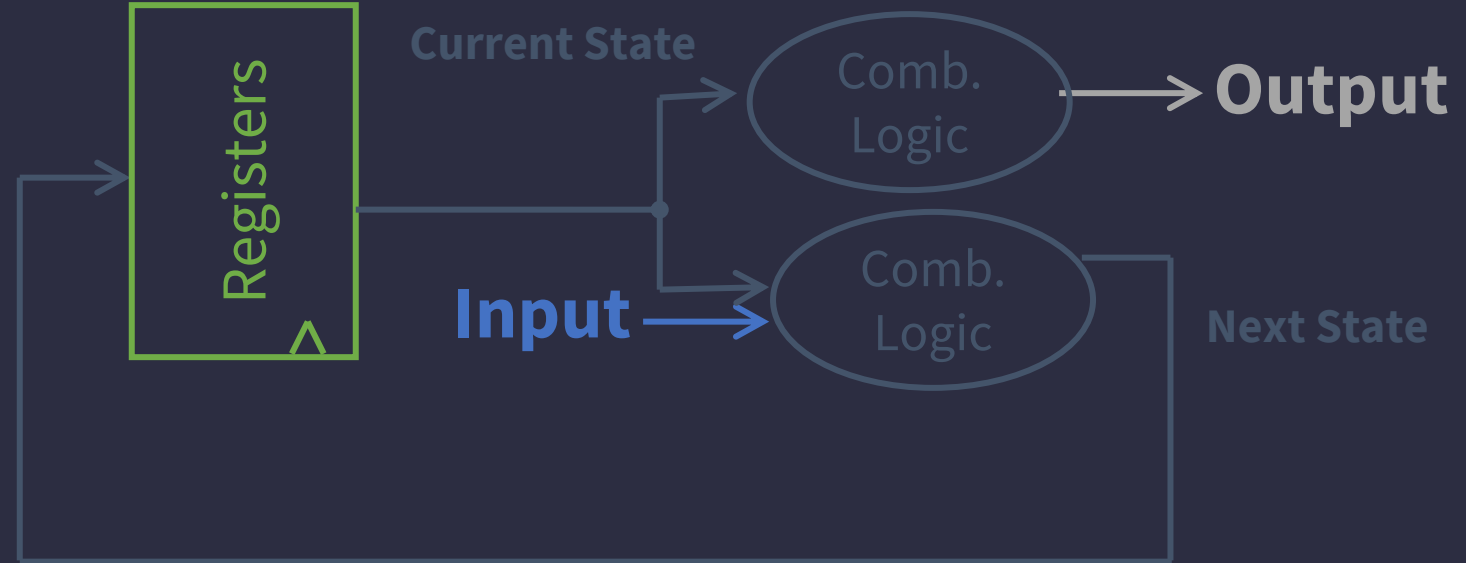

Outputs depend only on current state

Moore Machine FSM Example

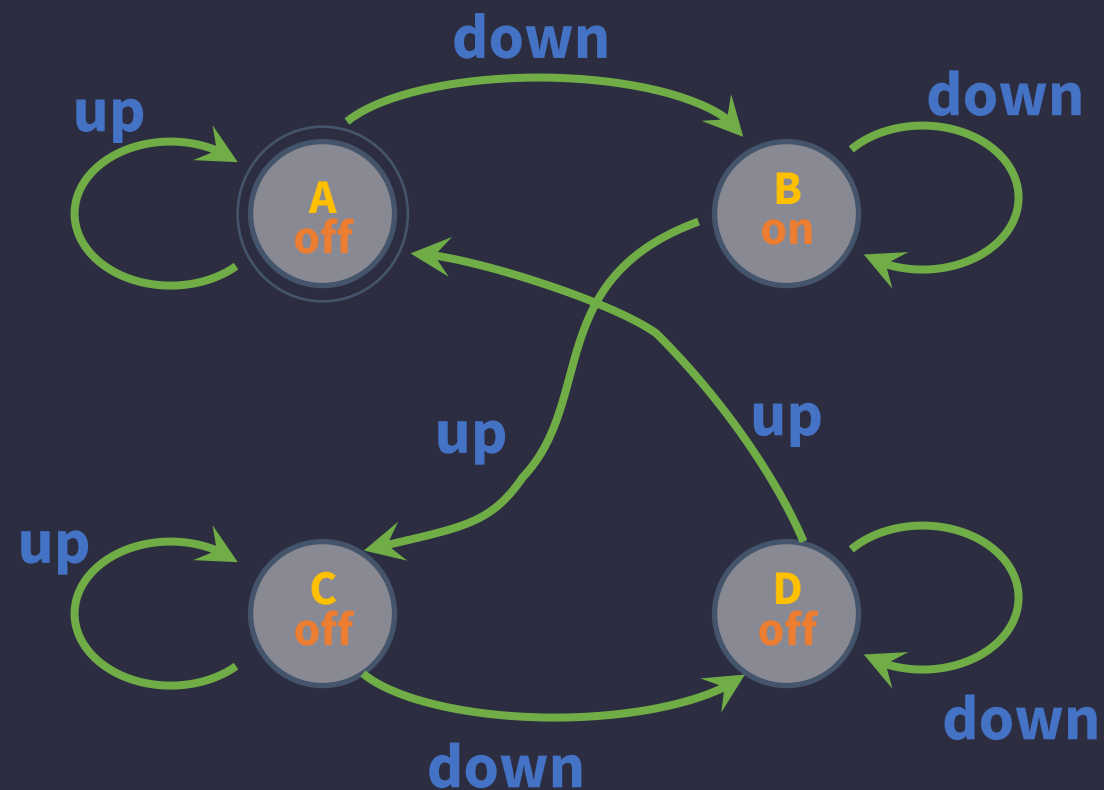
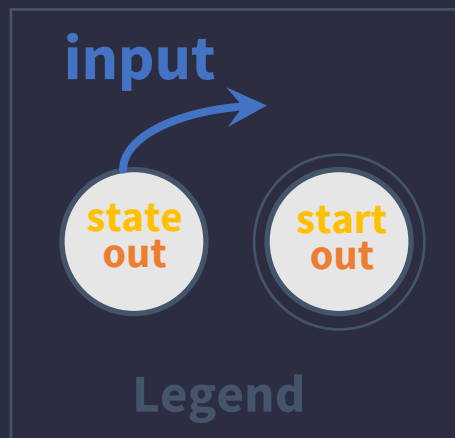


Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

Mealy Machine FSM Example

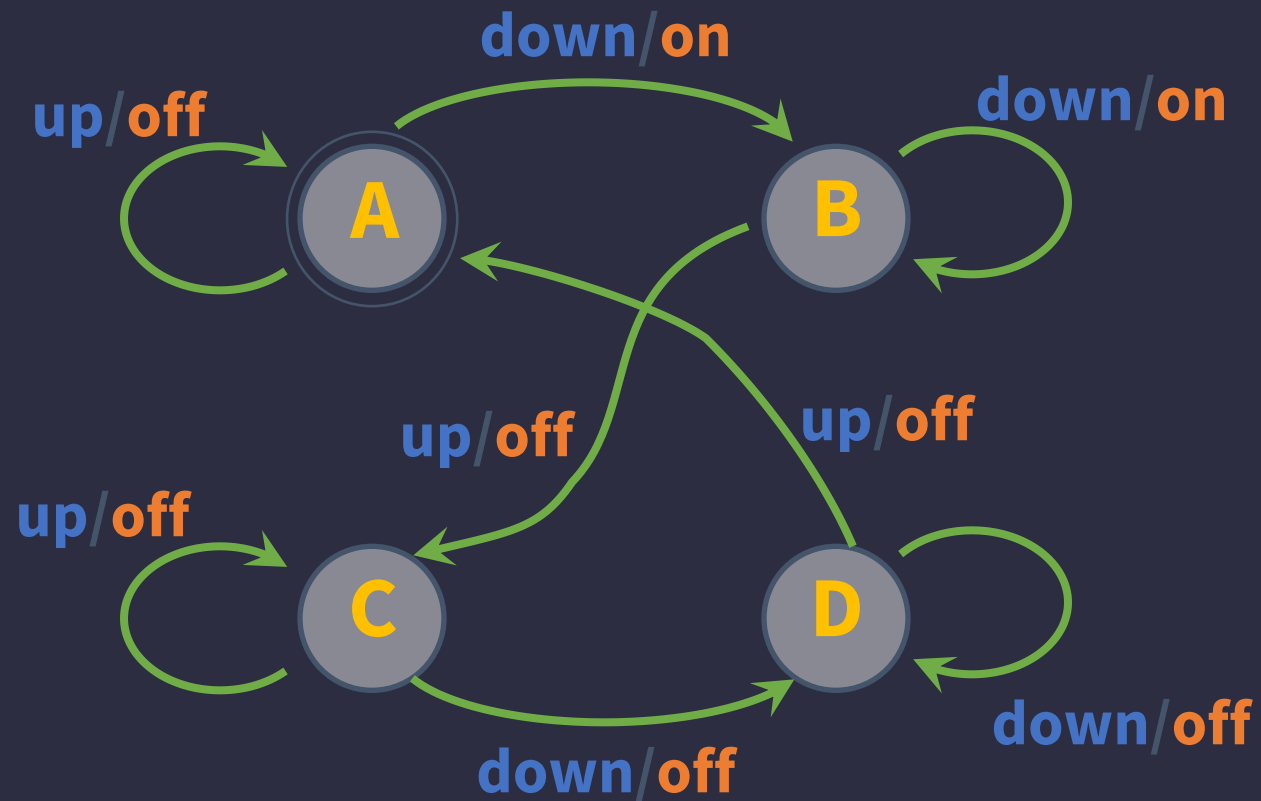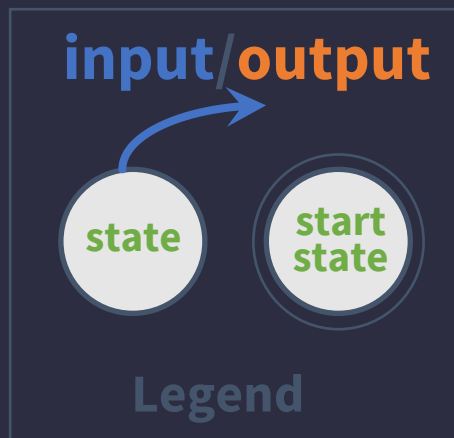


Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

FSM Example

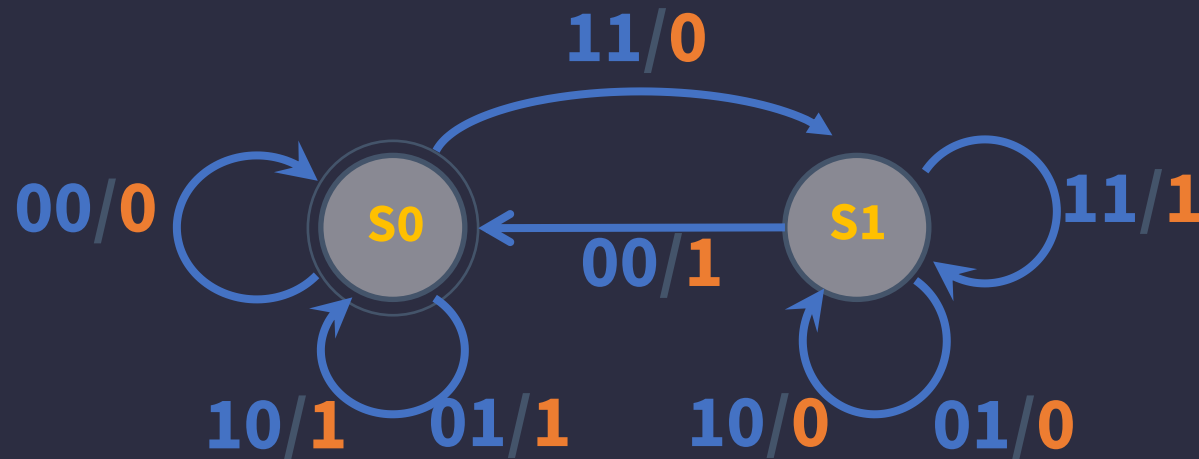

Two states: S0 (no carry in), S1 (carry in)


Inputs: a and b

Output: z

- z is the sum of inputs a, b, and carry-in (one bit at a time)
- A carry-out *is* the next carry-in state.
- Arcs labeled with input bits a and b, and output z


FSM Example

a	b	Current state	z	Next state
0	0	S0	0	S0
0	1	S0	1	S0
1	0	S0	1	S0
1	1	S0	0	S1
0	0	S1	1	S0
0	1	S1	0	S1
1	0	S1	0	S1
1	1	S1	1	S1

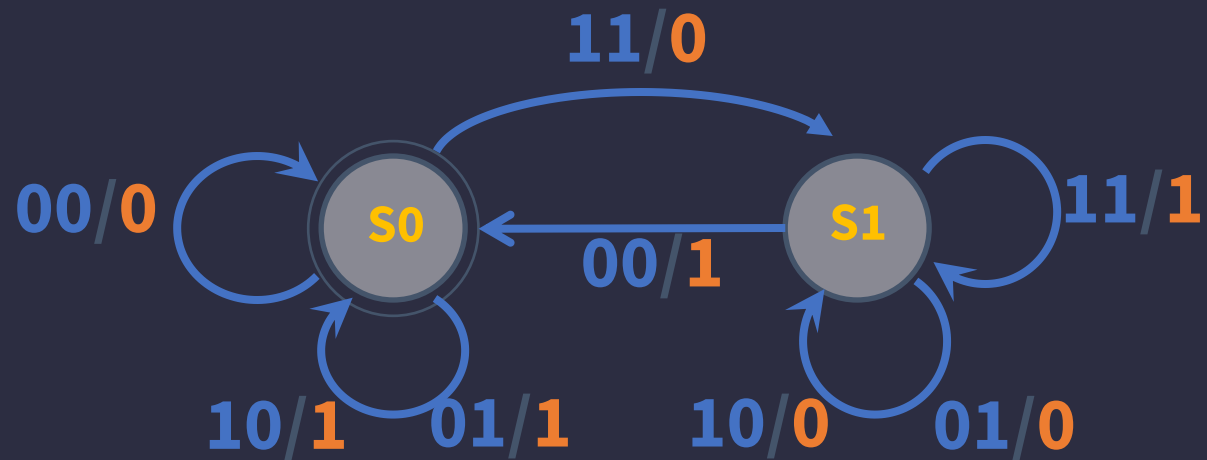

FSM Example

a	b	s	z	s'
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

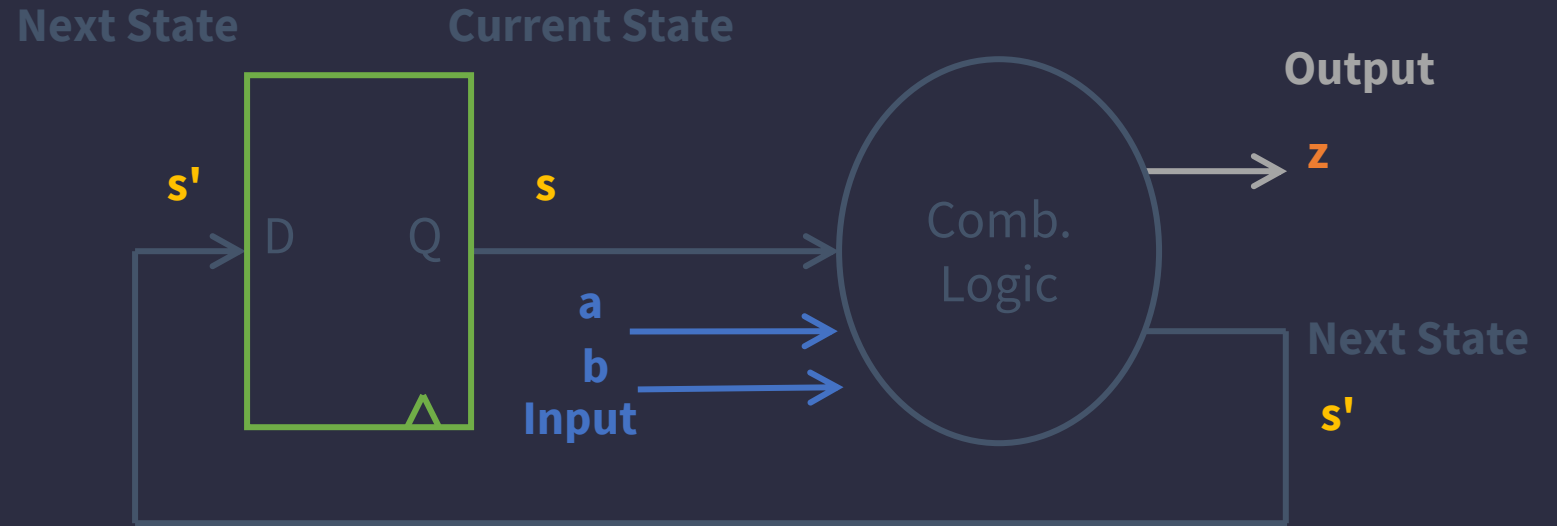


Combinational Logic Equations

$$z = \bar{a}b\bar{s} + a\bar{b}s + \bar{a}\bar{b}s + abs$$

$$s' = ab\bar{s} + \bar{a}bs + a\bar{b}s + abs$$

Mealy Machine


General Case: Mealy Machine

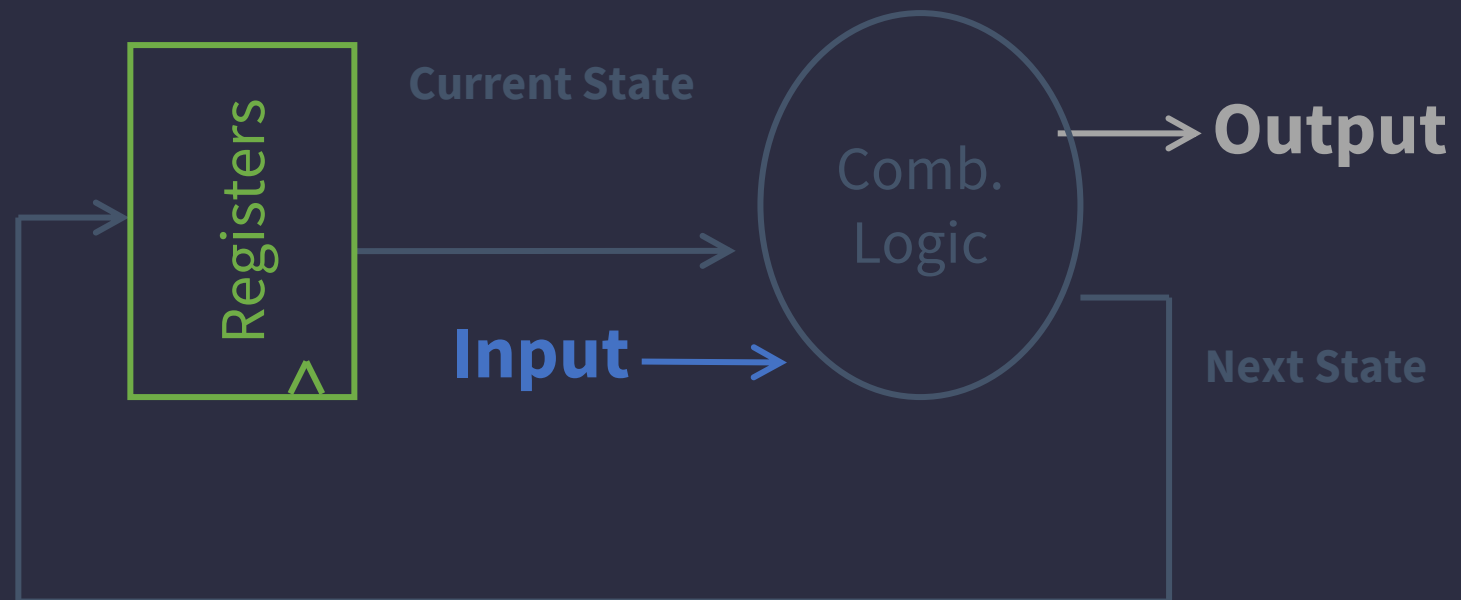

Outputs and next state depend on both current state and input

Moore Machine

Special Case: Moore Machine

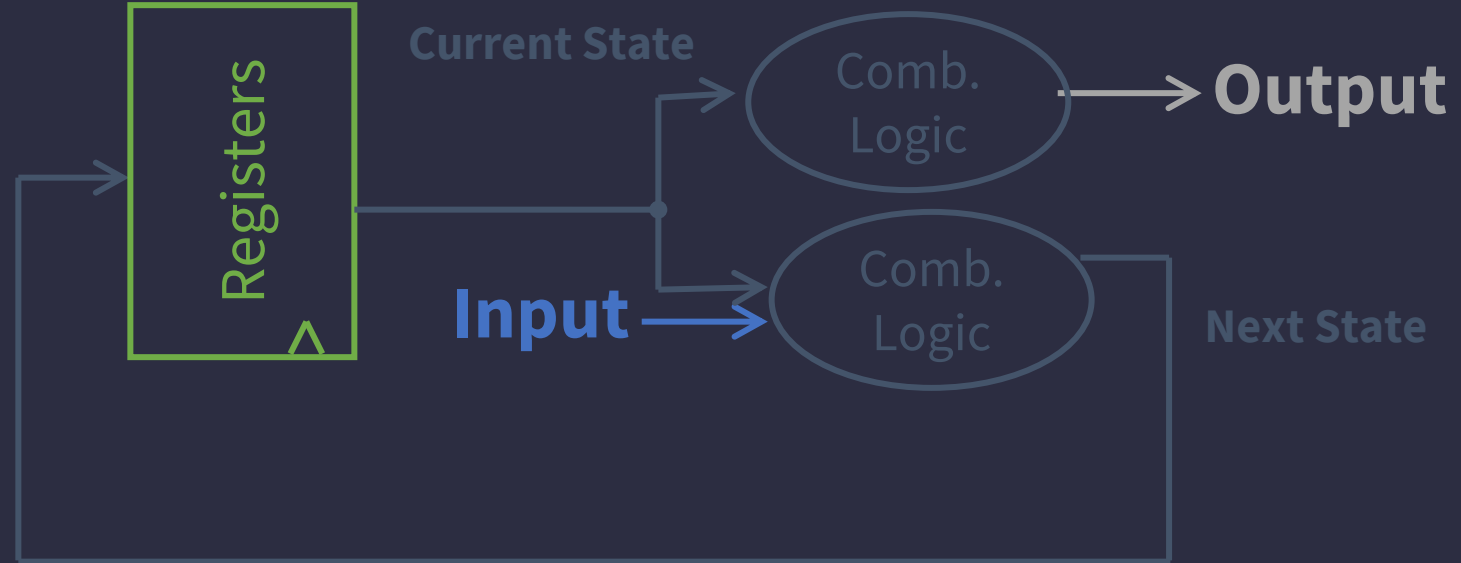

Outputs depend only on current state