

# Digital Design

## Week 11: Optimizations and Trade-offs



Fenerbahçe University




# Lesson plan


- Optimizations and Trade-offs
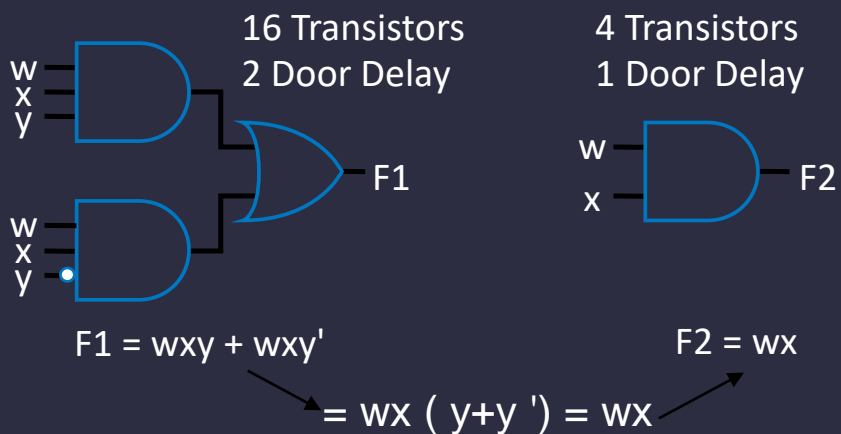
# Optimizations and Trade-offs

- We know how to build digital circuits
  - How to build better circuits?
- Two major constraints
  - **Delay** ( Latency ) – Elapsed time between input to output
  - **Area** – Number of transistor





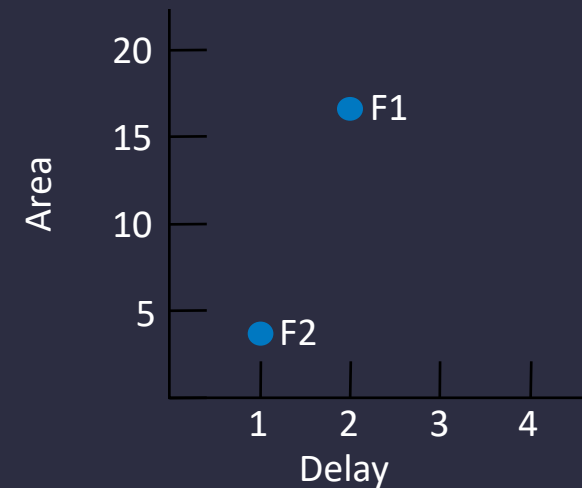
Note: Assume the gate delays are equivalent


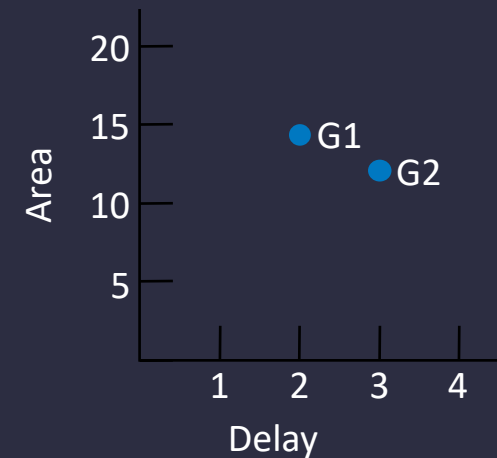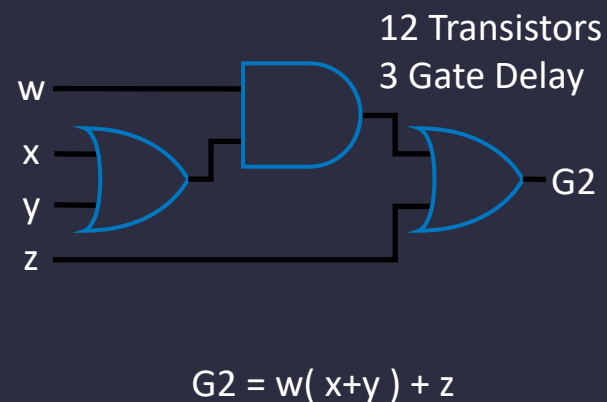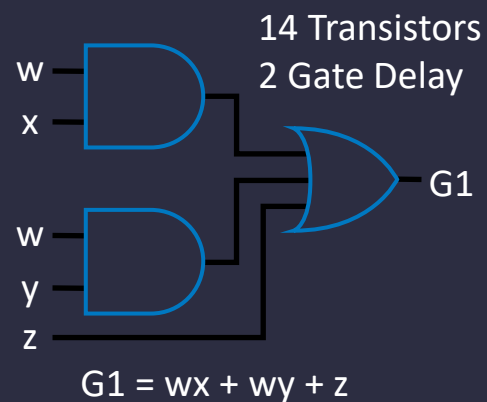
# Optimizations and Trade-offs

- Tradeoff

- When 1 criterion improves, the other criterion worsens.
- Design is made by giving priority or balancing according to a criterion.




Note: Assume the gate delays are equivalent

# Optimizations and Trade-offs


## **Optimization**

Improvement of all  
criteria

 
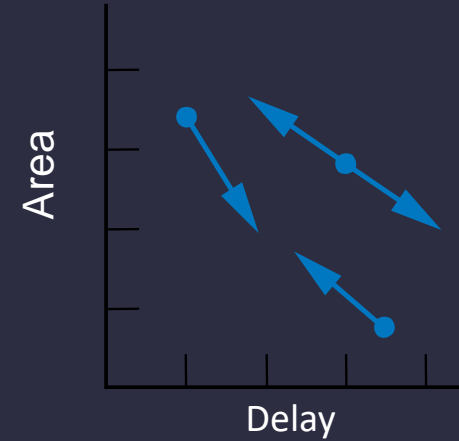
## **trade-off**

Some criteria improve  
while others worsen.



- If possible, the design is made by optimizing, otherwise making a choice according to the requirements and making tradeoffs.
  - It is designed according to the target, such as how it is not the most comfortable, the most fuel-efficient and the fastest car.

# Optimizations and Trade-offs

- Space optimization
- Express the problem as a function
  - Simplify the equation with


Sample

$$F = xyz + xyz' + x'y'z' + x'y'z$$

$$F = xy(z + z') + x'y'(z + z')$$




$$F = xy*1 + x'y'*1$$
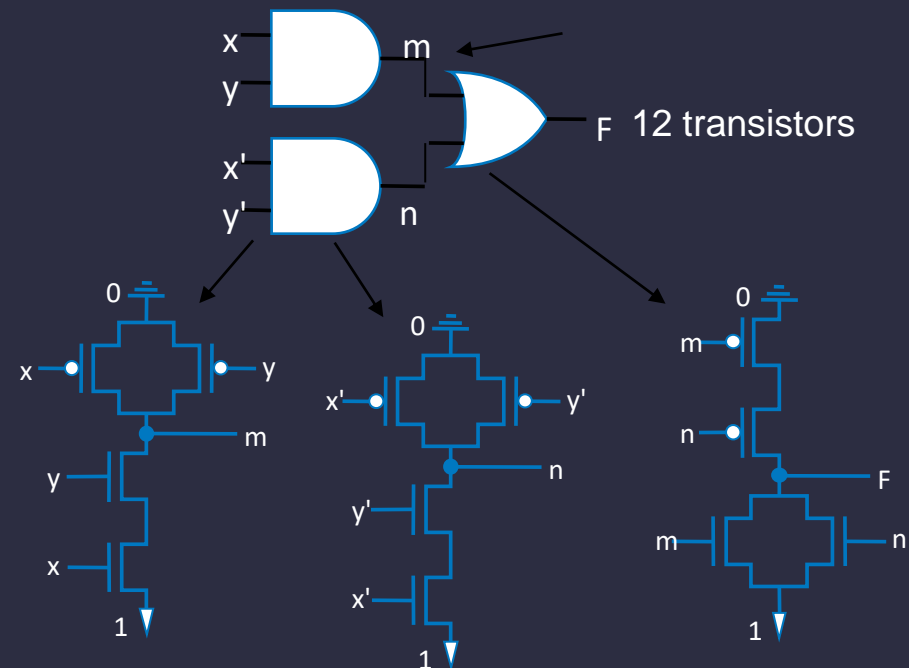
$$F = xy + x'y' \rightarrow 6 \text{ gates}$$


  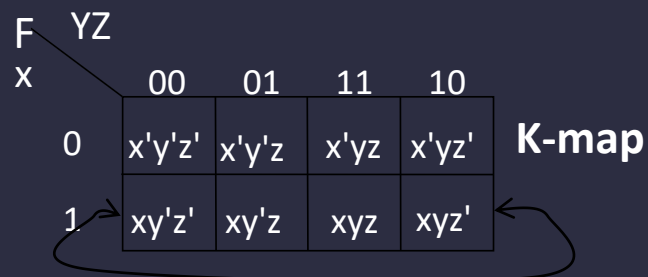
# Karnaugh Maps

- Moore 's rules, it is very possible to miss expressions that can be simplified.
- **Karnaugh Map (K-map)**
  - Provides a graphical overview for simplification
  - Simplification is done by grouping expressions.
    - Simplification is made within the rectangle groups formed by



$$F = x'y' + xy$$

$$F = xyz + xyz' + x'y'z' + x'y'z$$

$$F = xy(z + z') + x'y'(z + z')$$

$$F = xy \cdot 1 + x'y' \cdot 1$$

$$F = xy + x'y'$$

# K-maps

- If there are 4 neighbor 1s, that value can be eliminated.
- In other words, if the output is 1 in all cases, it means that it has no effect on the output.



$$G = xy'z' + xy'z + xyz + xyz'$$

$$G = x(y'z' + y'z + yz + yz')$$

$$G = x(y'(z' + z) + y(z + z'))$$

$$G = x(y' + y)$$


$$G = x$$

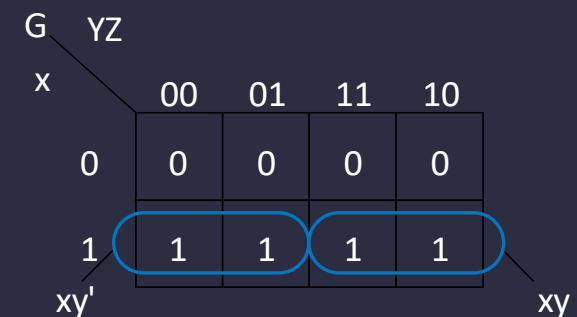 




# K-maps

- Examples

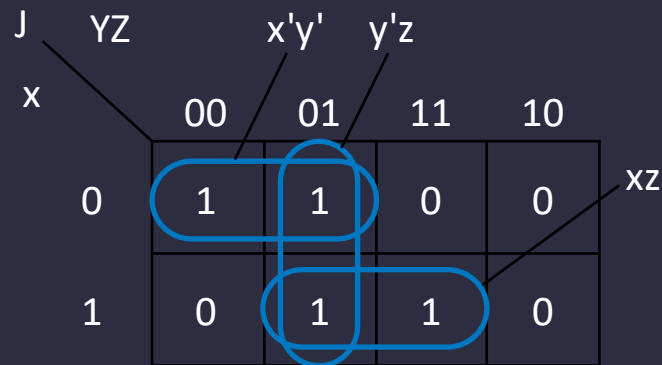


$$J = x'y' + y'z + xz$$

$$H = x'y'z + x'yz + xy'z + xyz$$

 

$$H = z$$

 

$$I = x'y'z + xy'z' + xy'z + xyz + xyz'$$



$$I = x'y'z + xy'z + xy'z' + xy'z + xyz + xyz'$$

$$I = (x'y'z + xy'z) + (xy'z' + xy'z + xyz + xyz')$$

$$I = (y'z) + (x)$$

 
 
# K-maps

- Rectangles can emerge from Kmap's boundaries from the opposite side.
- Rectangles must have multiples of 1, 2, 4, 8 ...



  
# K-maps

- can be calculated by the same principle in Kmaps with 4 values
- 5 and 6 value maps
  - However, it is very difficult to use



$$F = w'xy' + yz$$

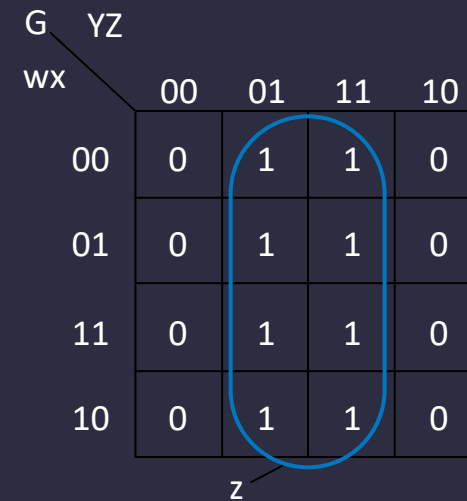


$$G = z$$

# K-maps

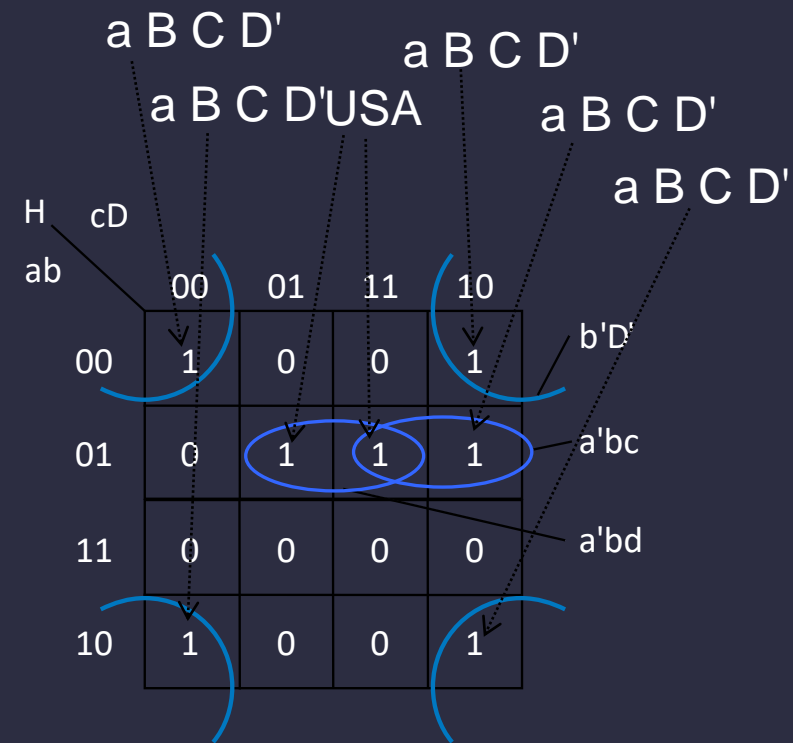- Example :

- $H = a'b'(cd' + c'd') + ab'c'd' + ab'cd' + a'bd + a'bcd'$



$$H = b'd' + a'bc + a'bd$$

# Do n't Care Entries

- Some input combinations may not be entered at all
  - $x, y,$  and  $z$  will never be 0 at the same time for the formula  $F = xy'z'$  and  $x=1, y=0, z=1$  will not be simultaneously, they can be written as negligible.
  - It can be thought of as 1 or 0 to help simplify the function
- in kmaps
  - X is written instead of ignored
  - Not to be confused with variable X

F		YZ		y'z'	
		00	01	11	10
x	0	x	0	0	0
	1	1	x	0	0

F		YZ		y'z'	
		00	01	11	10
x	0	x	0	0	0
	1	1	x	0	0

$xy'$

Brings too many terms in unnecessary use

# don't Minimization


- Example :
  - $F = a'bc' + abc' + a'b'c$
  - Ignored entries :
    - $aBC$
    - $aBC$

F		bc			
		00	01	11	10
a	0	0	1	x	1
	1	0	0	x	1

$F = a'c + b$
 
# Condition Mitigation

- Reducing the number of states without changing the behavior of
  - Fewer states will likely result in less footprint
- FSMs for



# Condition Mitigation

If the two conditions are equivalent



If they assign the same value to the output

- So  $S_0$  and  $S_2$  are throwing 0 to the output ,
- **$S_1$  and  $S_3$  throw 1 to the output**

If starting from equivalent states and producing the same outputs when the same inputs come,

- for example  $x = 1, 1, 0, 0, \dots$ 
  - **$S_1$  start** ,  $y = 1, 1, 0, 0, \dots$
  - **$S_3$  initial** ,  $y = 1, 1, 0, 0, \dots$

Statuses can be used in common.

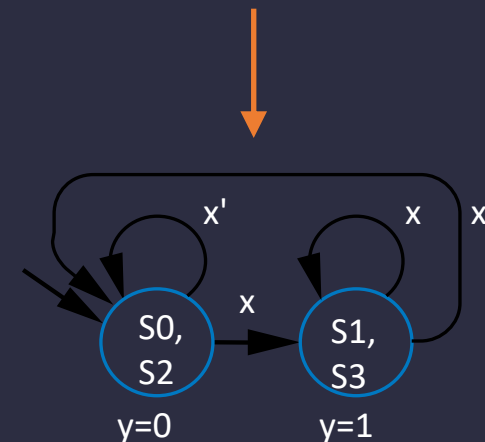 



# Pipelining

**Pipelining:** It is a structure that divides a job into stages, where the stages feed data to each other and can work in parallel.

Sample;

- You are washing the dishes, your friend is setting up.
  - 1 plate washed
  - While 1 plate is dried , *2 plates are washed*
  - While 2 dishes are being dried , 3 dishes are being washed...
  - You don't wait for your friend to finish drying the plate.

Time  
→

without

W1 D1 W2 D2 W3 D3

with


W1 W2 W3

“ Stage 1”

D1 D2 D3

“ Stage 2”


# Pipelining Example

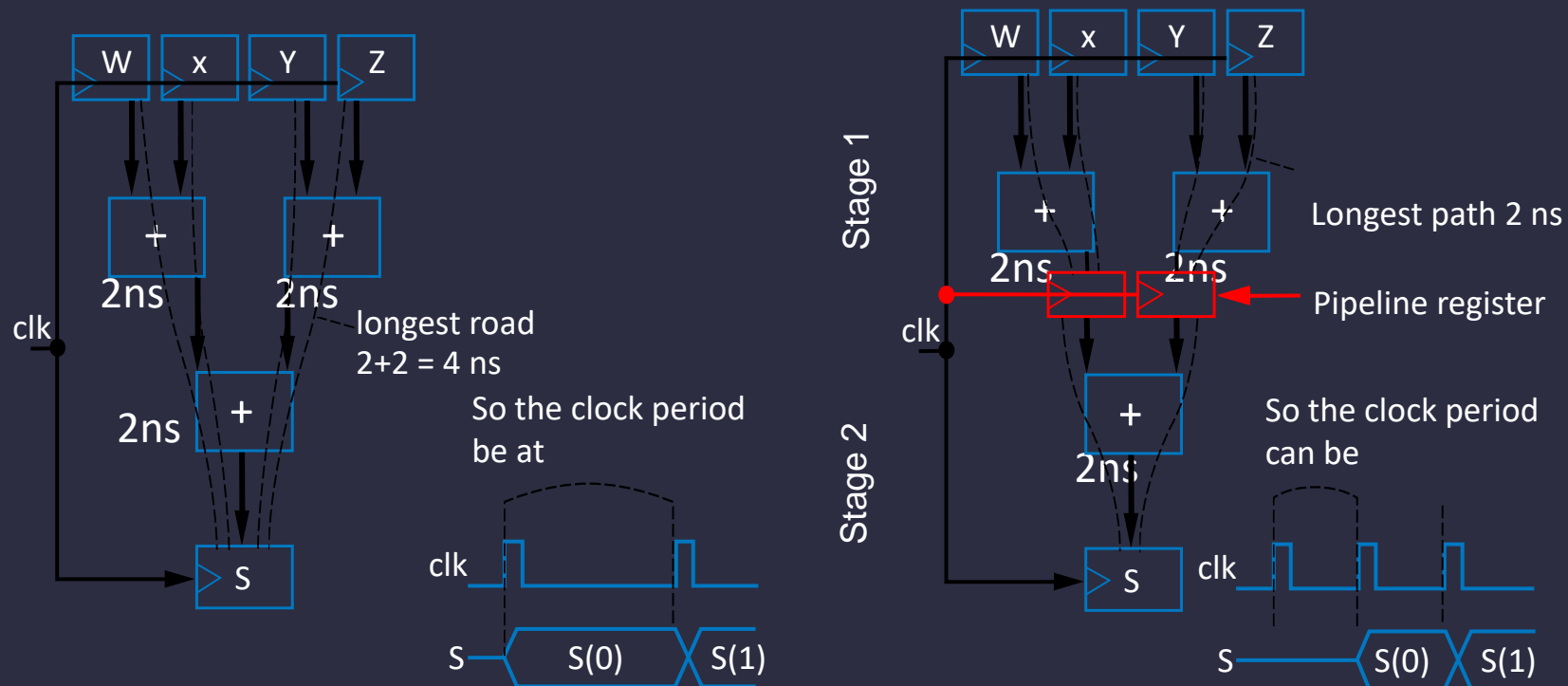

- $S = W+X+Y+Z$
- The left-hand circuit can receive inputs as fast as 4 ns .
- The circuit on the right can receive input in 2 ns as the fastest . Speed doubled.

 
# Algorithm Selection

- The chosen algorithm has great influence
- Example : Searching for an element in a 256-address memory
  - Algorithm 1: “ Linear search ”
    - Each element is checked individually M[0] , M[1], M[2], ...
    - Worst case 256 attempts
  - Algorithm 2: “ Binary search ”
    - Only takes 8 worst tries


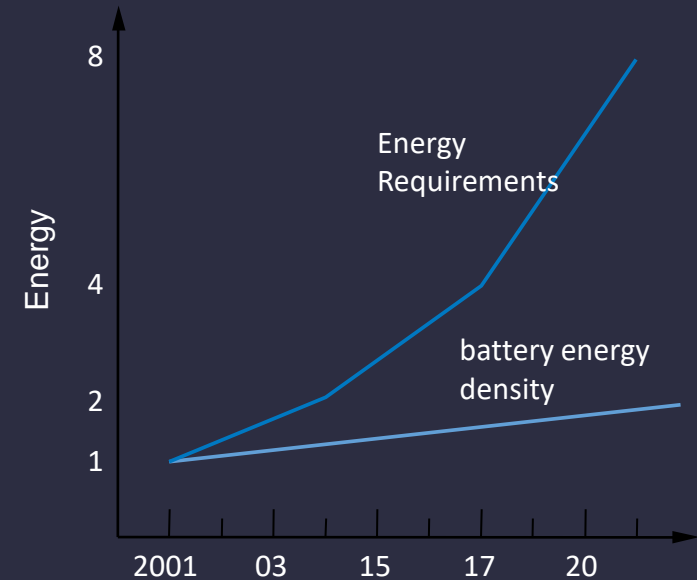
# Power Optimization



- **Strength** Another important design criterion is
  - Watts (Volts \* Current)
- It is an important parameter as space consumption.
  - Especially important on mobile devices
  - With the developments in batteries, the required energy need does not increase at the same level.
  - Therefore, more power efficient designs are required.
  - CMOS technology, switching from 0 to 1 (Dynamic Power, Dynamic power )
    - $P = k * CV^2 f$ 
      - k: constant ;
      - C: capacitance of cables ;
      - V: voltage ;
      - f: Switching frequency





# Power Optimization (Clock Gating )

- Exchange of signals within the chip increases power consumption
- The solution to this is to stop unused registers in certain situations.
  - Ande gate

# Power Optimization (Clock Gating)

 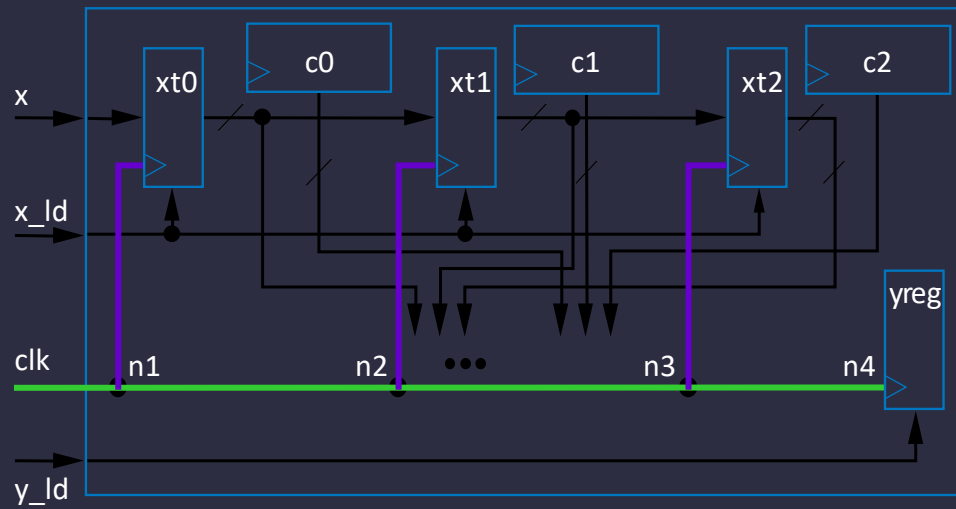

*You heavily have a*

 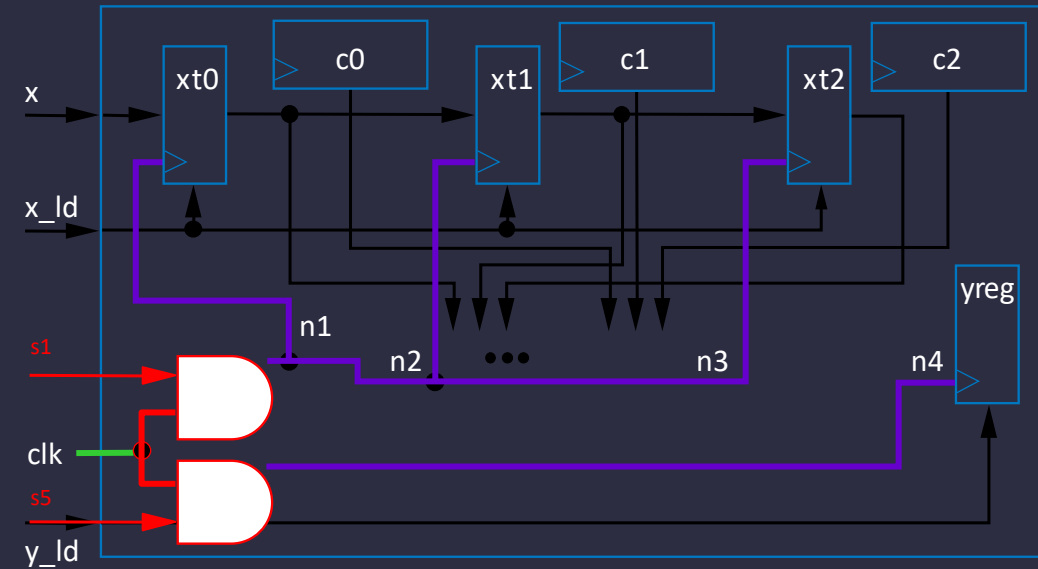

*switching is reduced*

## Power Optimization (Low Power Gates)

- Low Power Gates
  - There can be multiple versions of doors performing the same task.
    - fast/high power consumption slow/low power consumption
  - critical path as slow/low power consumption, the power can be reduced without affecting the total delay.

