

Digital System

Week 2: Number Systems and Boolean Algebra Part III



Fenerbahçe University

Course 3 Content

- Transistors
- Logic Gates
 - Not
 - Or, Nor
 - And, Nand
 - De Morgan's Law
 - Multi-input Logic Gates


Design of Processor Blocks with

- Number of Transistors in Processors


- Intel 4004 (1971): 2250
- Intel 8088 (1979): 29k
- AMD K6 (1997): 7.5 million
- Intel Pentium 4 (2006): 184 Million
- Intel I7 Haswell -E (2014): 2.6 Billion
- AMD Epyc Rome (2019): 32 Billion

Design of Processor Blocks with

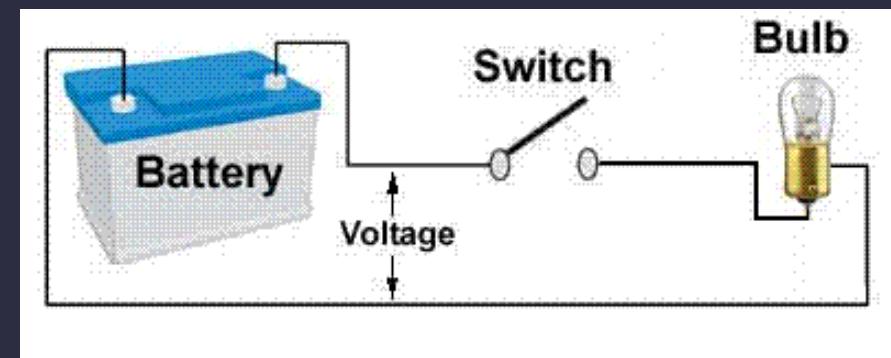- Transistors work like switches.
- They form the control mechanisms in the circuit.
- Multiple transistors come together to form logic circuits.
 - And , Or , Not
- With the combination of logic gates
 - Structures such as adders, multipliers can be created.
- A processor can be made with adder, multiplier and store structures.





Simple Switch Circuit

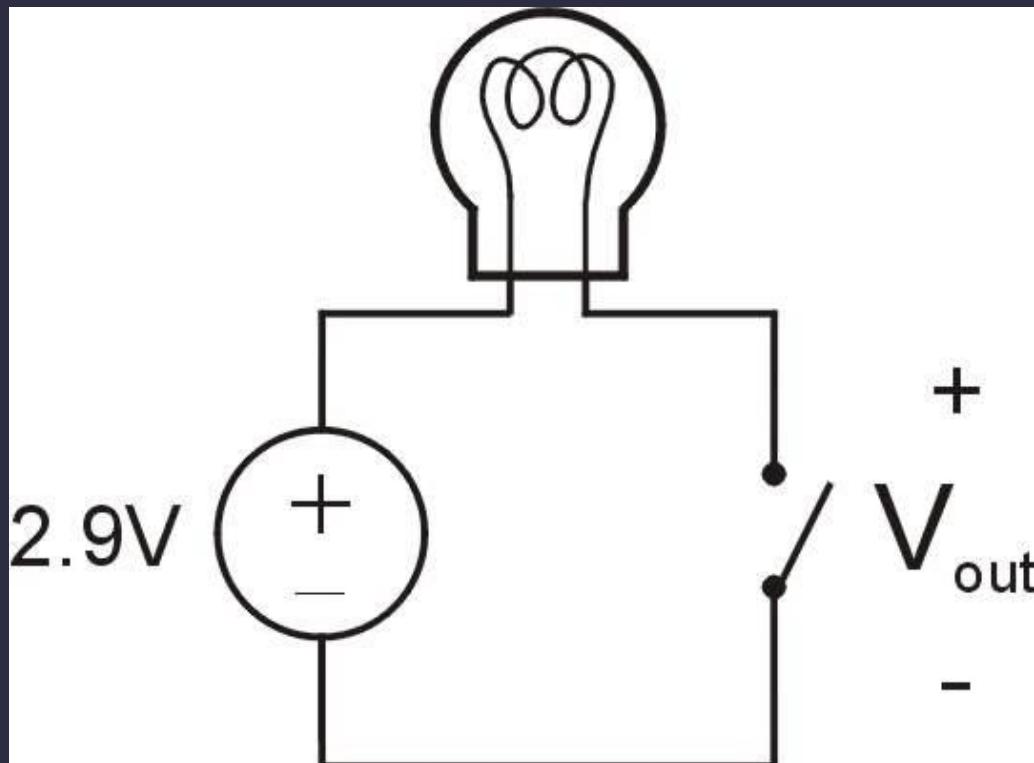

- Switch On:
 - There is no current flow.
 - lamp off
 - $V_{out} +2.9V$ (There is potential difference)
- Switch Off :
 - There is current flow in the circuit.
 - lamp on
 - $V_{out} 0V$ (No potential difference)

Vacuum Tubes

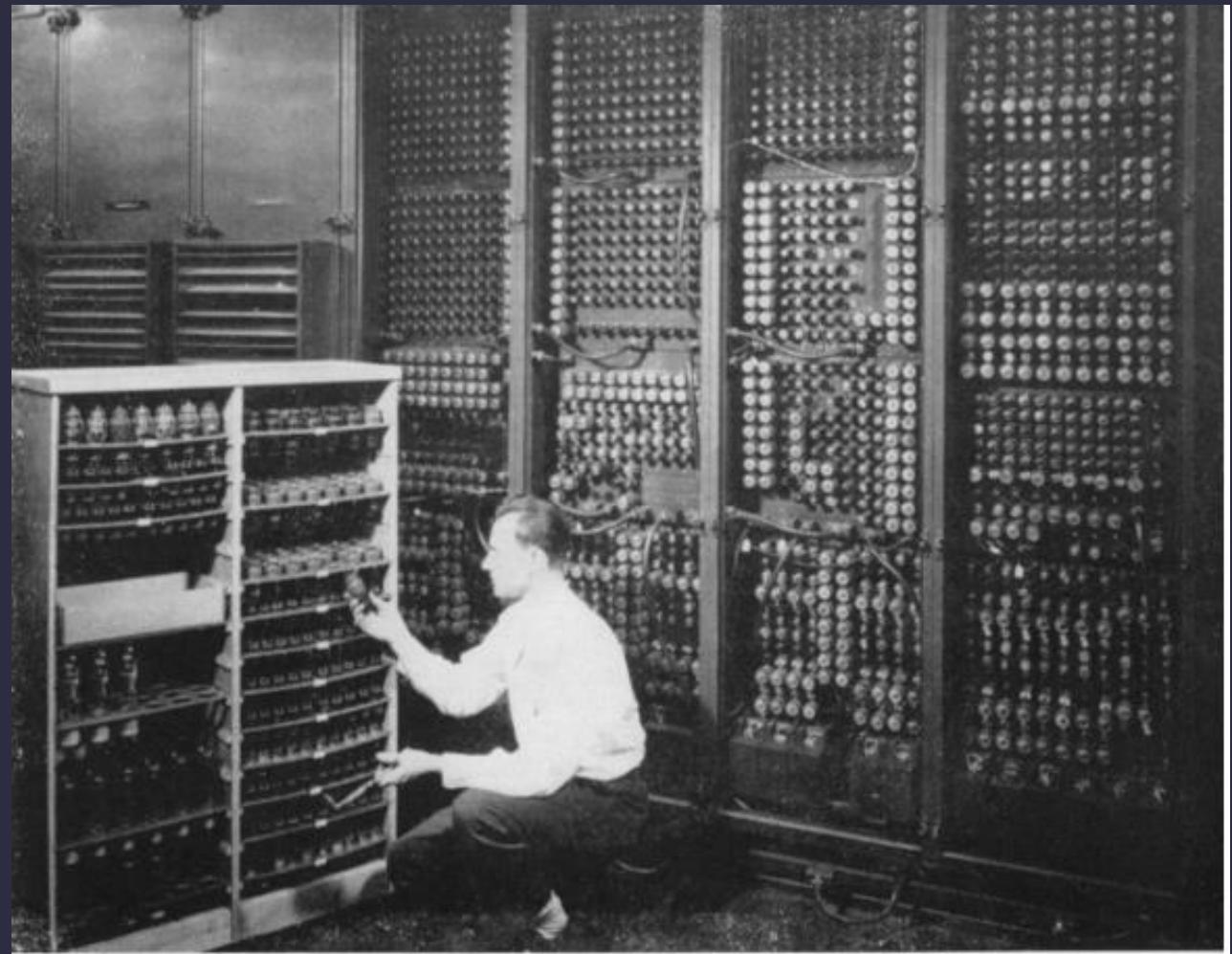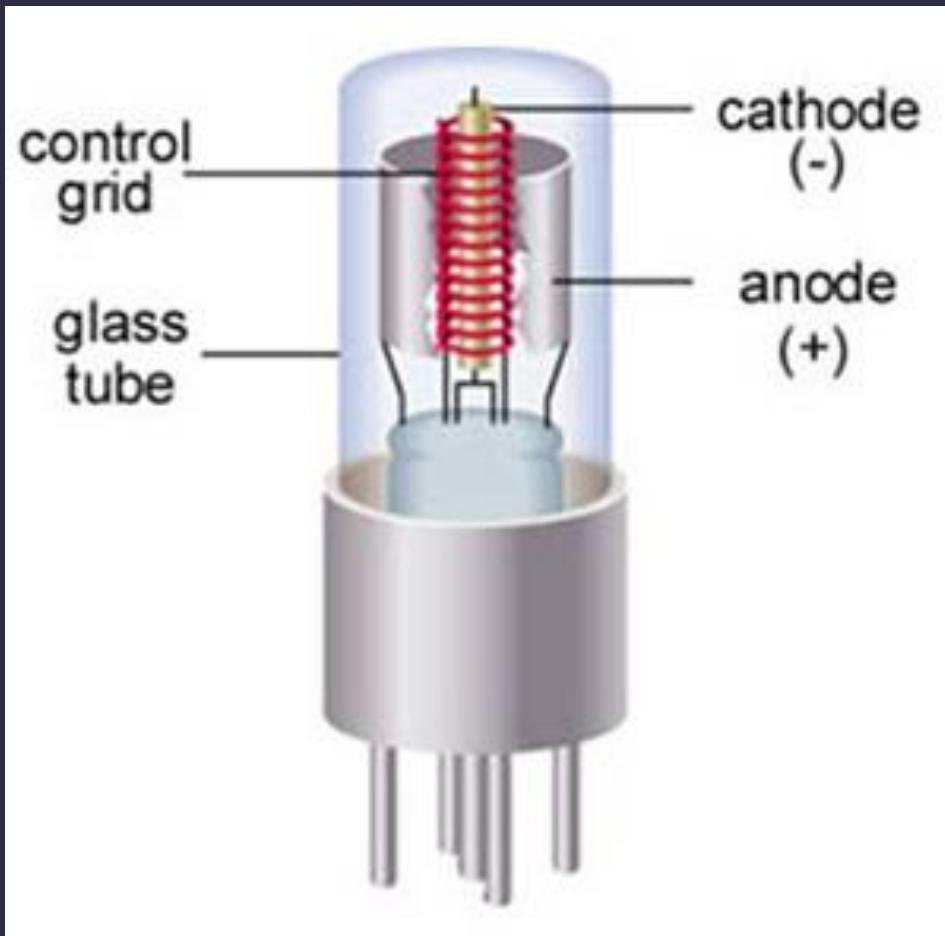


Transistors




Silicon Element

Transistors

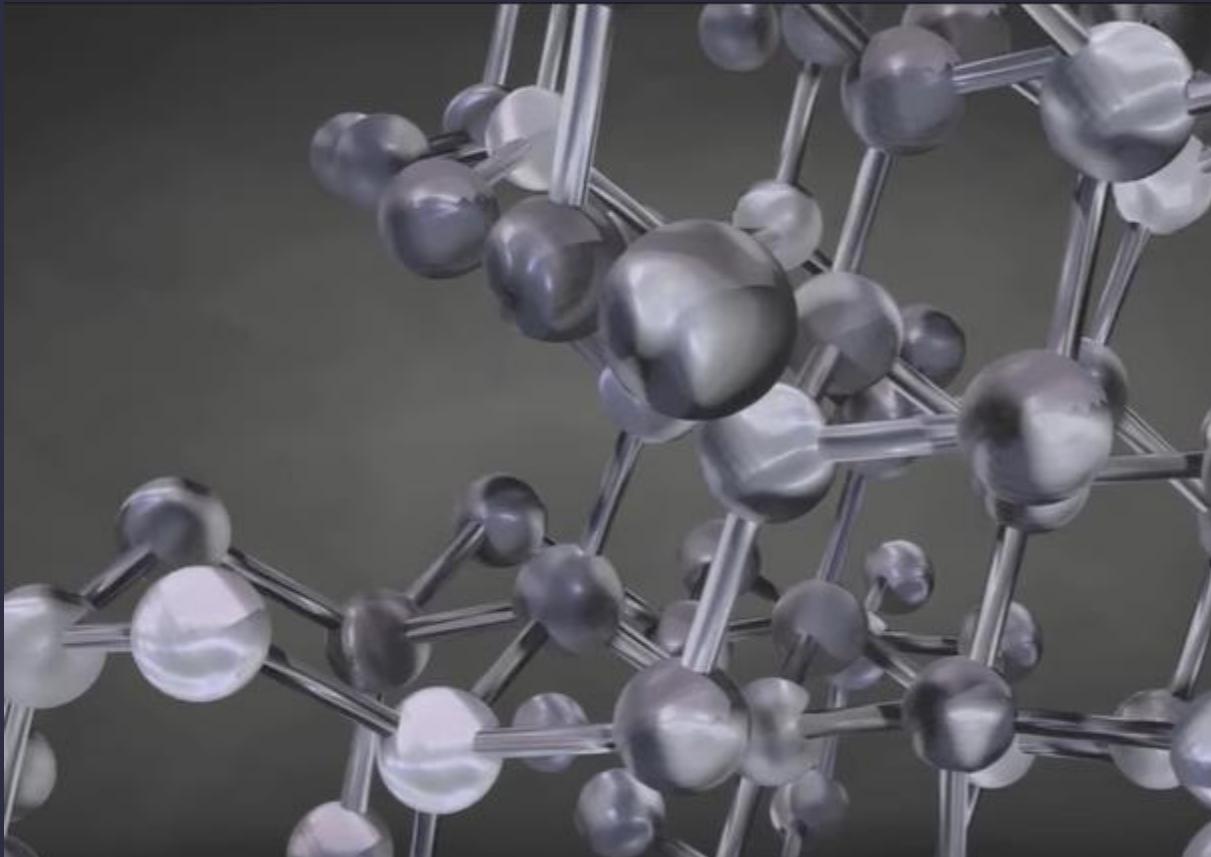


Each silicon atom forms a covalent bond with 4 surrounding silicon atoms.



Transistors

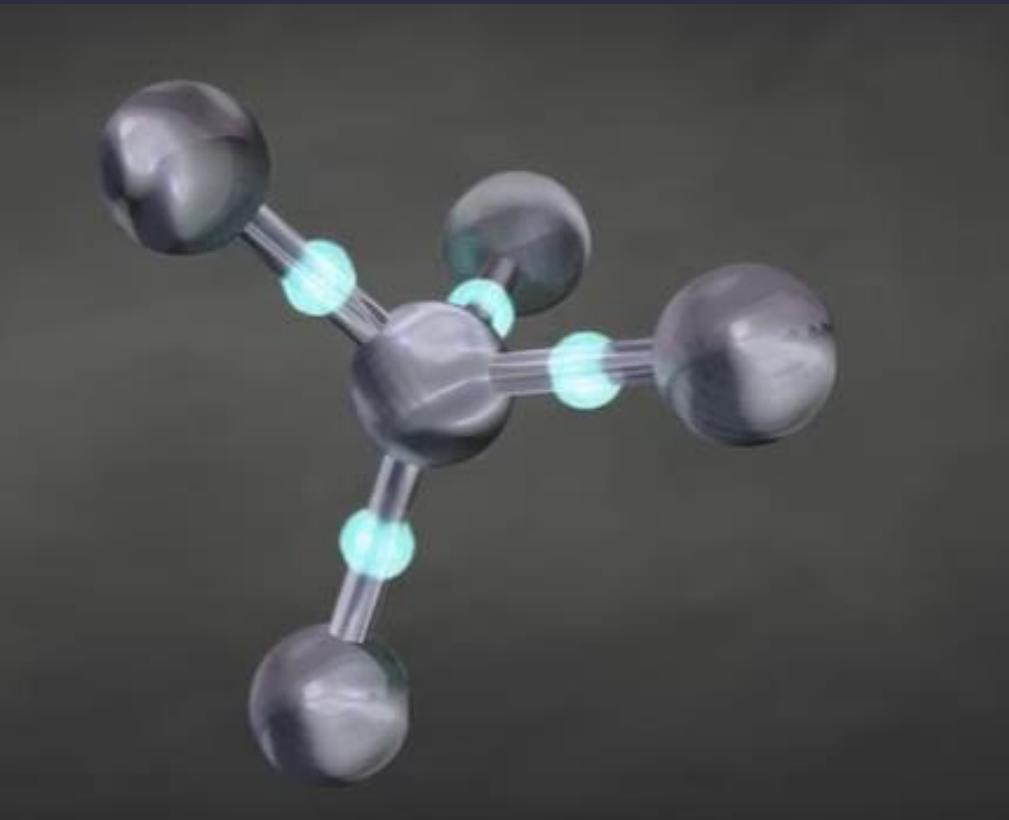

4 electrons

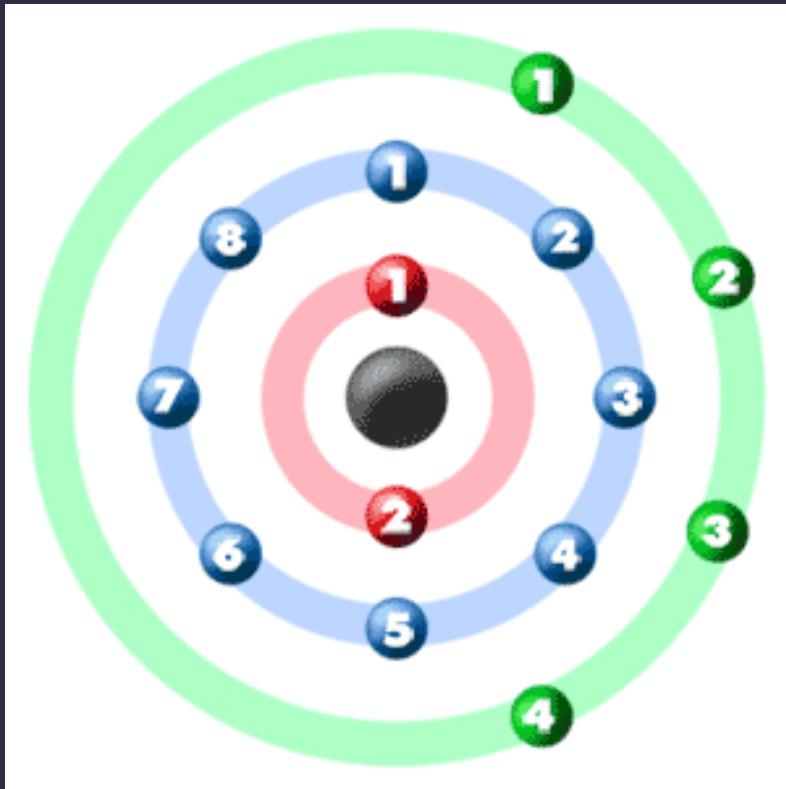


Transistors

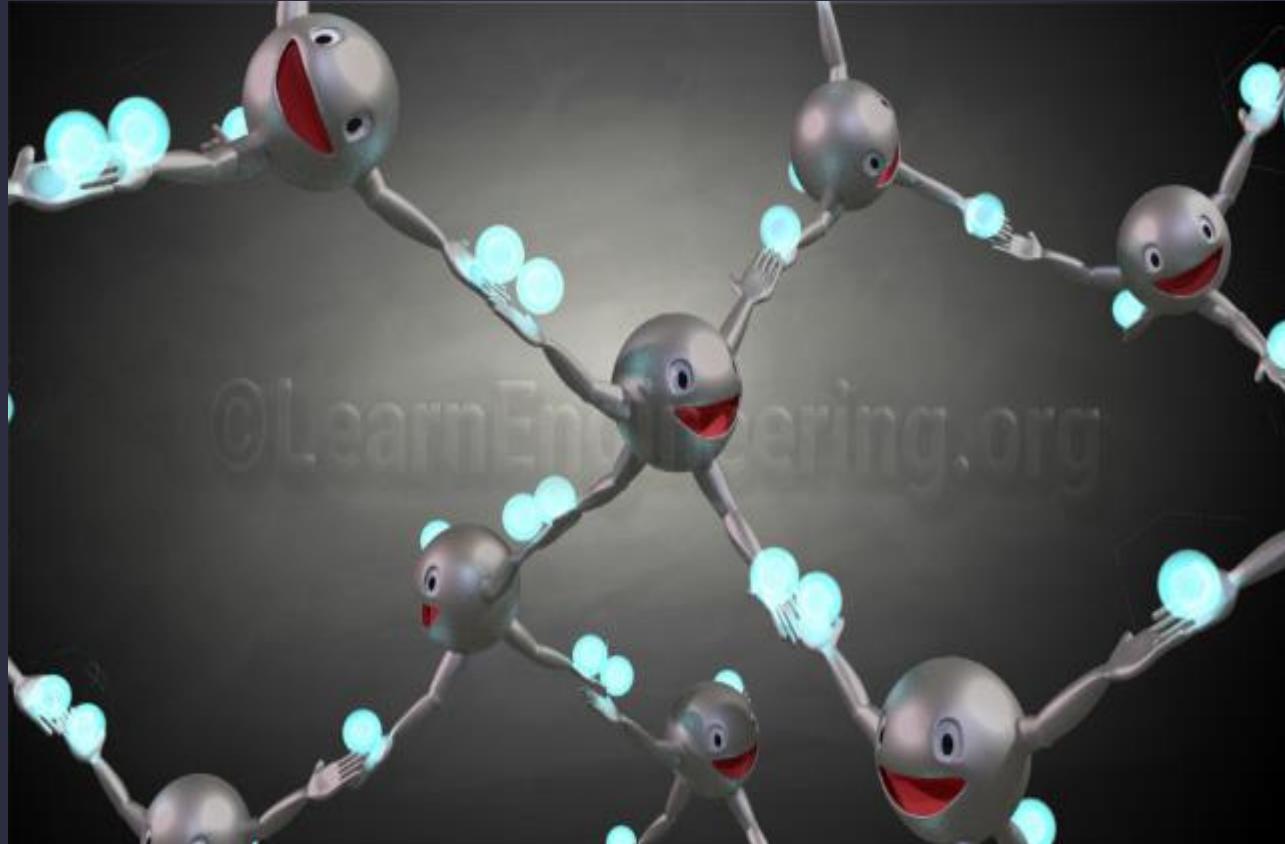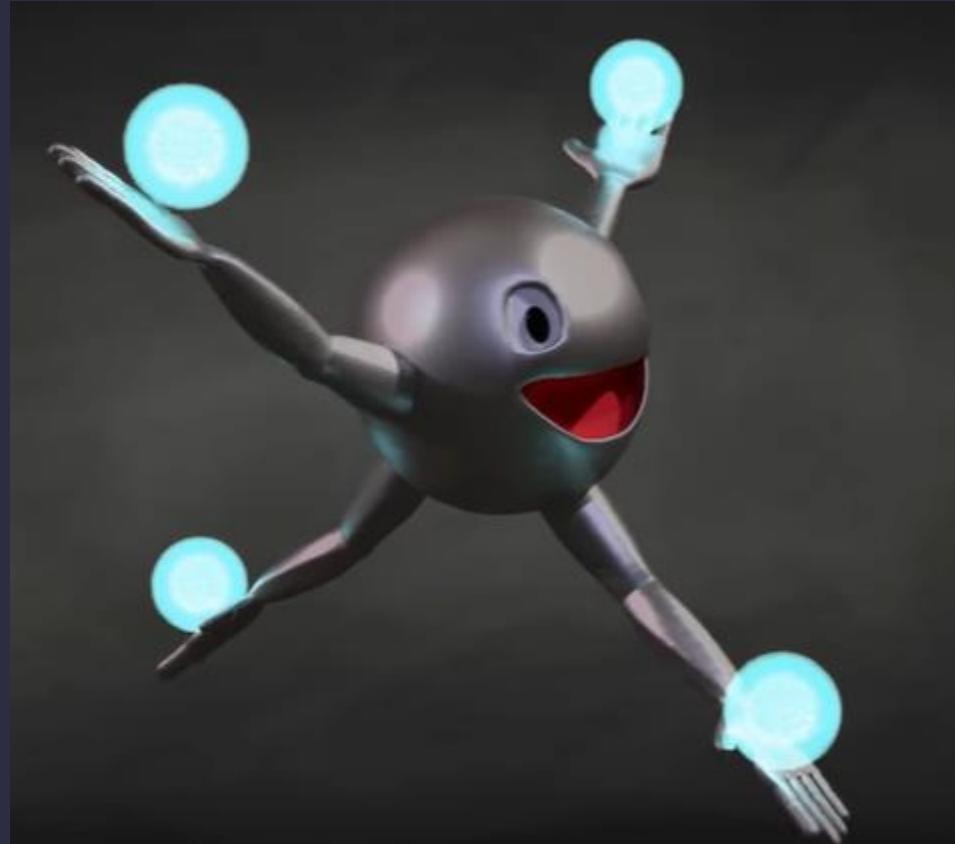


4 electrons in its last orbital .
It is semiconductor but has low conductivity.

Transistor Doping Process

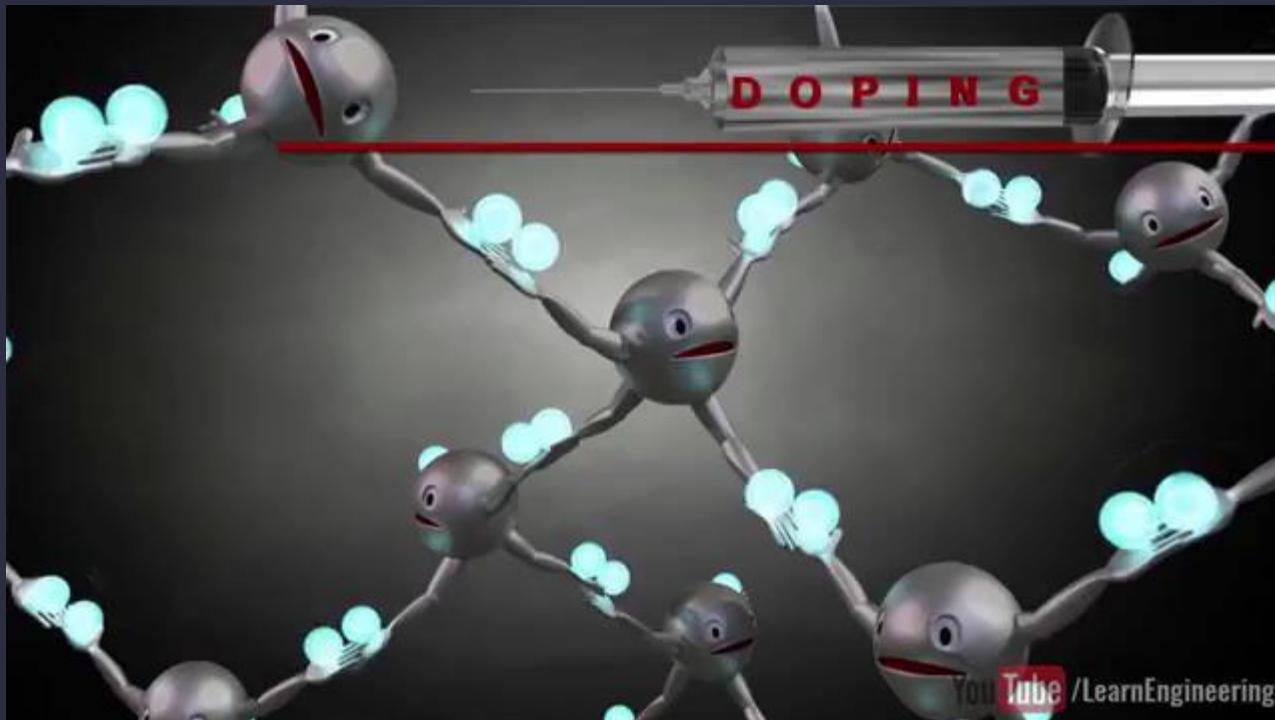


"Doping" technique, which is used to increase the conductivity of semiconductors, is applied.

N Type

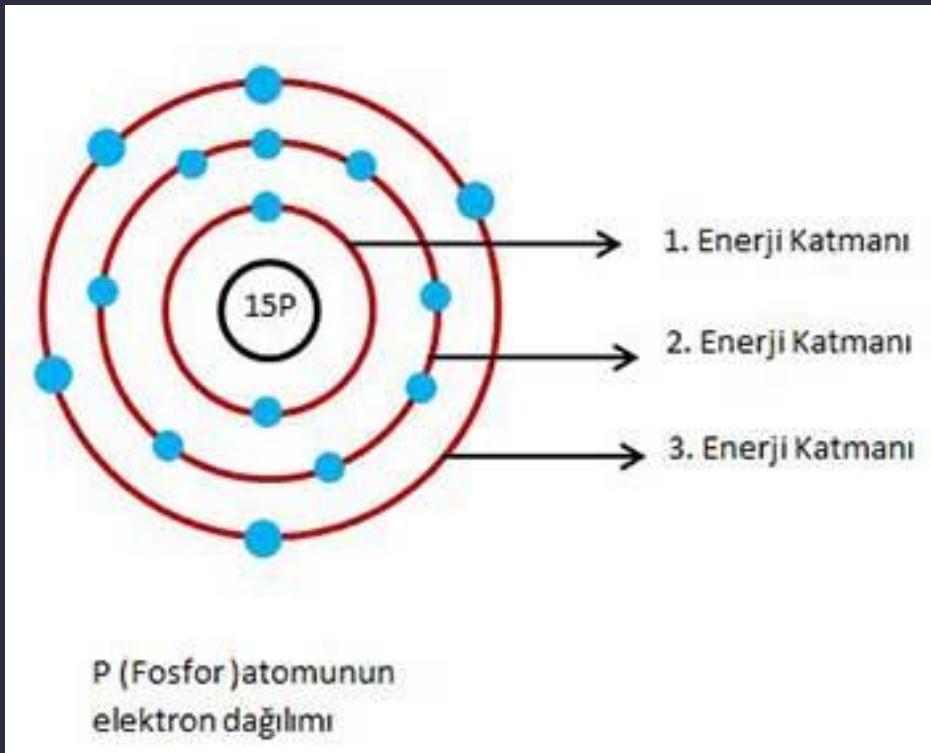

Phosphorus Atom

Transistor Doping Process

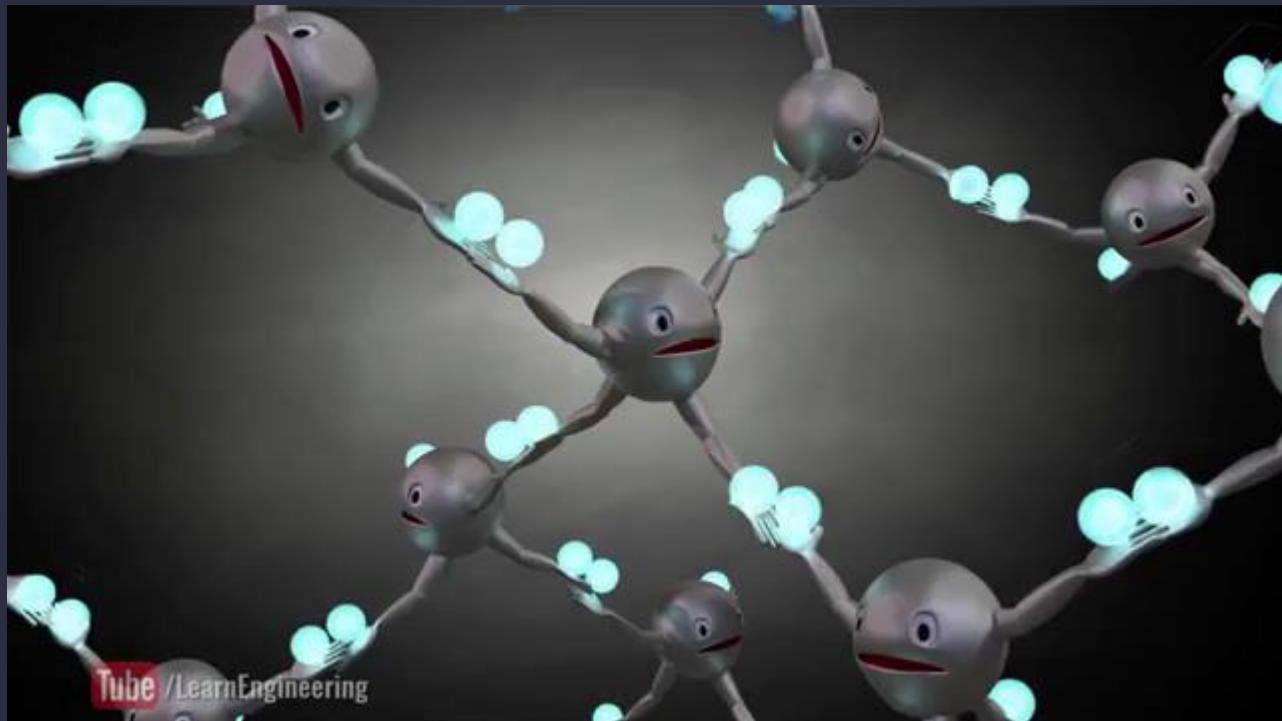


"Doping" technique, which is used to increase the conductivity of semiconductors, is applied.

P Type

Boron Atom

Transistor Doping Process

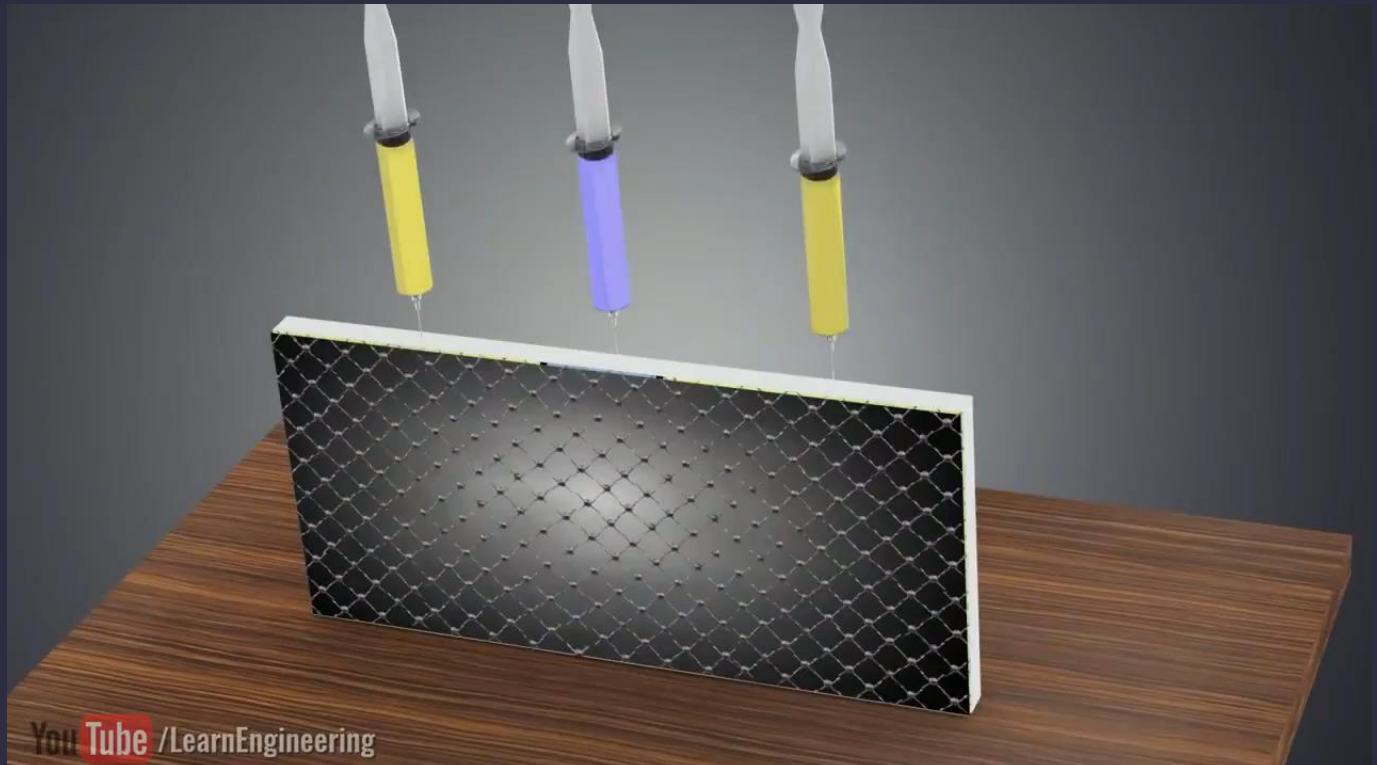


Structure of Transistor
NPN Transistor

Transistor Doping Process




Diode Structure

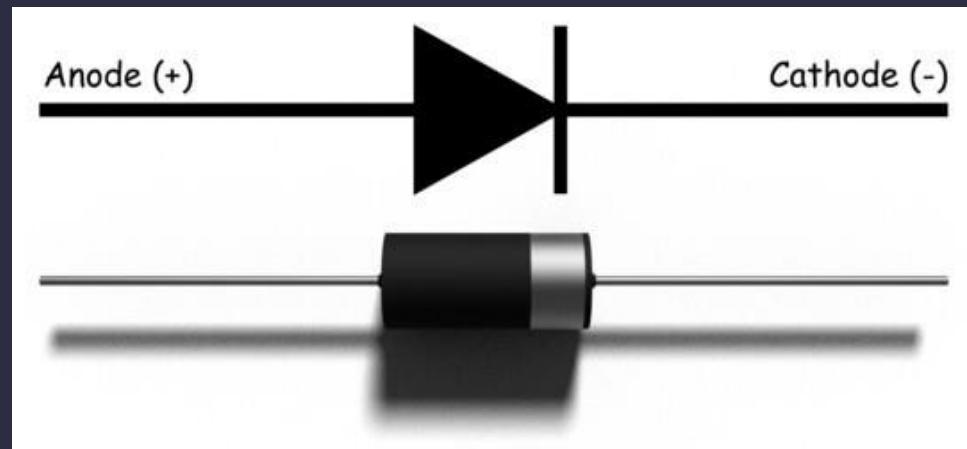

Diode

Transistor Doping Process

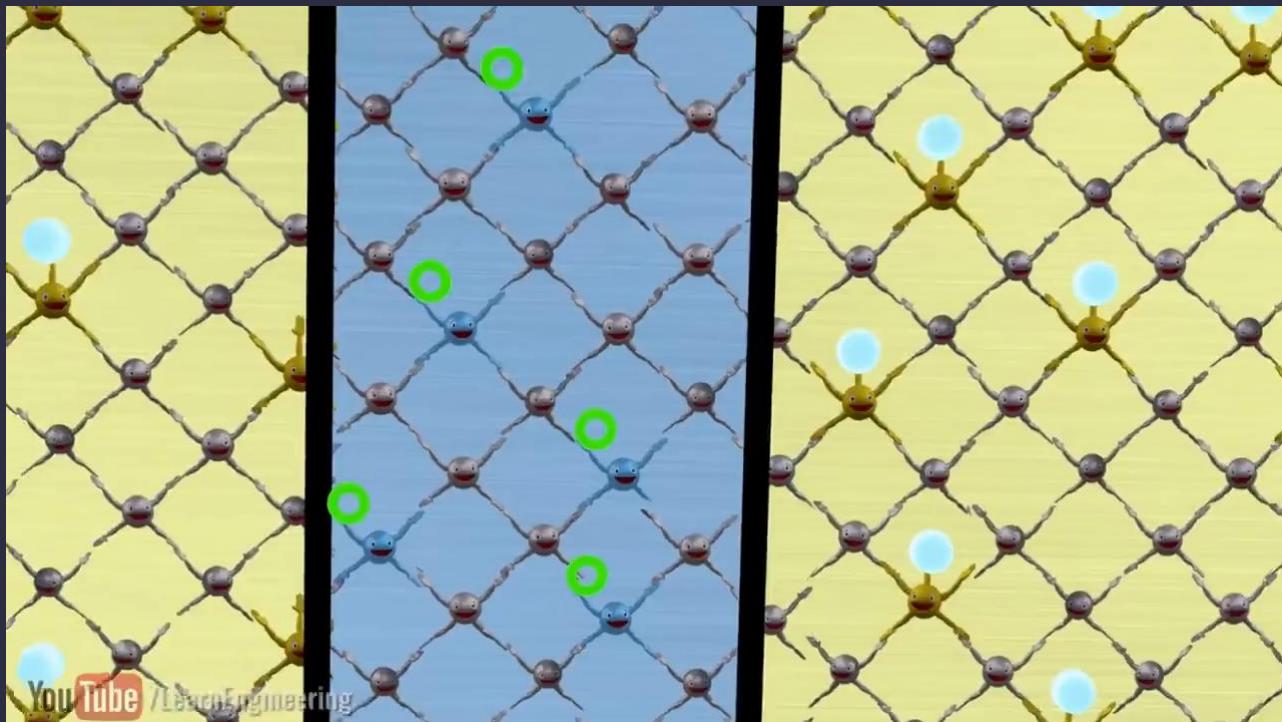


NPN Transistor

Electrons cannot advance unless voltage is applied to the base input.




NPN Transistor

Transistor Doping Process

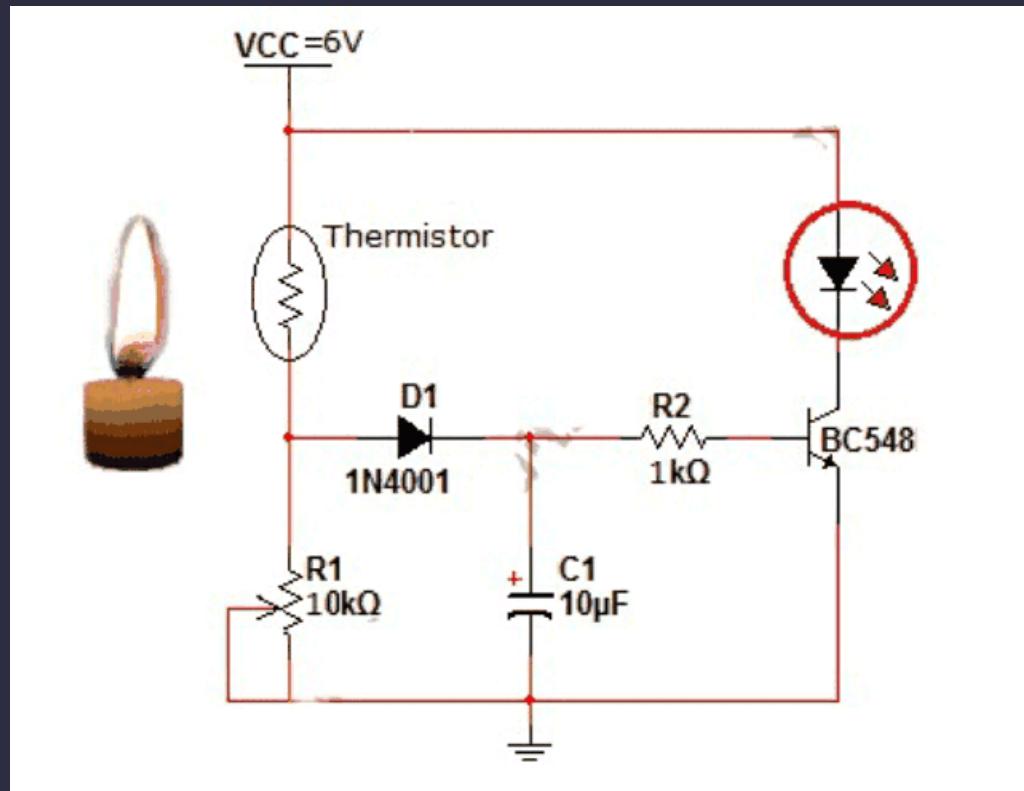

A Simple Fire Alarm Circuit with a
Transistor

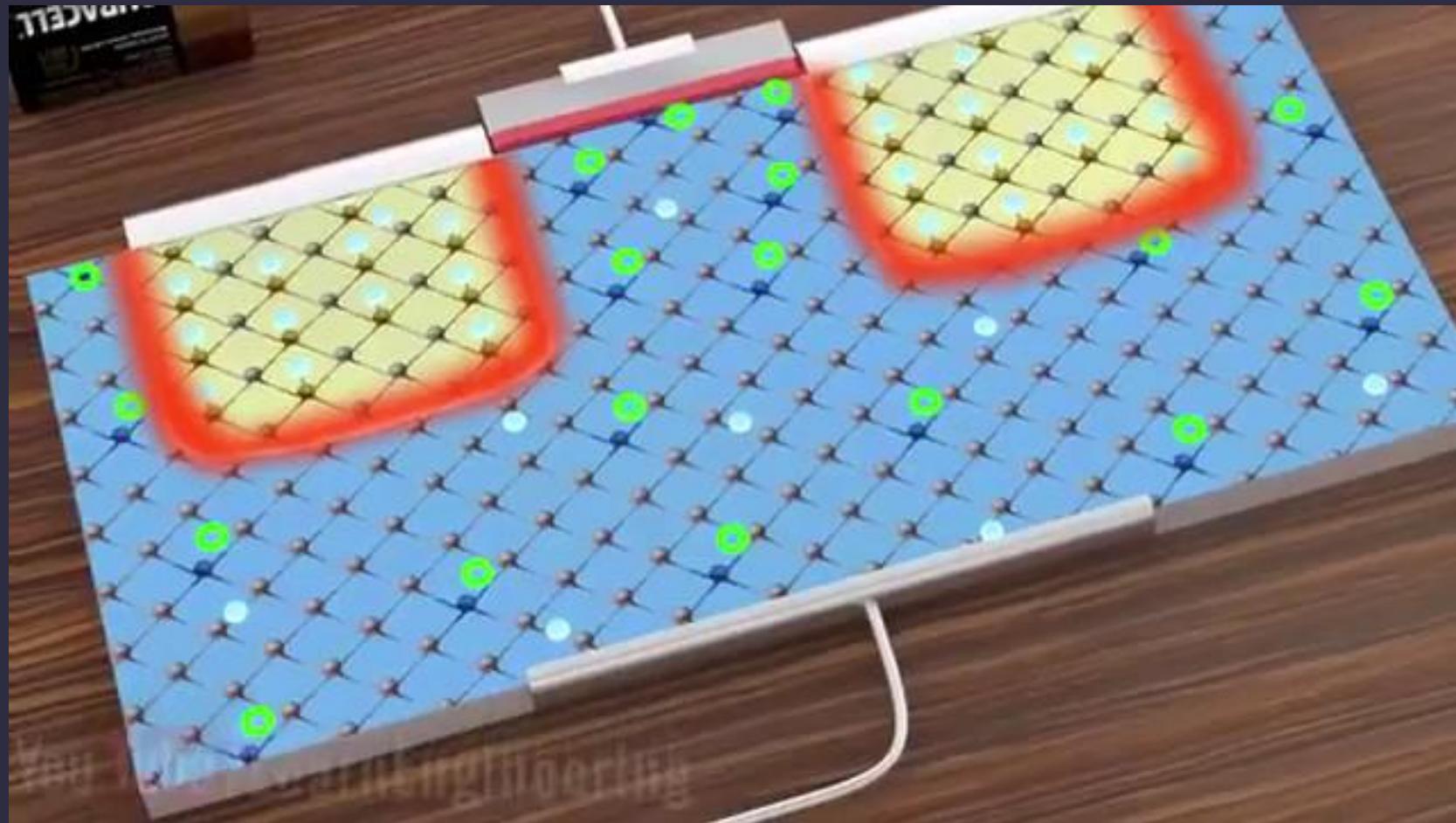
MOS Transistors , Also known as MOSFET (Metal Oxide Semi-conductor Field Effect Transistor)



MOSFETs

N Type MOS Transistors

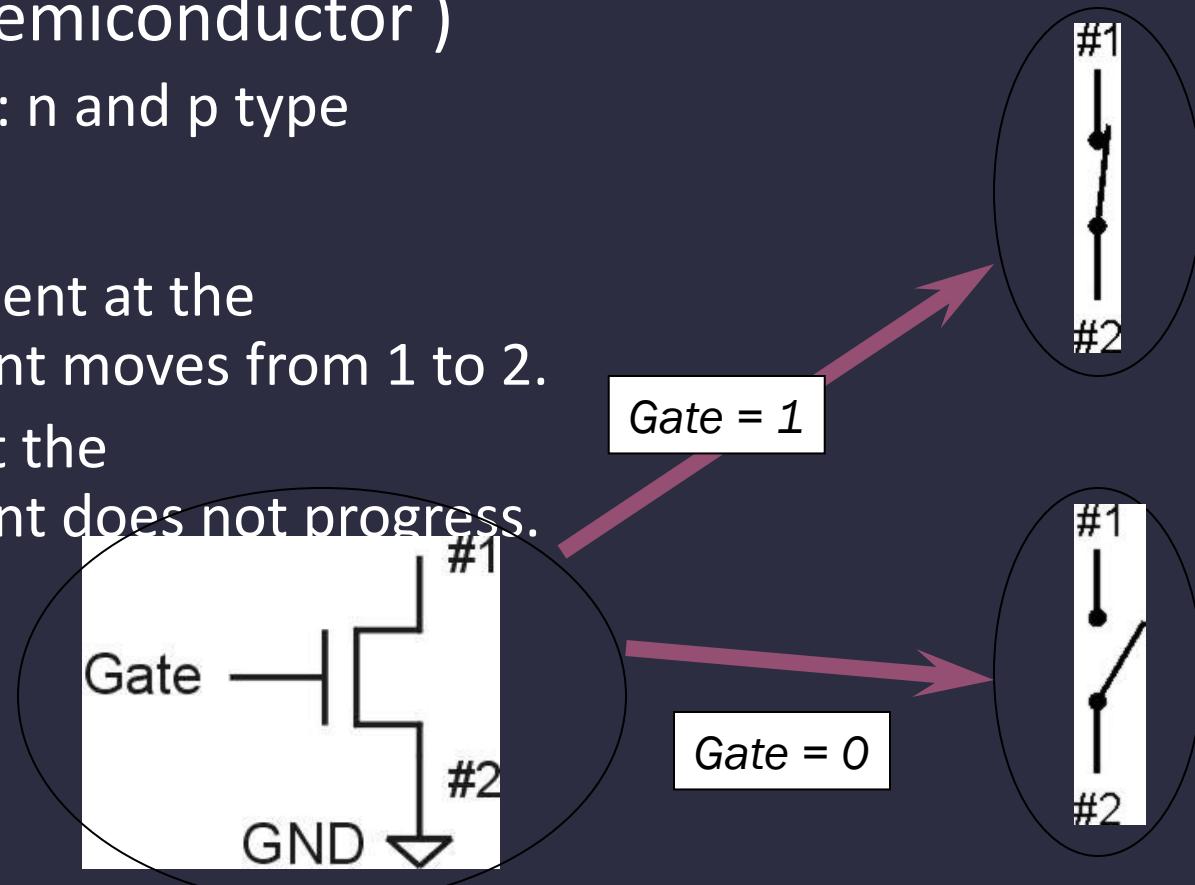
- MOS (Metal Oxide Semiconductor)
 - There are two types : n and p type
- N Type
 - When voltage is present at the gate input, the current moves from 1 to 2.
 - there is no voltage at the gate input, the current does not progress.



Terminal #2 must be connected to GND (0V).

P Type MOS Transistors

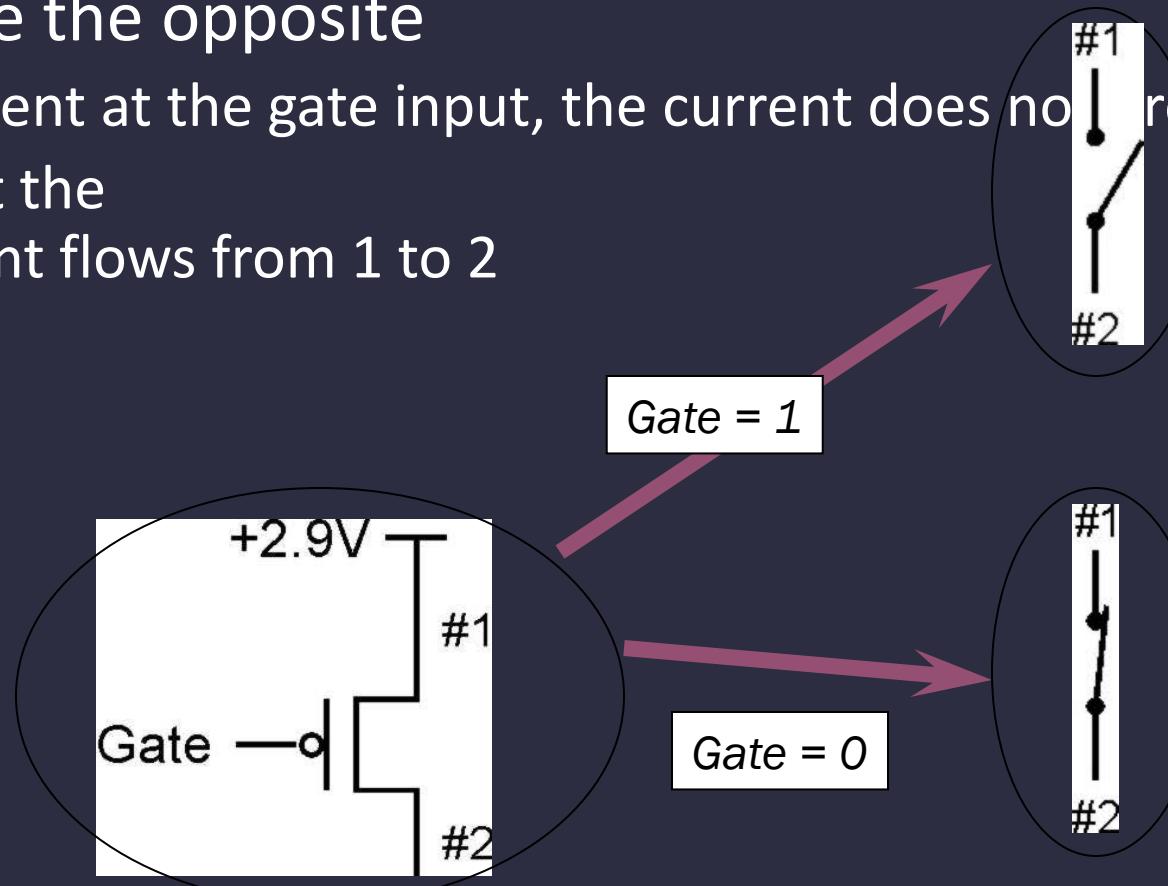- P- type transistors are the opposite
 - When voltage is present at the gate input, the current does not progress.
 - there is no voltage at the gate input, the current flows from 1 to 2



Logic Gates


- Many logic gates can be implemented with MOSFETs . Examples of these are
- Digital Symbols :



- A wide variety of voltage values are used in the electronics world.
 - Usually Yes – for 1 : +5V, +3.3V, +2.9V values
 - For None, 0V value is used.

CMOS (Complementary MOS) Circuit

- Both NMOS and PMOS transistors .



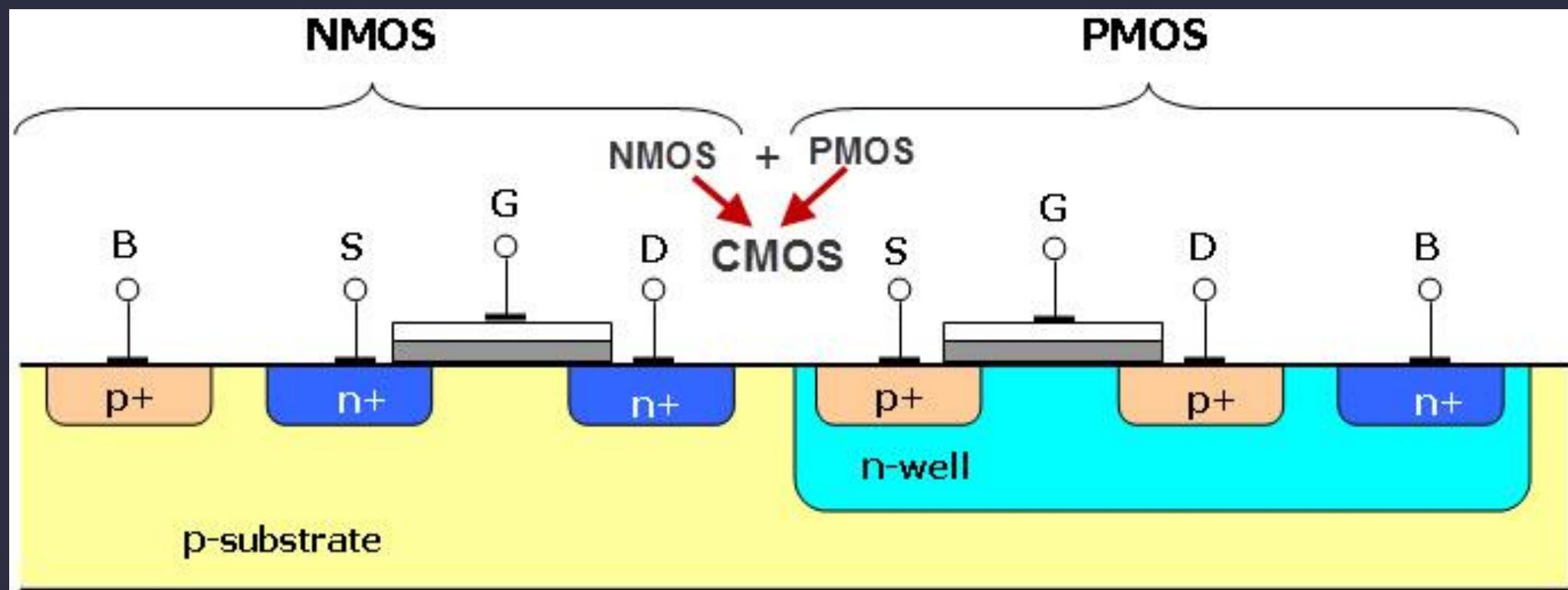


CMOS (Complementary MOS) Circuit

Has several advantages over NMOS and PMOS.



- Power consumption is low
- Circuit complexity is low
- It has high noise resistance

CMOS NOT Gate

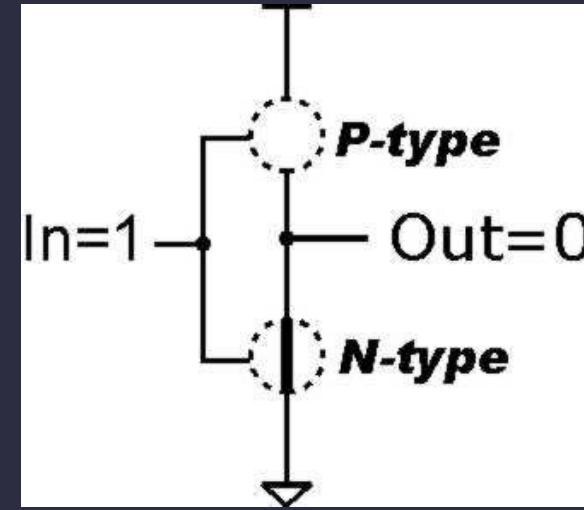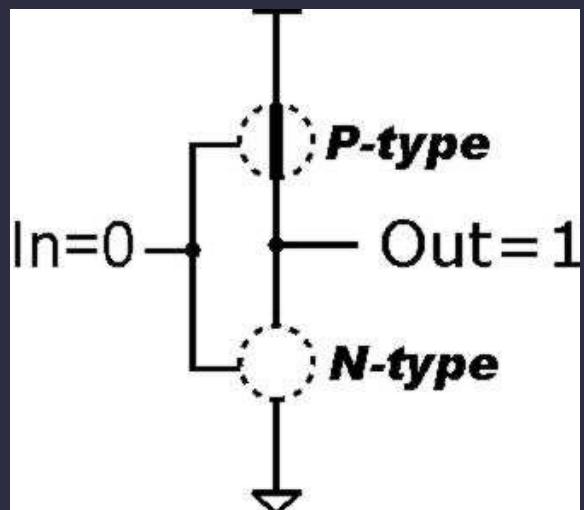
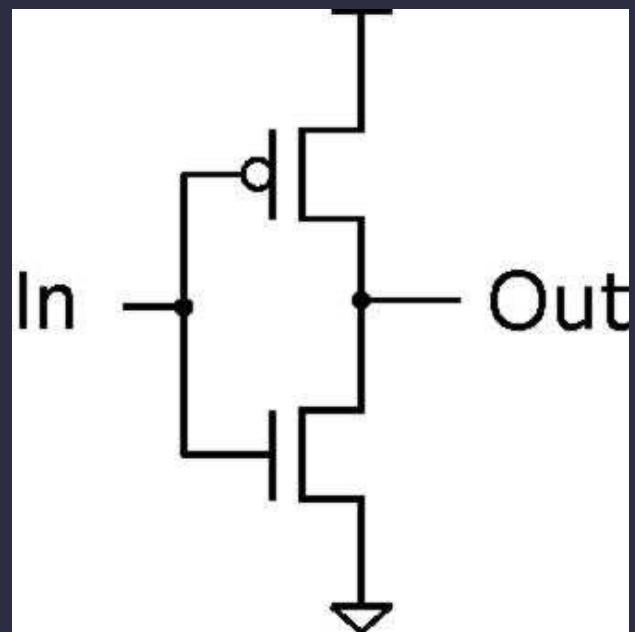


| Logic | Out | Logic | Out |
|-------|------|-------|-----|
| 0V | 2.9V | 0 | 1 |
| 2.9V | 0V | 1 | 0 |

Truth Table

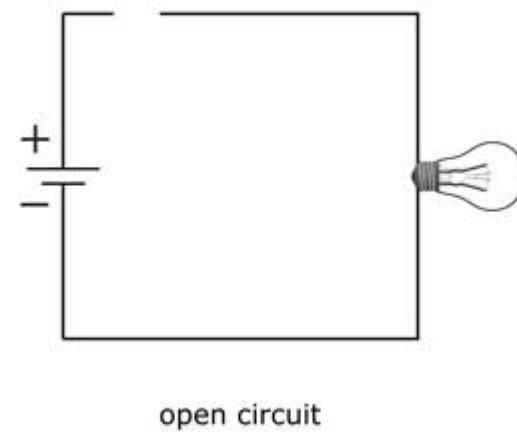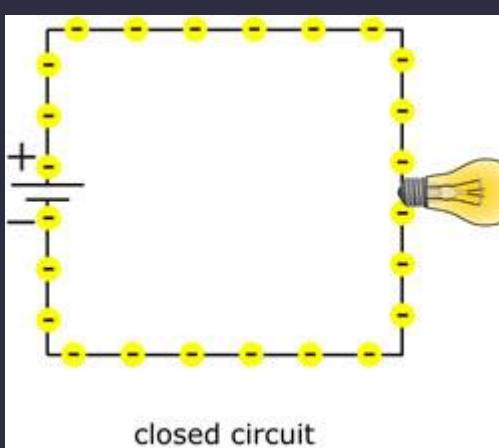


NOR gate

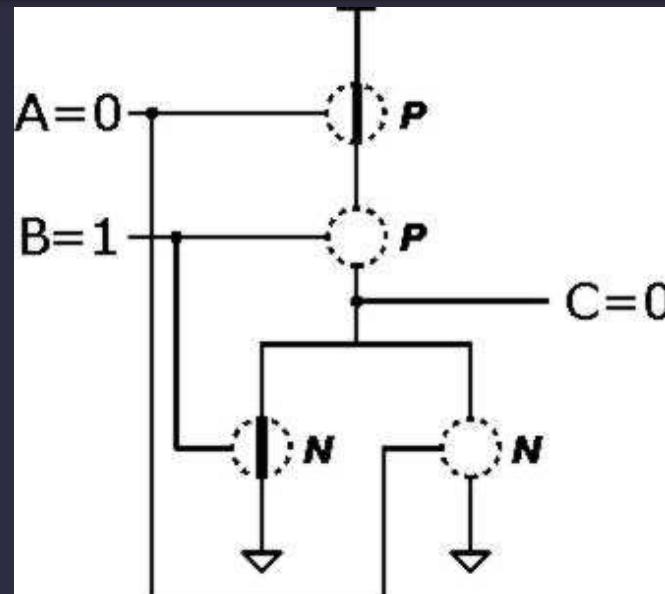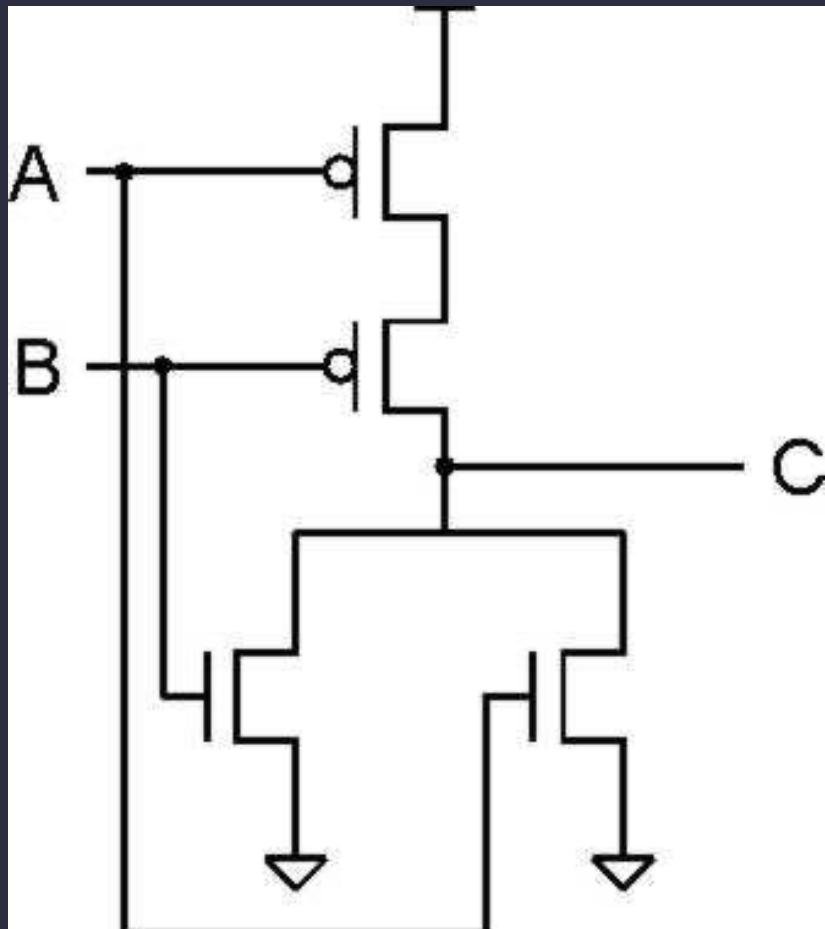

| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |



Or gate

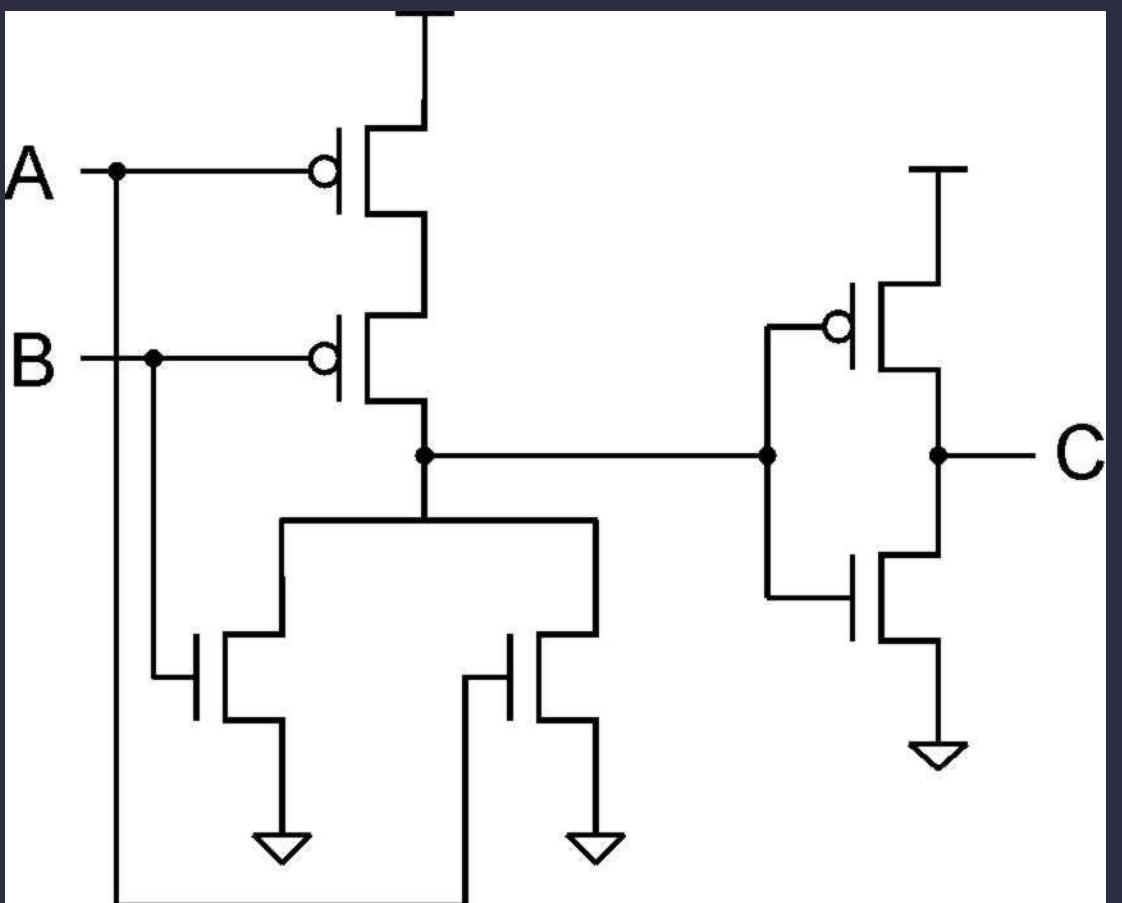

| A | B | C |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |


NOR gate but not gate added

NAND gate

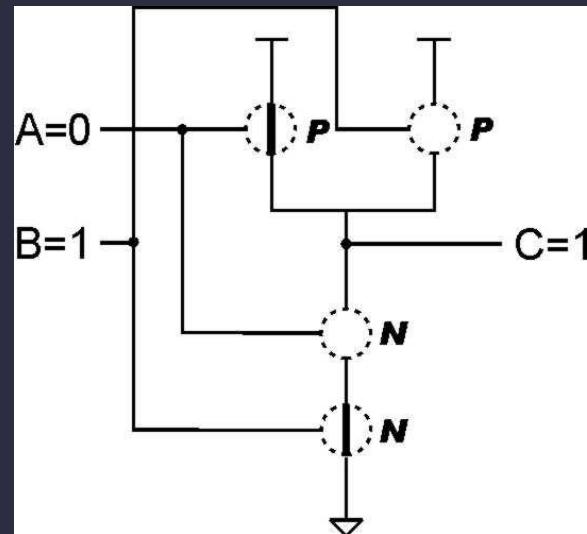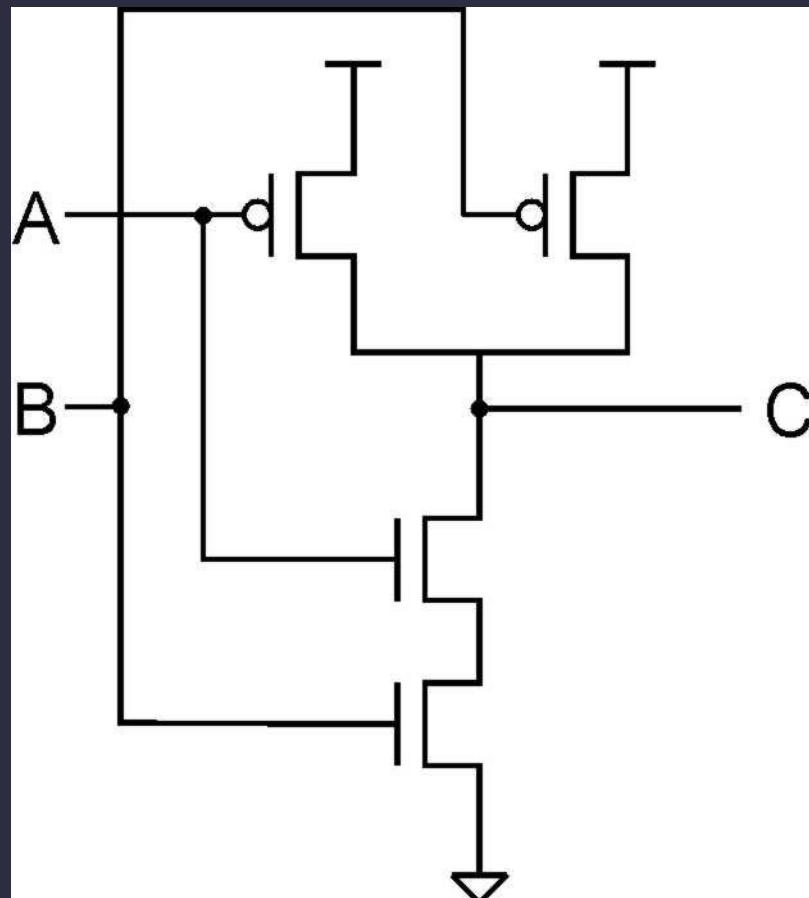


| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

and (AND) gate

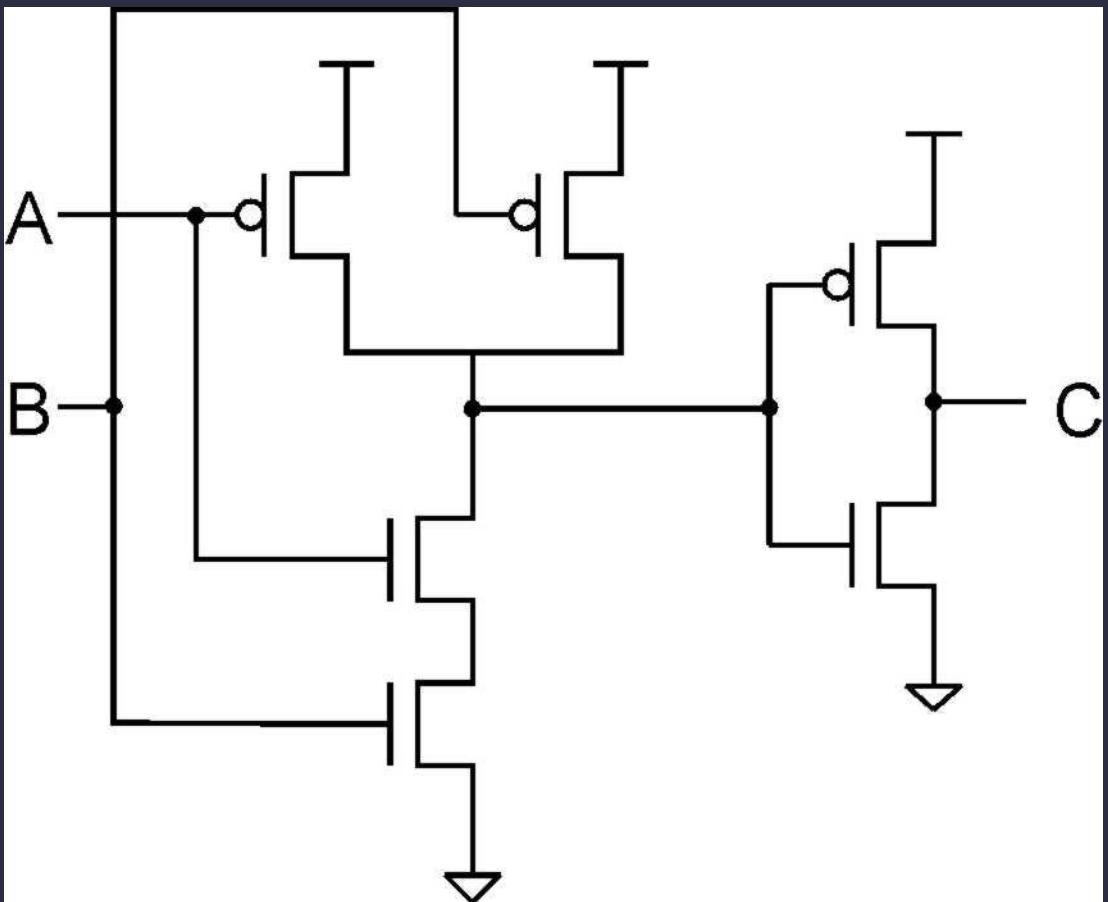


| A | B | C |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Simple Logic Gates

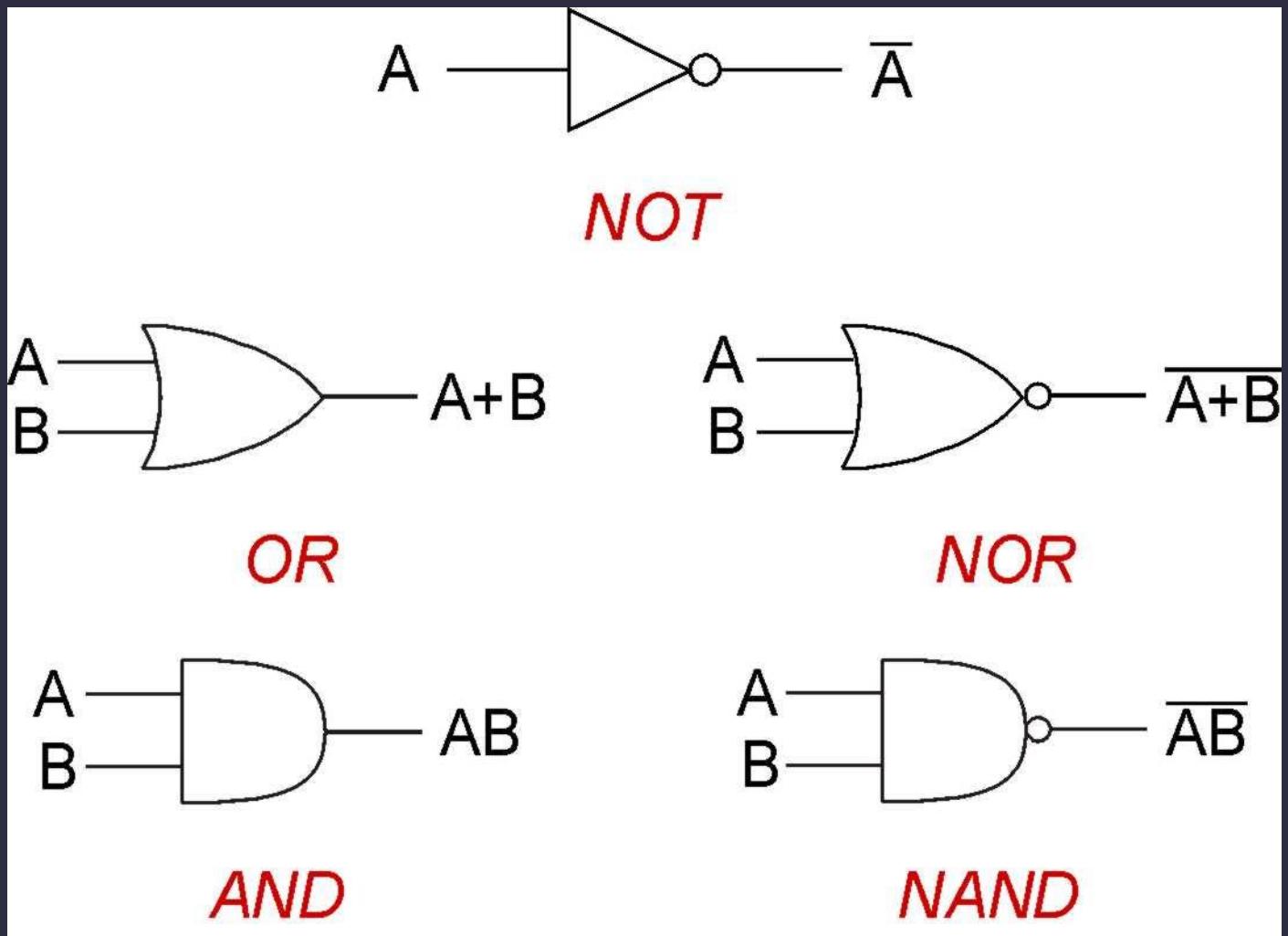

DeMorgan's rule

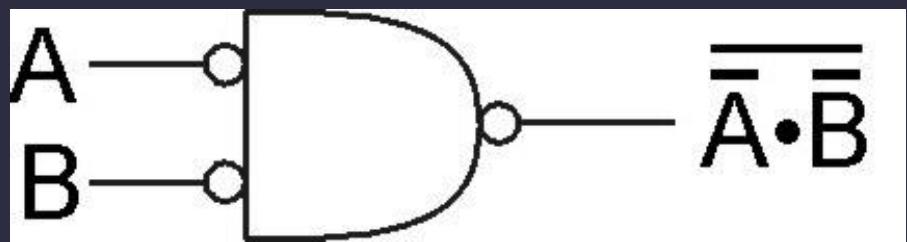- Allows conversion between And – Or gates




$$(\overline{xy}) = \overline{x} + \overline{y}$$

$$\overline{(x+y)} = \overline{x}\overline{y}$$

| A | B | \bar{A} | \bar{B} | $\bar{A} \cdot \bar{B}$ | $\overline{\bar{A} \cdot \bar{B}}$ |
|---|---|-----------|-----------|-------------------------|------------------------------------|
| 0 | 0 | 1 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 1 |

Situations With More Than Two Inputs – Complex Doors

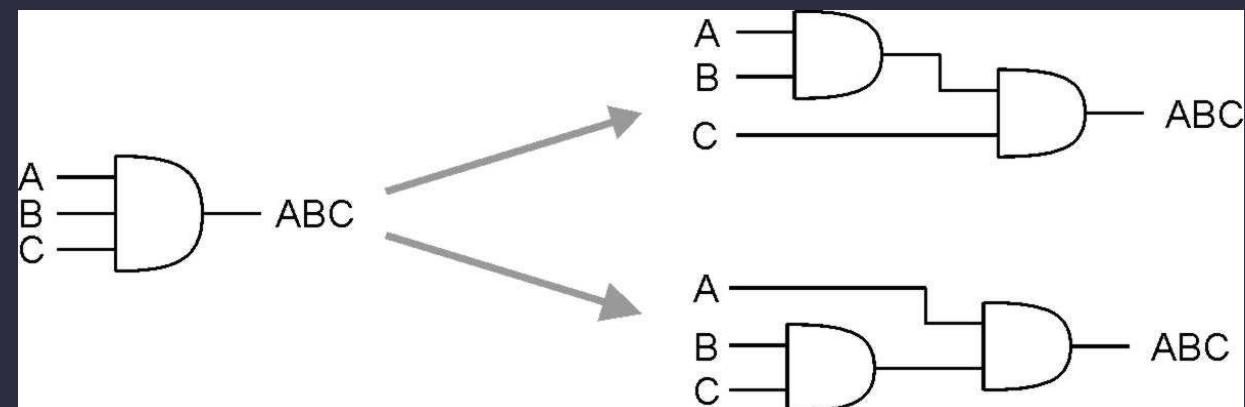- And/or operations can take multiple inputs.
 - And which infers 1 when all inputs are 1
 - Or which infers 1 when any input is 1
- Two-input gates or with a single cmos circuit can be used.



Source Videos

You can access the source videos from the addresses below.

Transistor

<https://www.youtube.com/watch?v=7ukDKVHnac4>

What is MOSFET?

<https://www.youtube.com/watch?v=stM8dgcY1CA>