

# Digital Design

## Week 3: Combinational Logic



Fenerbahce University



# Instructors

Instructor: Dr. Vecdi Emre Levent

Office: 311

Email : [emre.levent@fbu.edu.tr](mailto:emre.levent@fbu.edu.tr)

T.A. Ugur Ozbalkan

Office: 311

Email : [ugur.ozbalkan@fbu.edu.tr](mailto:ugur.ozbalkan@fbu.edu.tr)



# Course Plan


- Combinational Logic

# Combinational Circuit Design Process



	<b>Process</b>	<b>Explanation</b>
Step 1	<b>Create Function</b>	A truth table or equation is created
Step 2	<b>Convert to Equation</b>	Convert truth table to equation. The equation is created by using output rows of 1
Step 3	<b>Create Circuit</b>	Draw the circuit from the equation

# Example : 3 consecutive 1 finder circuits

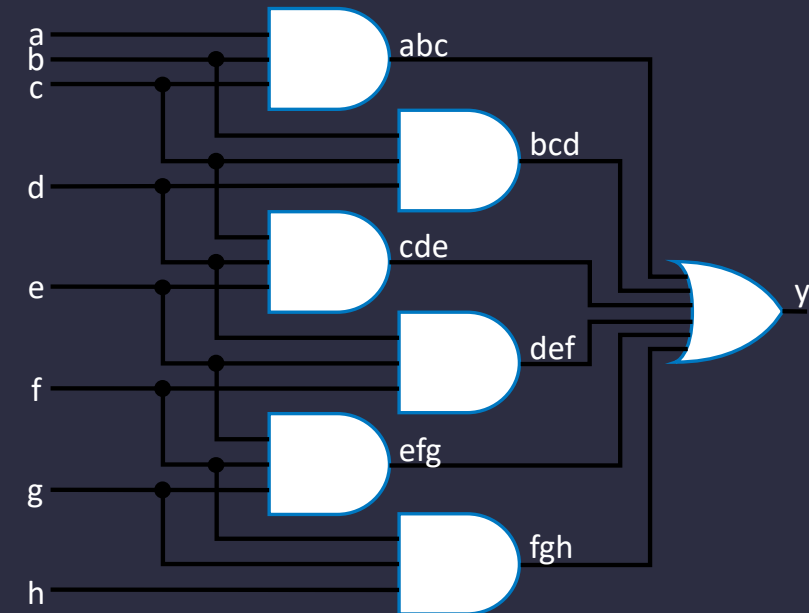- Example : Draw a circuit can find consecutive 1s out in a 8 bit number: abcdefgh
  - 00011101  $\rightarrow$  1    10101011  $\rightarrow$  0    11110000  $\rightarrow$  1
  - **Step 1: Create the function**
    - Truth table or equation ?
      - The truth table will be very long as it will be  $2^8=256$  rows.
      - Equation : Identify and combine equations that will result 1
    - $y = abc + bcd + cde + def + efg + fgh$
  - **Step 2: Convert to equation -- done**
  - **Step 3: Create the circuit**




# Logic Gates

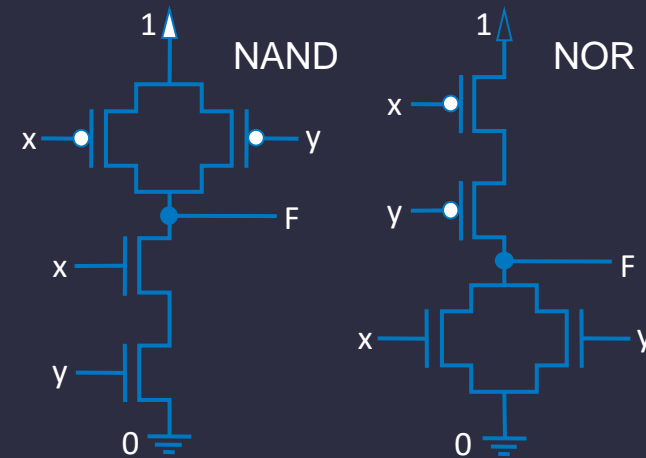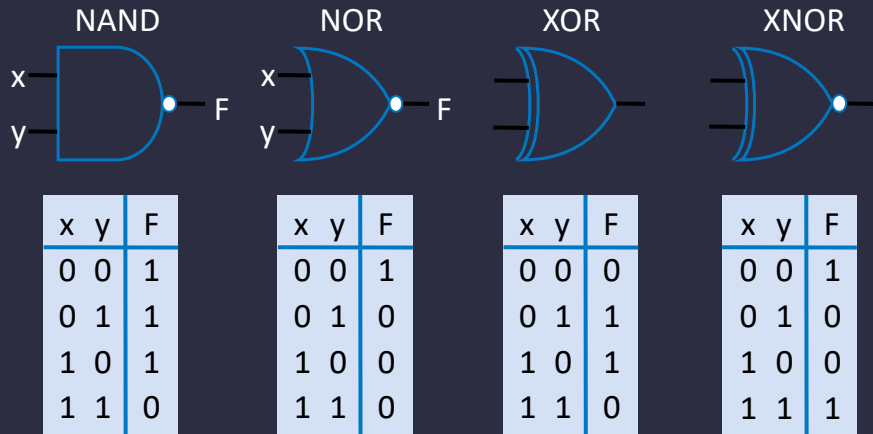

- NAND: NOT AND
- NOR: NOT OR
- XOR: Exclusive OR
- XNOR: NOT XOR

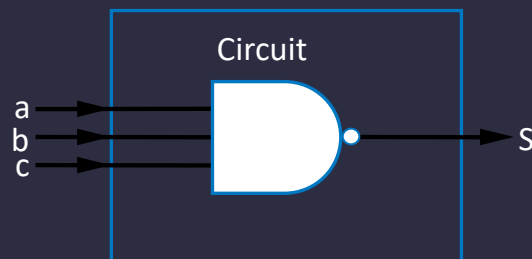
# Logic Gates

- Aircraft sink usage light
  - $S = (abc)'$


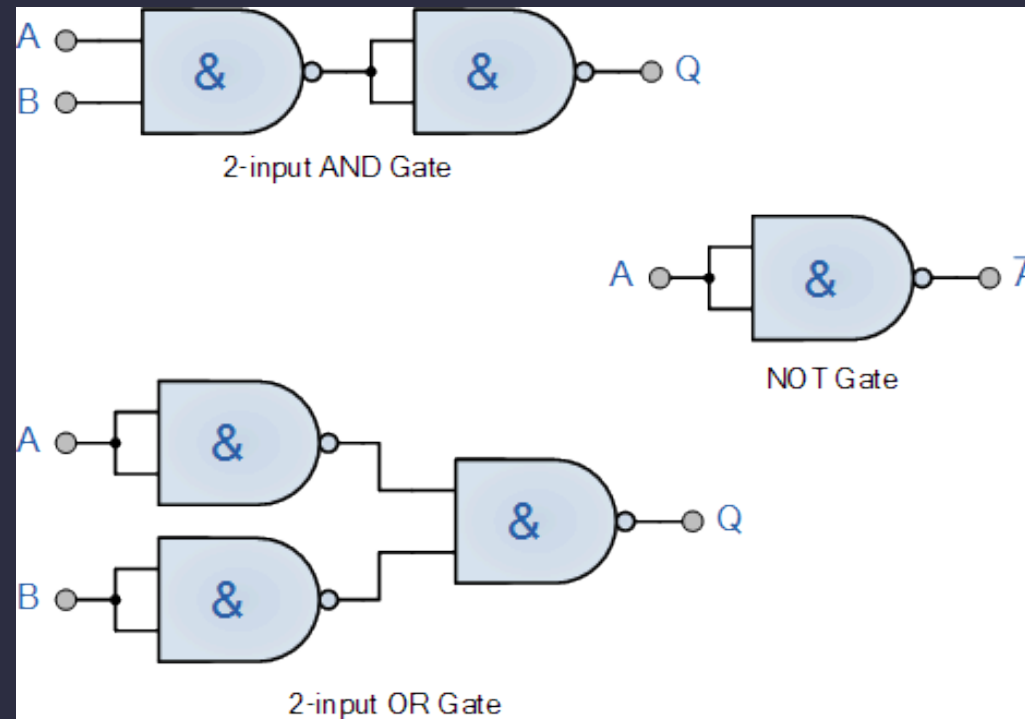
# NAND Gate




- In the digital design the NAND gate is using frequently.
- This is because all circuits can be made with NAND Gate.
  - NOTE
  - AND
  - OR





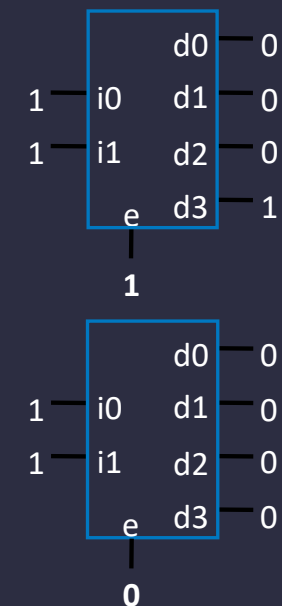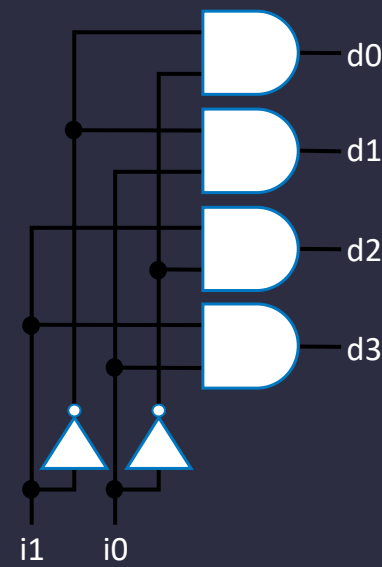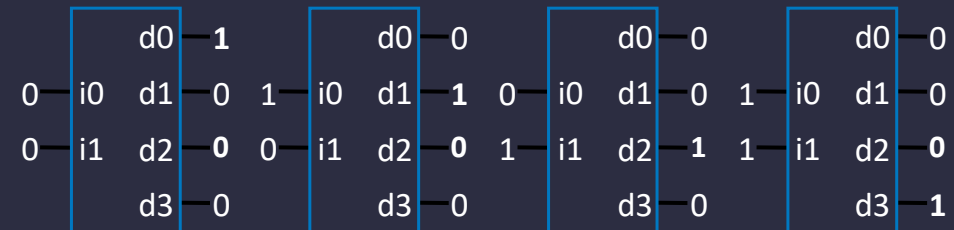
# Decoder and MUX

- **Decoder** : Activates the pin corresponding to the number received in the input.
- 2 -input decoder: There are 4 possible inputs.
  - It has 4 outputs
- Enable with pin decoder
  - If  $e=0$  , all outputs are 0
  - If  $e=1$  , it behaves normally
- N input decoder:  $2^n$  exit



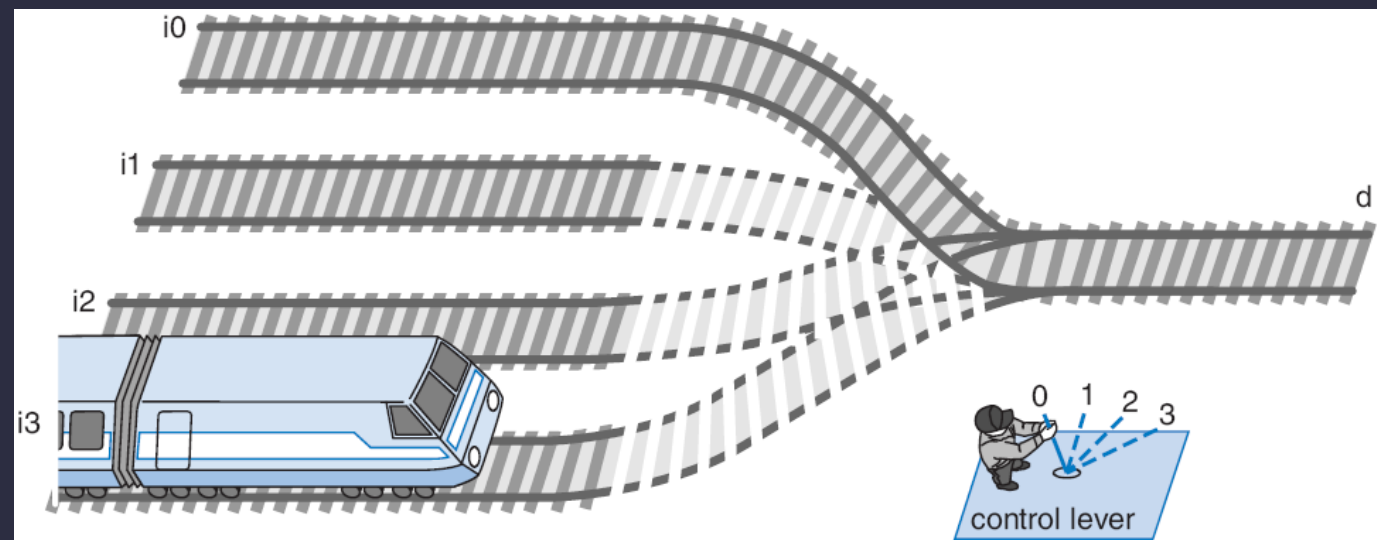
# Multiplexer (Mux)





- Mux: It is a combinational circuit. Outputs incoming inputs according to the select bit.
  - 4 input mux  $\rightarrow$  2 select inputs
  - 8 input mux  $\rightarrow$  3 select input
  - N inputs  $\rightarrow \log_2(N)$  select input




# Mux Internal Structure

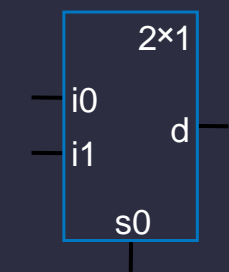


2x1 mux

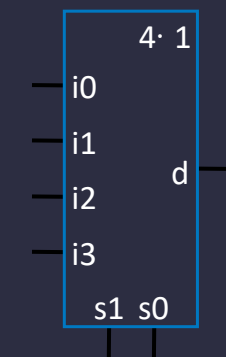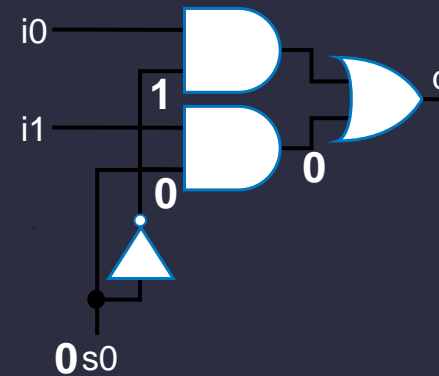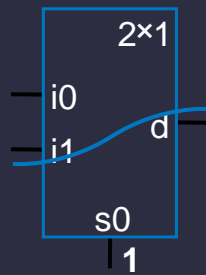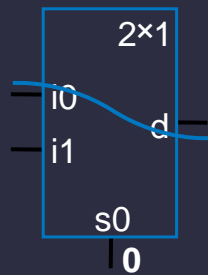

4x1 mux

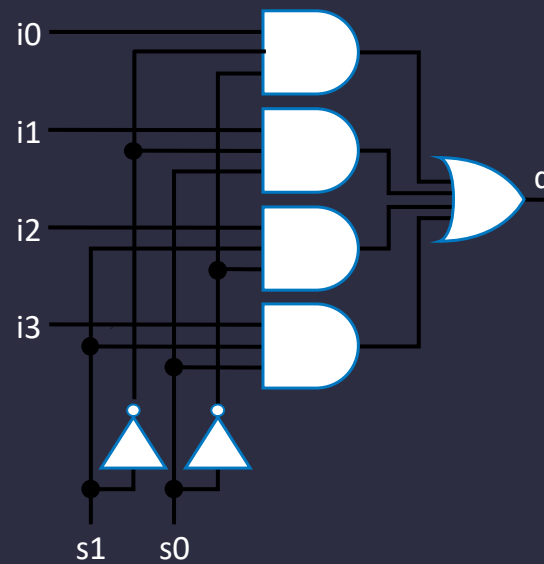


# MUX Merge

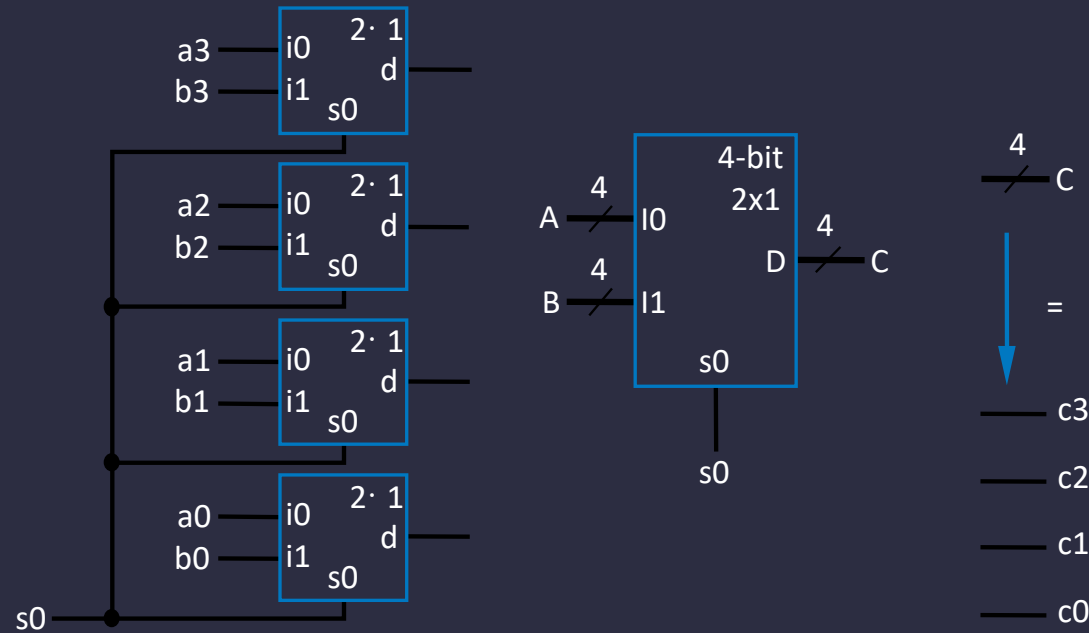


- Example : Two 4-bit inputs , A (a3 a2 a1 a0) and B (b3 b2 b1 b0)
  - 4-bit 2x1 MUX can be done using 4 1 bit, 2x1 MUX

# N-bit MUX Example

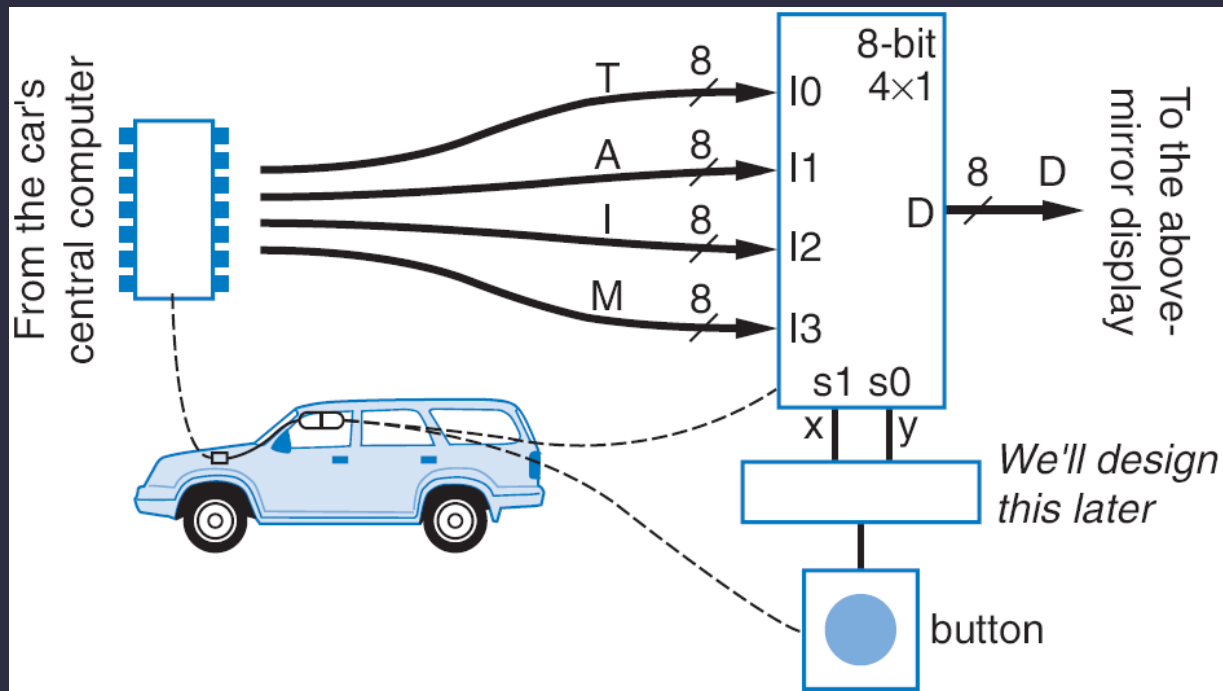

- There are 4 possible texts to display
  - Temperature , Average Fuel Usage , Average Speed , KM Remaining - all
  - Which one will appear on the screen is selected with the x and y bits.
  - 8-bit 4x1 MUX can be used.

# Door Delays

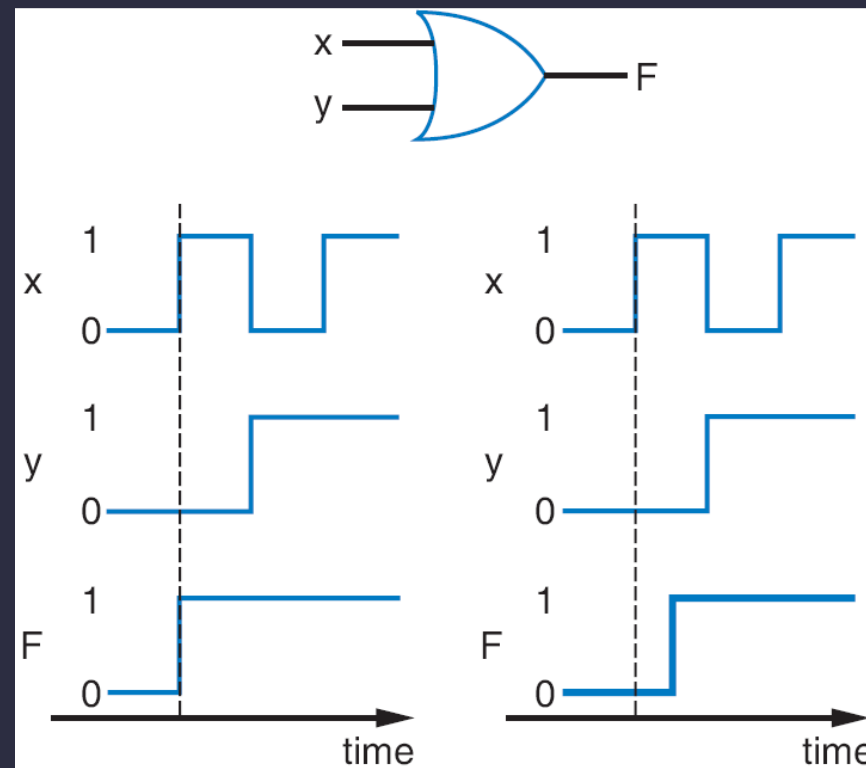

- All circuits have a delay.
  - Outputs don't change instantly