

Digital Design

Week 6: Finite State Machines



Fenerbahçe University



Instructors

Faculty Member: Dr. Vecdi Emre Levent

Office: 311

Email : emre.levent@fbu.edu.tr

R.A. Ugur Ozbalkan

Office: 311

Email : ugur.ozbalkan@fbu.edu.tr


Course

- Finite State Machines




Determining the Behavior of the Sequential Circuit FSM

- Finite-State Machine (FSM)
 - It is a representation of the behavior of the sequential circuit according to the states.
 - Lists states and transitions between states
 - Example : Let there be an output signal named X and each clock change value in cycle
 - Two states : “Off” ($x=0$), and “On” ($x=1$)
 - There are transitions from the Off state to the On state and from the On state to the Off state.
 - The initial state is indicated by an arrow.

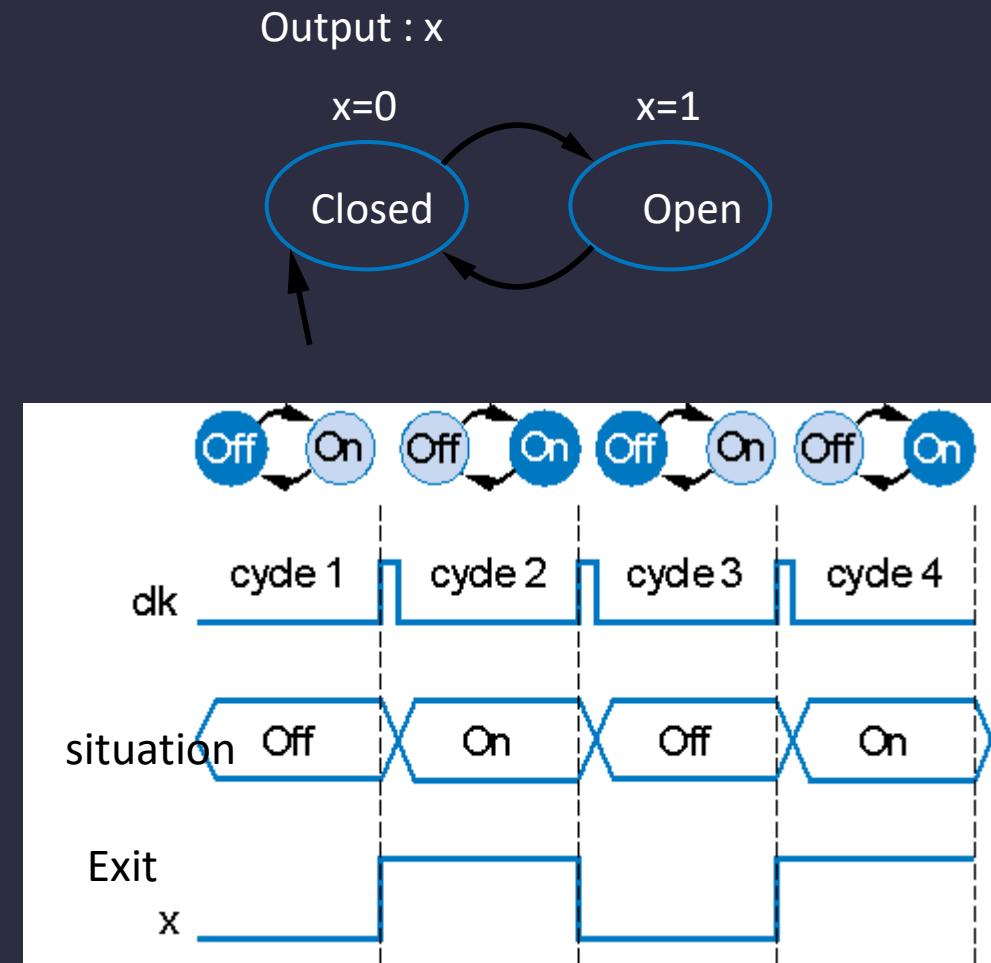

FSM Example : 0,1,1,1, repetition


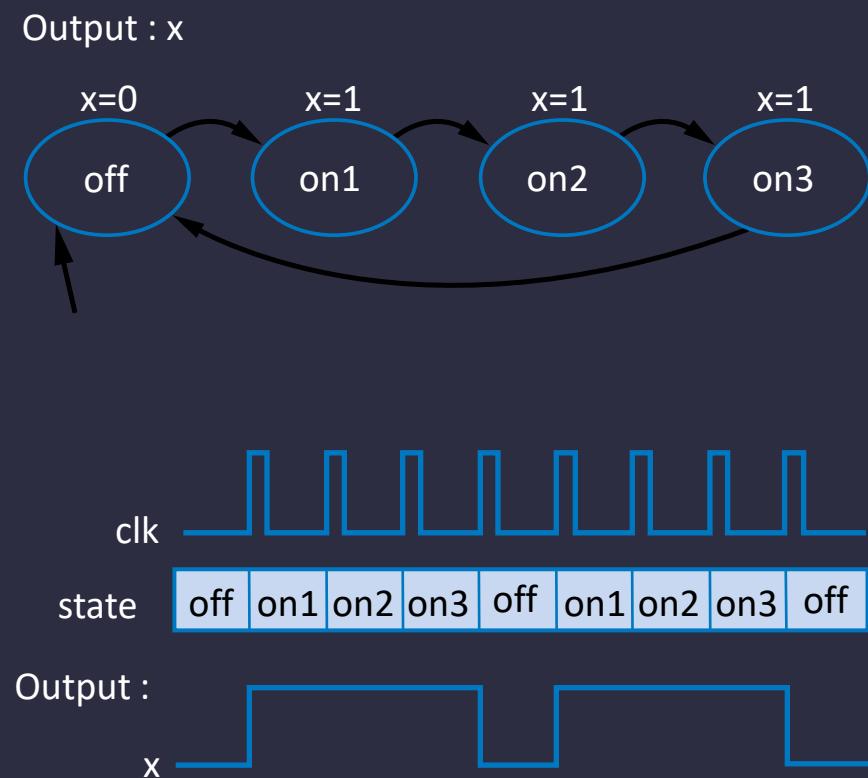
- In order $0, 1, 1, 1, 0, 1, 1, 1, \dots$ A circuit that gives its outputs will be designed.
 - Each value is a clock It appears in the cycle .
- Can be designed with FSM
 - There are 4 states



FSM Example


take a one-bit input named b,
 Output pattern 101 and waits for
 input b again.

Inputs : b; Outputs : x

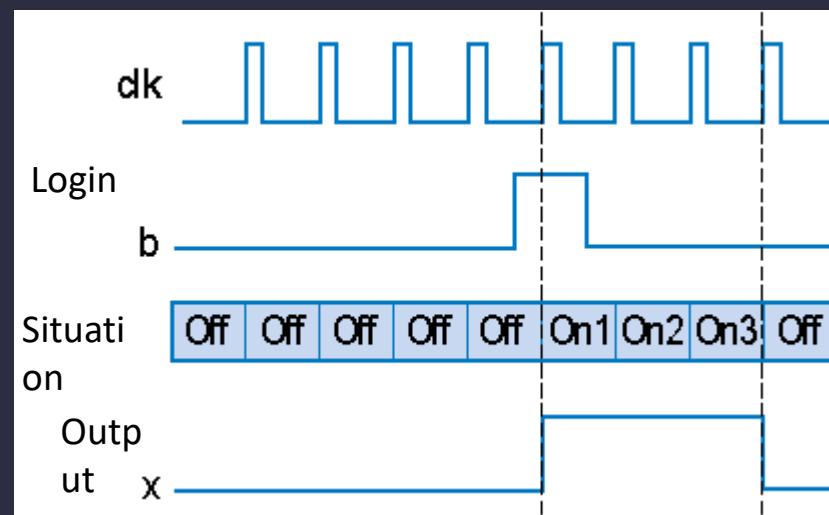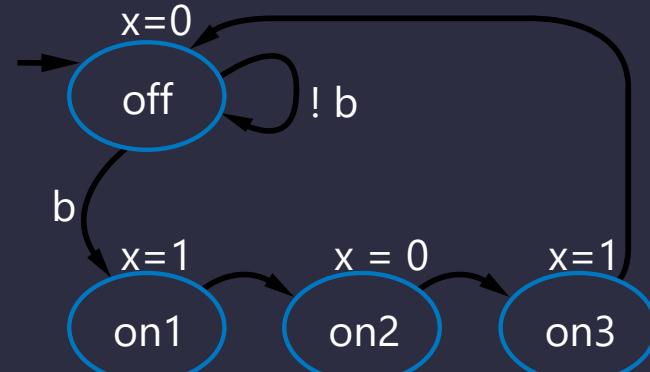



FSM Example: Car Key

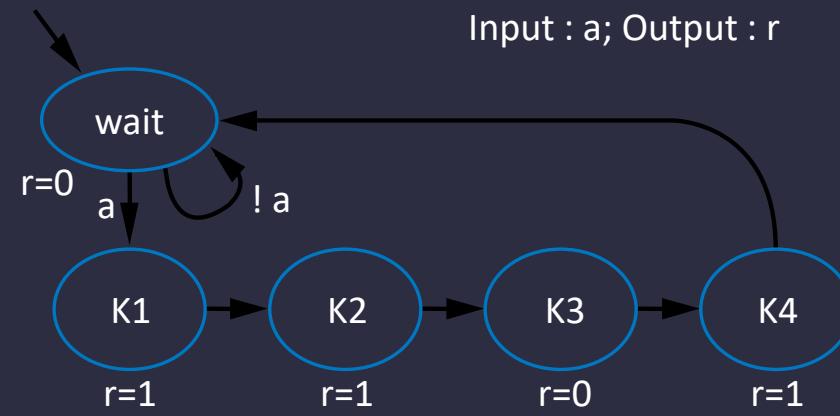- Car keys contain a chip that holds the key's identity.
 - When the key is inserted in the car, it asks the key for identification.
 - Sends key credential, if not correct the tool won't start
- FSM
 - Wait for request ($a=1$)
 - Send ID (For example , 1101)





FSM Example: Car Key

- FSM Timings

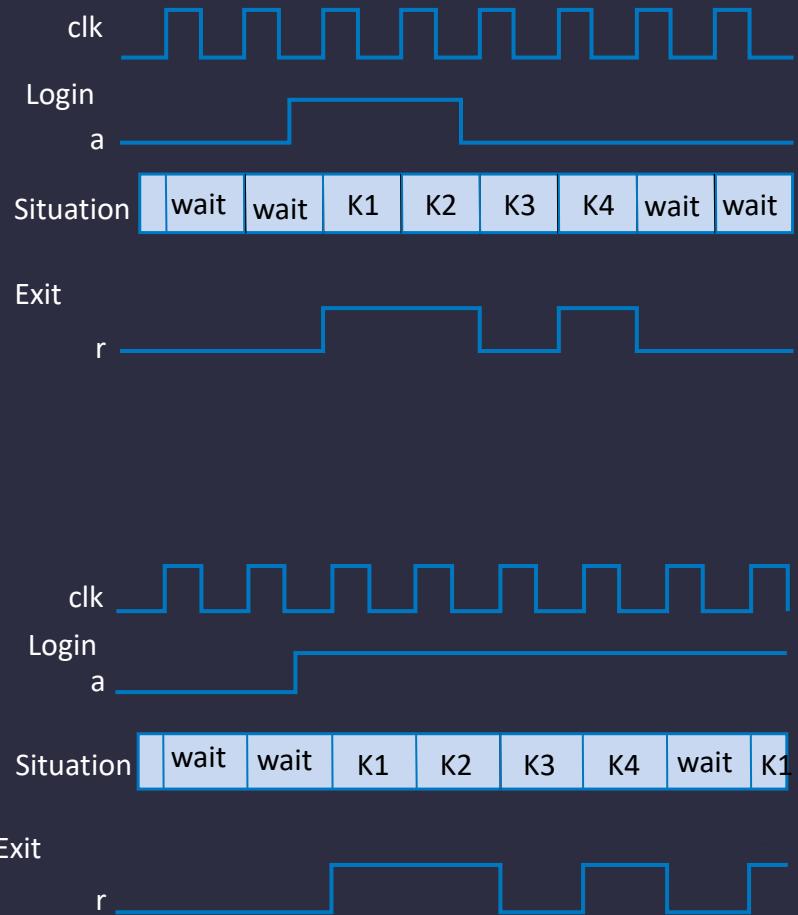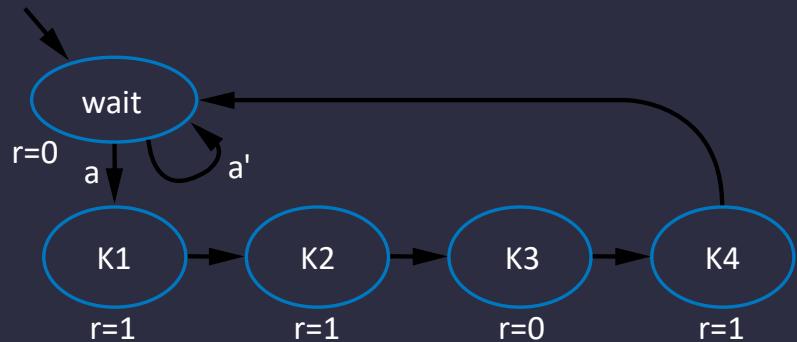


FSM Example: Code Detector

- A door is only opened when the following button sequence is pressed ($u=1$)
 - start , red , blue , green , red
- s, r, g, b
 - If input a, buttons of other color
- FSM
 - While in wait state, start when start
 - When start is pressed
 - If it's red, go to K1
 - Then, if it's blue, M
 - Then, if green, Y
 - Then, if it's red, K2
 - In this case, the signal to open the door is generated ($u=1$)
 - Any wrong input will revert to wait state

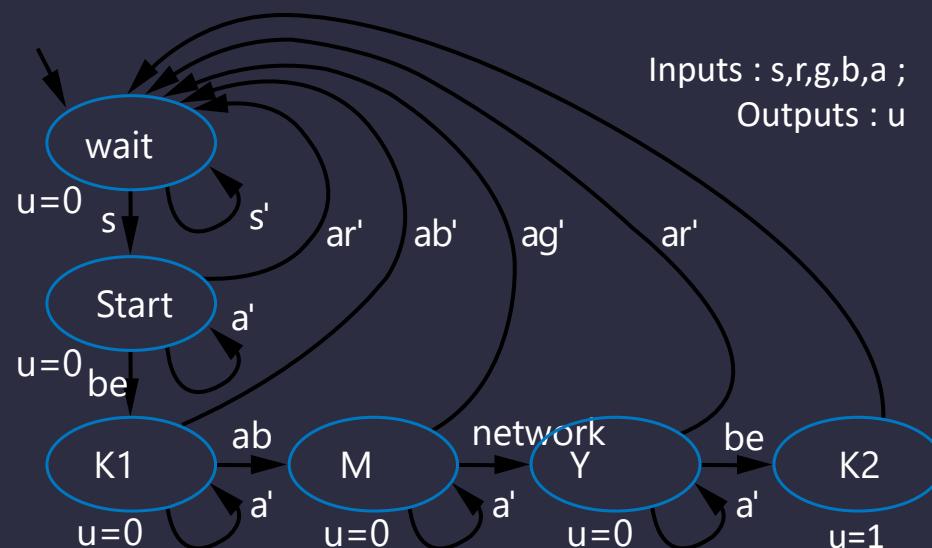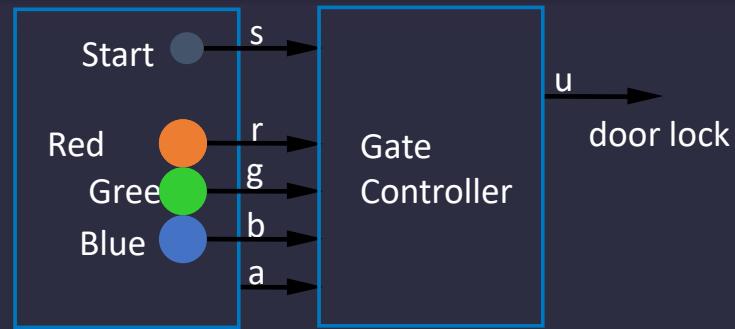




FSM Example: Code Detector, Improvements

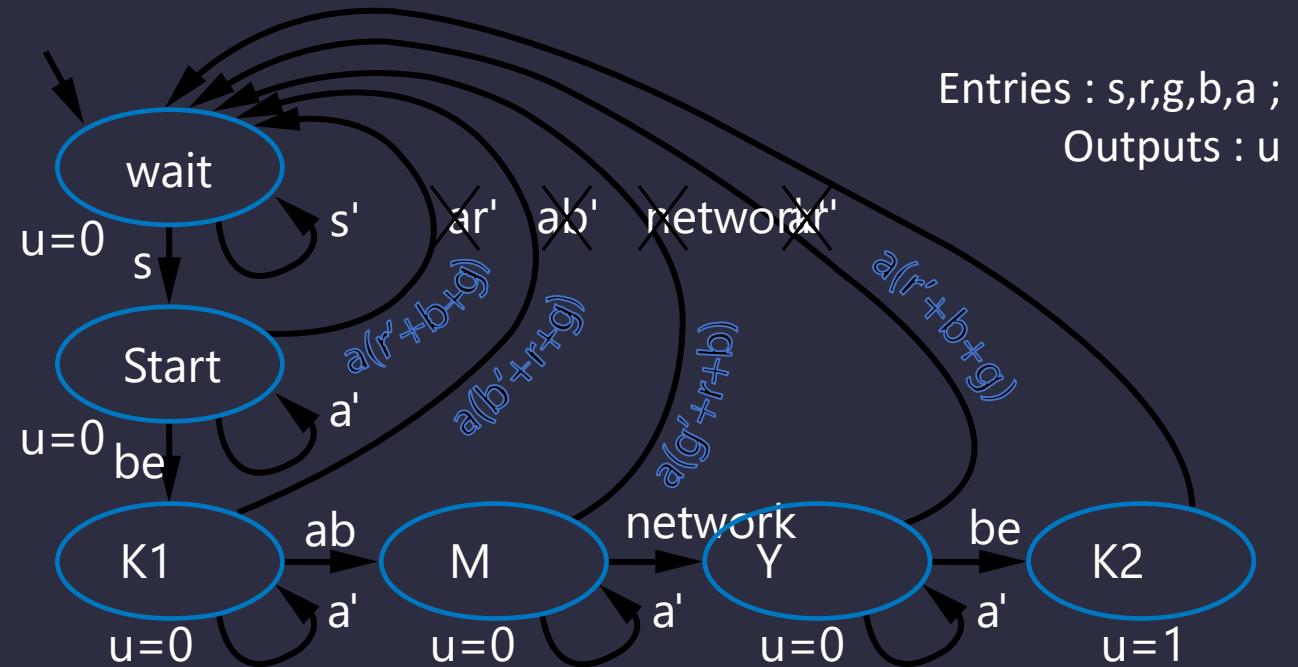

In the new state machine, pressing the wrong button returns to the "Wait" state.



FSM Architecture

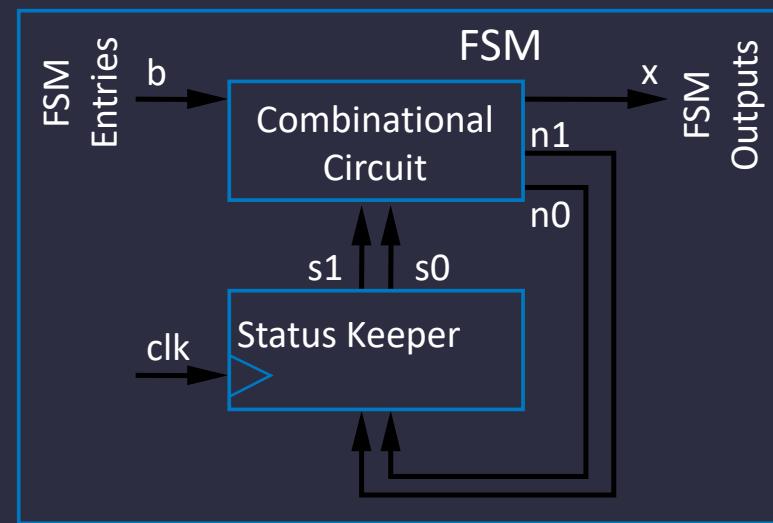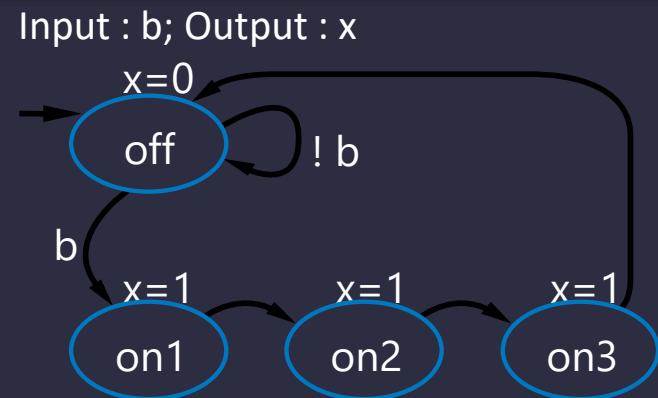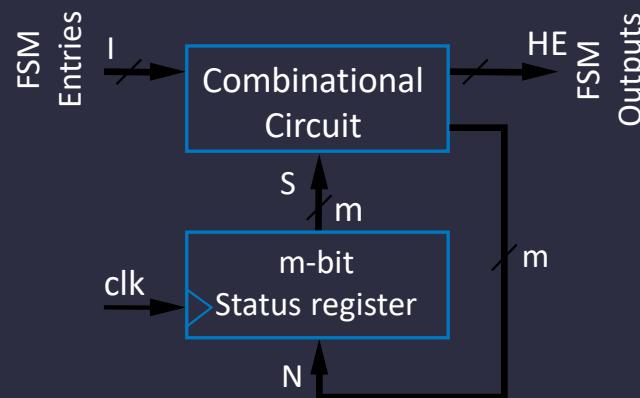- How is FSM implemented as a sequential circuit ?
 - Status register - to keep the current state
 - Combinational circuit – to calculate output and next state



FSM Design Example

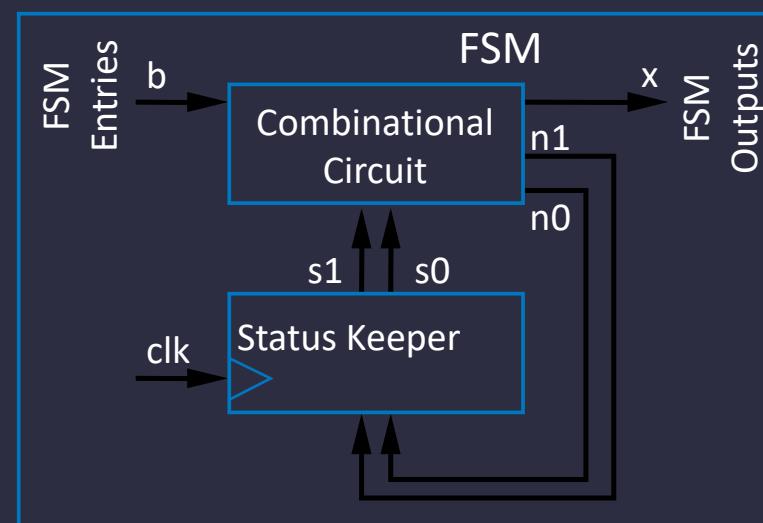
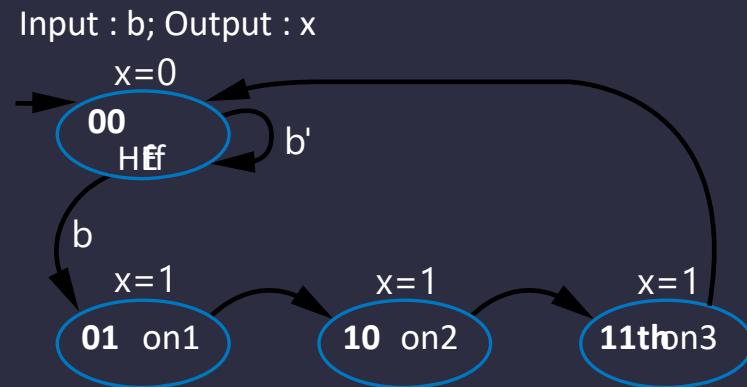
- Step 1: Analyze the requirements
- Step 2: Extract architecture
 - 2-bit state register (for 4 states)
 - Input b, output x
 - Next status signals n₁, n₀
- Step 3: Encode the states



FSM Design Example

- Step 4: Create a Truth Table


	Entries			Outputs		
	s_1	s_0	b	x	n_1	n_0
<i>Off</i>	0	0	0	0	0	0
	0	0	1	0	0	1
<i>On1</i>	0	1	0	1	1	0
	0	1	1	1	1	0
<i>On2</i>	1	0	0	1	1	1
	1	0	1	1	1	1
<i>On3</i>	1	1	0	1	0	0
	1	1	1	1	0	0

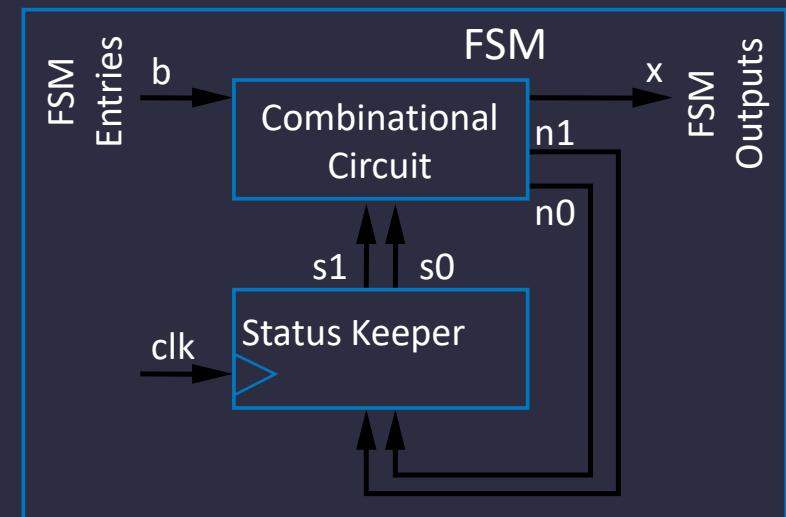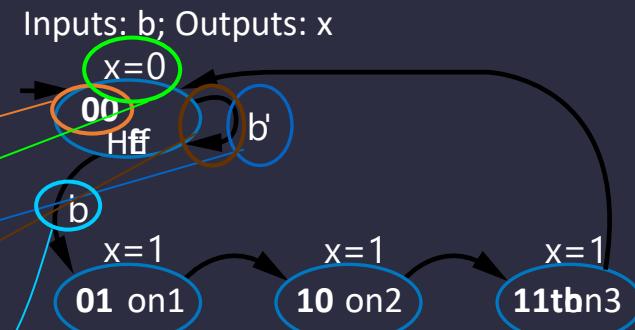

FSM Design Example

- Step 5: Combinational Circuit Implementation

	Entries			Outputs		
	s1	s0	b	x	n1	n0
Off	0	0	0	0	0	0
	0	0	1	0	0	1
On1	0	1	0	1	1	0
	0	1	1	1	1	0
On2	1	0	0	1	1	1
	1	0	1	1	1	1
On3	1	1	0	1	0	0
	1	1	1	1	0	0

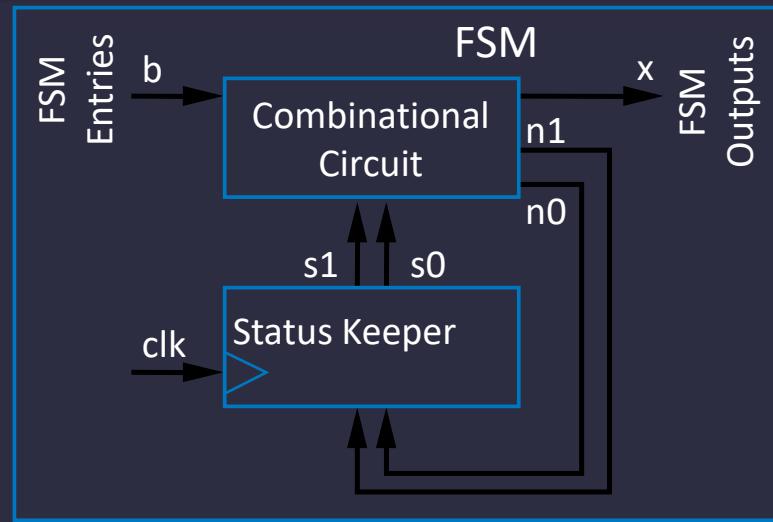

$$x = s1 \mid s0$$

$$n1 = s1's0b' \mid s1's0b \mid s1s0'b' \mid s1s0'b$$

$$n1 = s1's0 \mid s1s0'$$

$$n0 = s1's0'b \mid s1s0'b' \mid s1s0'b$$

$$n0 = s1's0'b \mid s1s0'$$

FSM Design Example


- Step 5: Build the combinational circuit

Entries			Output		
s1	s0	b	x	n1	n0
Off	0	0	0	0	0
	0	0	1	0	1
On1	0	1	0	1	1
	0	1	1	1	0
On2	1	0	0	1	1
	1	0	1	1	1
On3	1	1	0	1	0
	1	1	1	1	0


$$x = s_1 \mid s_0$$

$$n_1 = s_1's_0 \mid s_1s_0'$$



$$n_0 = s_1's_0'b \mid s_1s_0'$$

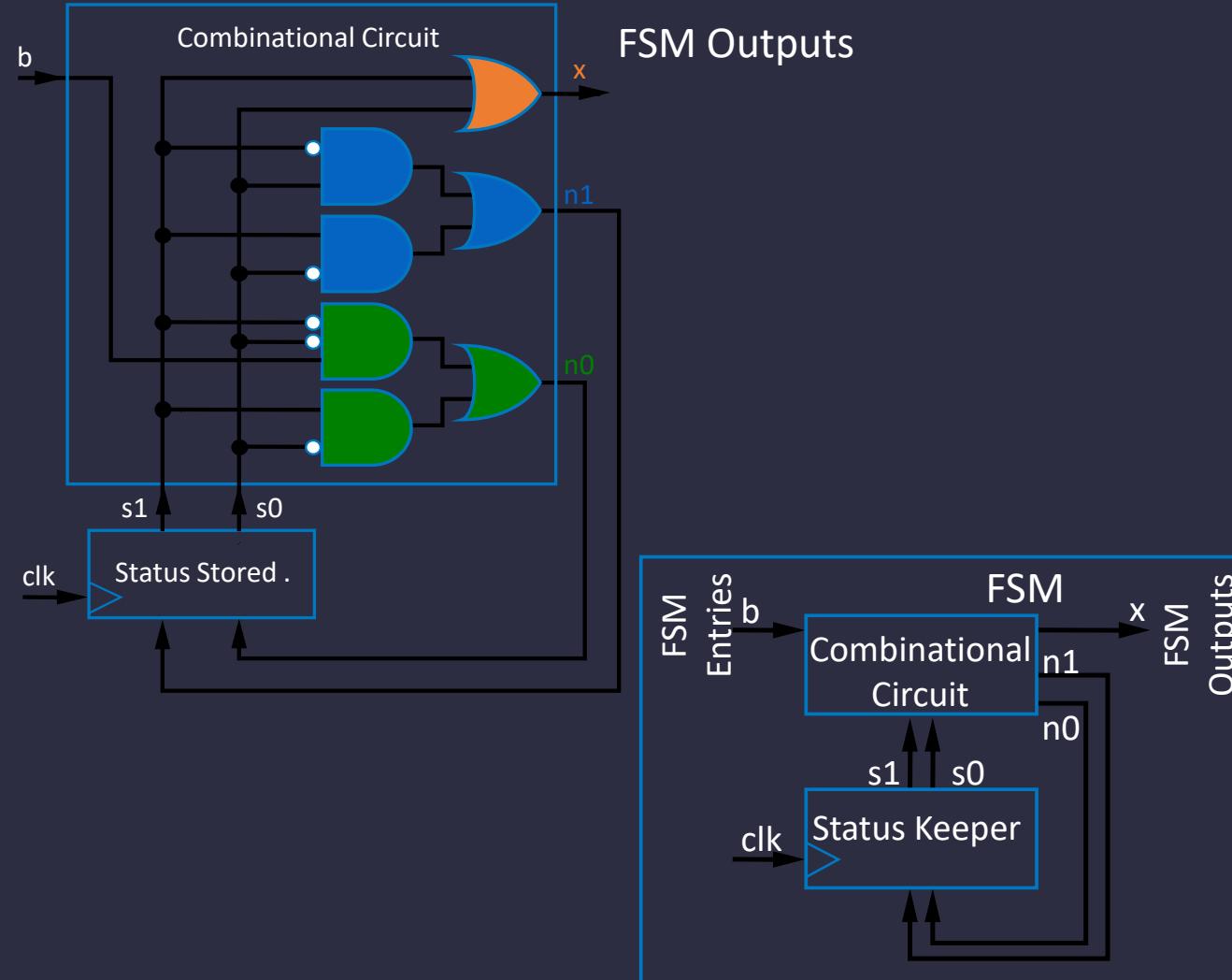

Internal Structure of

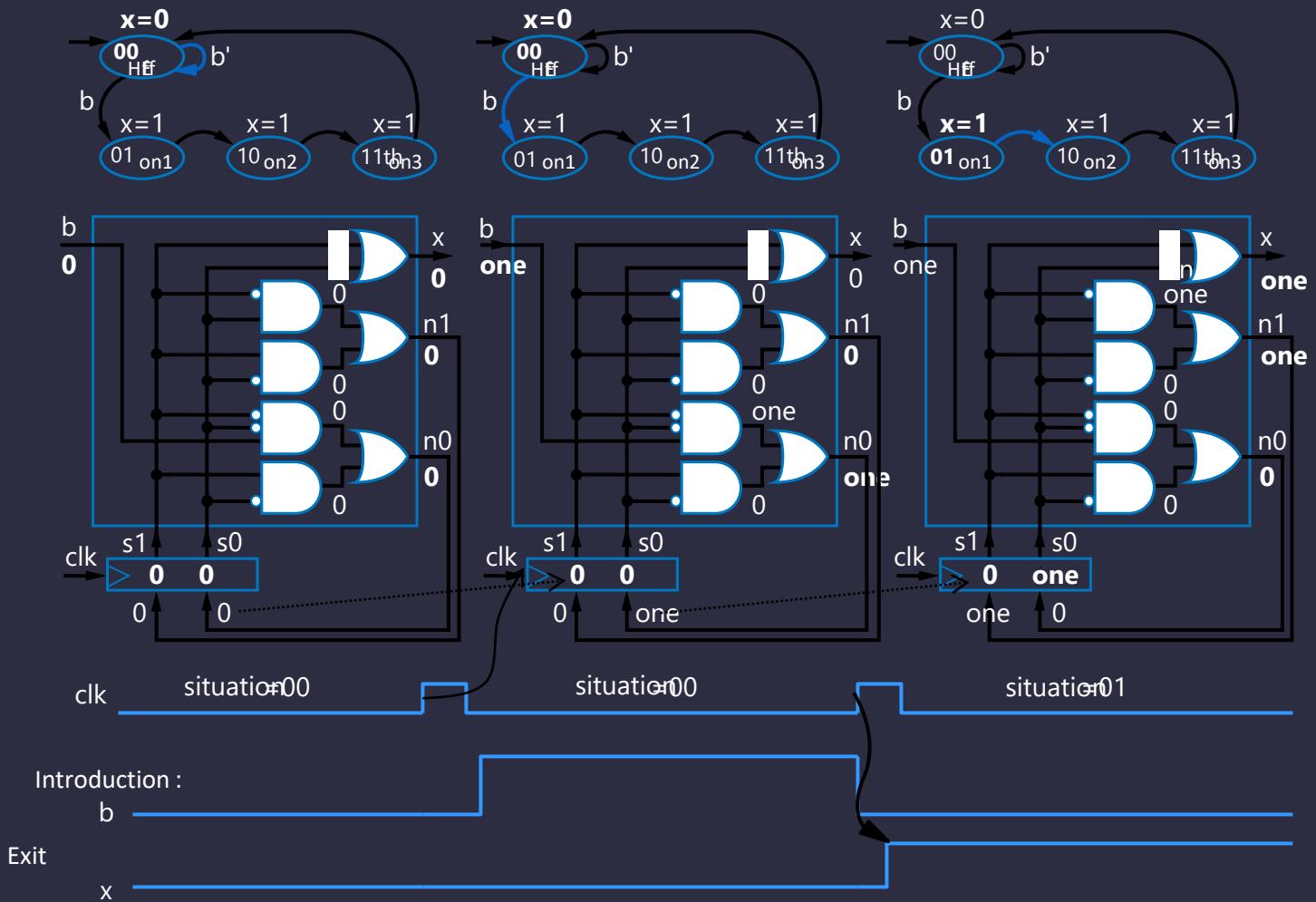


Button Filter Module Example

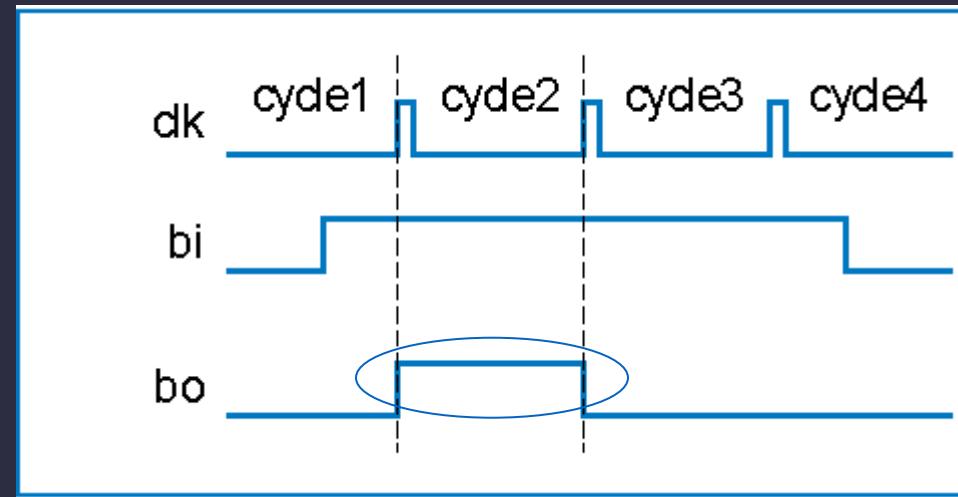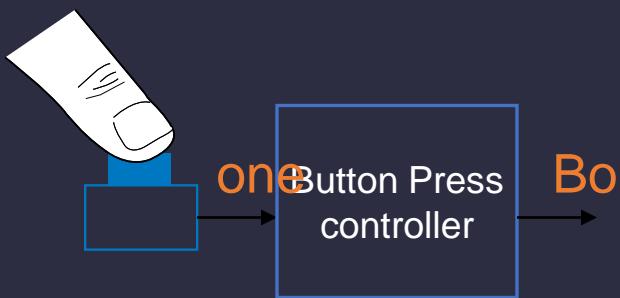

- cycle when the button is pressed A design that produces a pulse is desired.


Button Filter Module Example

FSM Inputs : bi; FSM outputs : bo

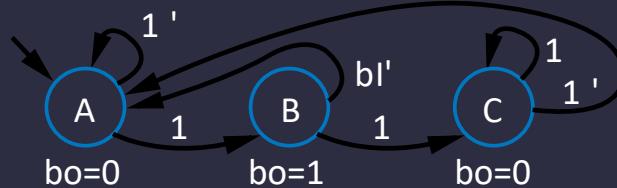


Step 1: FSM

FSM input : bi; FSM output : bo

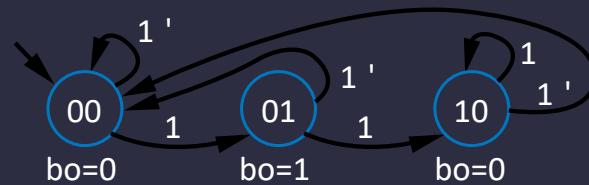

Step 3: State coding

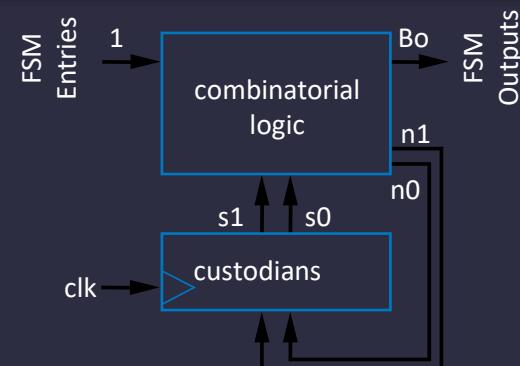


Step 2: Build architecture

Entries			Outputs		
s1	s0	bi	n1	n0	bo
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	0	0

Step 4: Status Chart

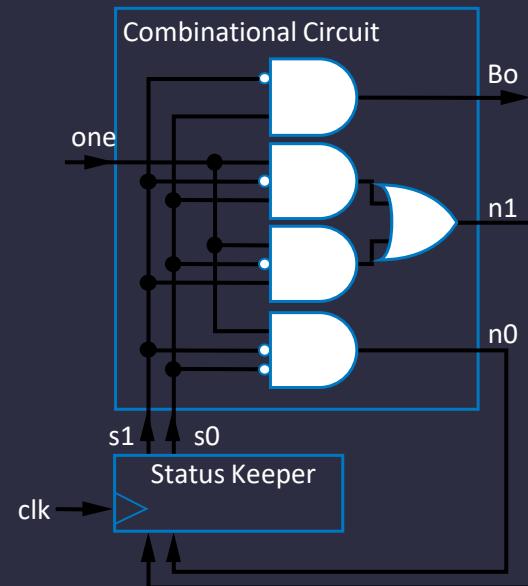
$$\begin{aligned} n1 &= s1's0bi \mid s1s0bi \\ n0 &= s1's0'bi \\ bo &= s1's0bi' \mid s1's0bi = s1s0 \end{aligned}$$



Step 5: Build Circuit


FSM Example

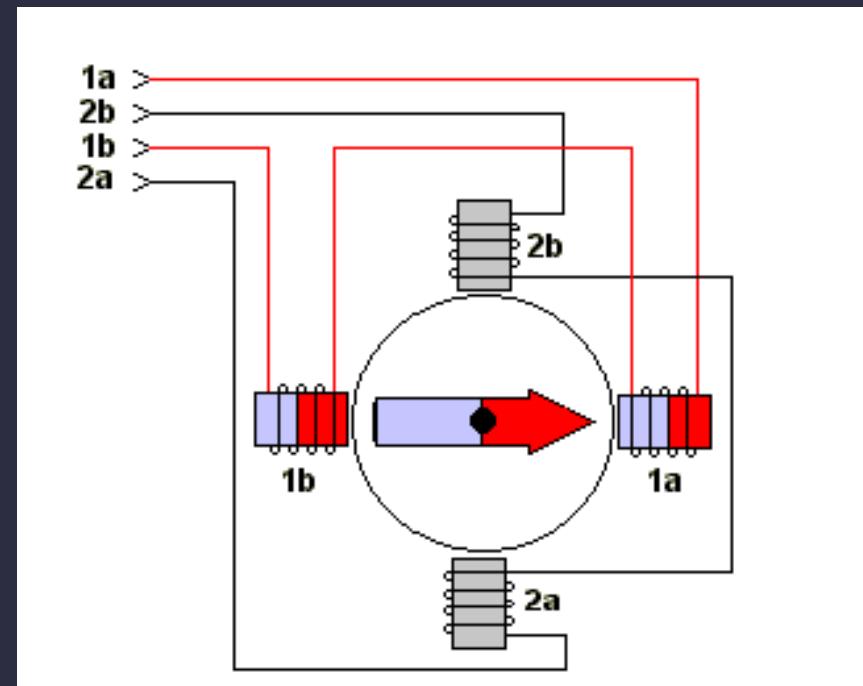- Design an FSM that outputs 0001, 0011, 1100, 1000 sequentially.
 - For example, for stepper motor control



FSM Example

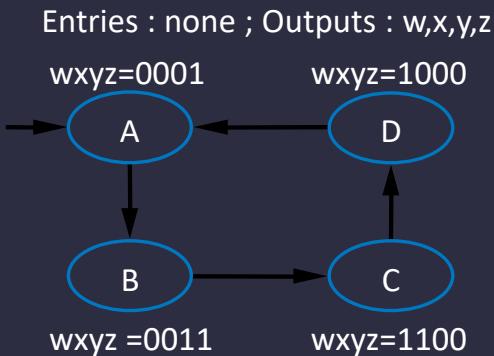
- Design an FSM that outputs 0001, 0011, 1100, 1000 sequentially.
 - For example, for stepper motor control



Step 1: Creating the FSM


Entries	Outputs					
s1 s0	w	x	y	z	n1	n0
A 0 0	0	0	0	1	0	1
B 0 1	0	0	1	1	1	0
C 1 0	1	1	0	0	1	1
D 1 1	1	0	0	0	0	0

Step 4: Create a Truth Table

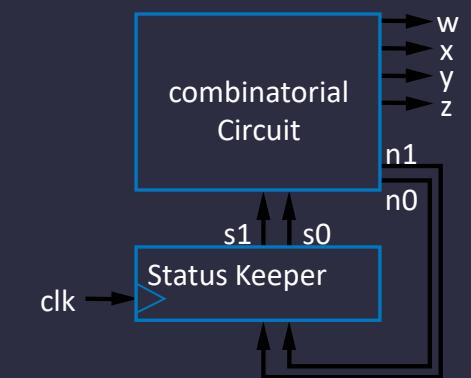


Step 2: Creating Architecture

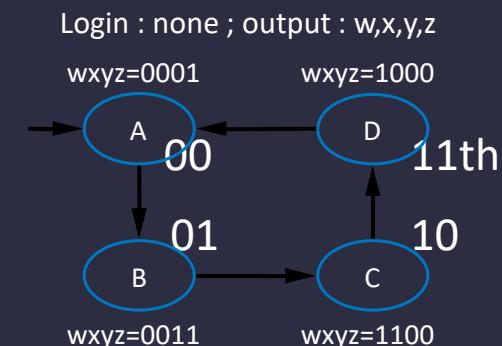
$$\begin{aligned}
 w &= s1 \\
 x &= s1s0' \\
 y &= s1's0 \\
 z &= s1' \\
 n1 &= s1 x \text{ or} \\
 s0 \\
 n0 &= s0'
 \end{aligned}$$



Step 3: State Coding

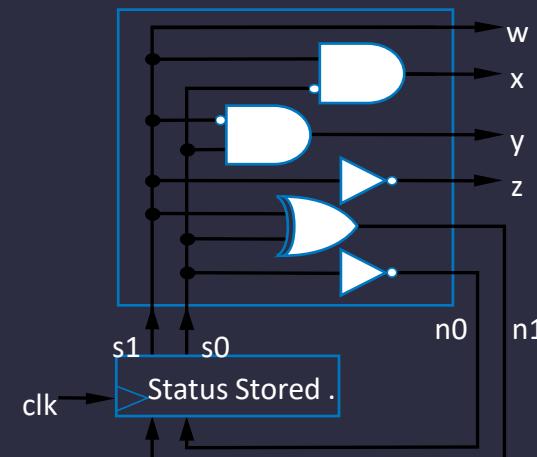

FSM Example, Car Key

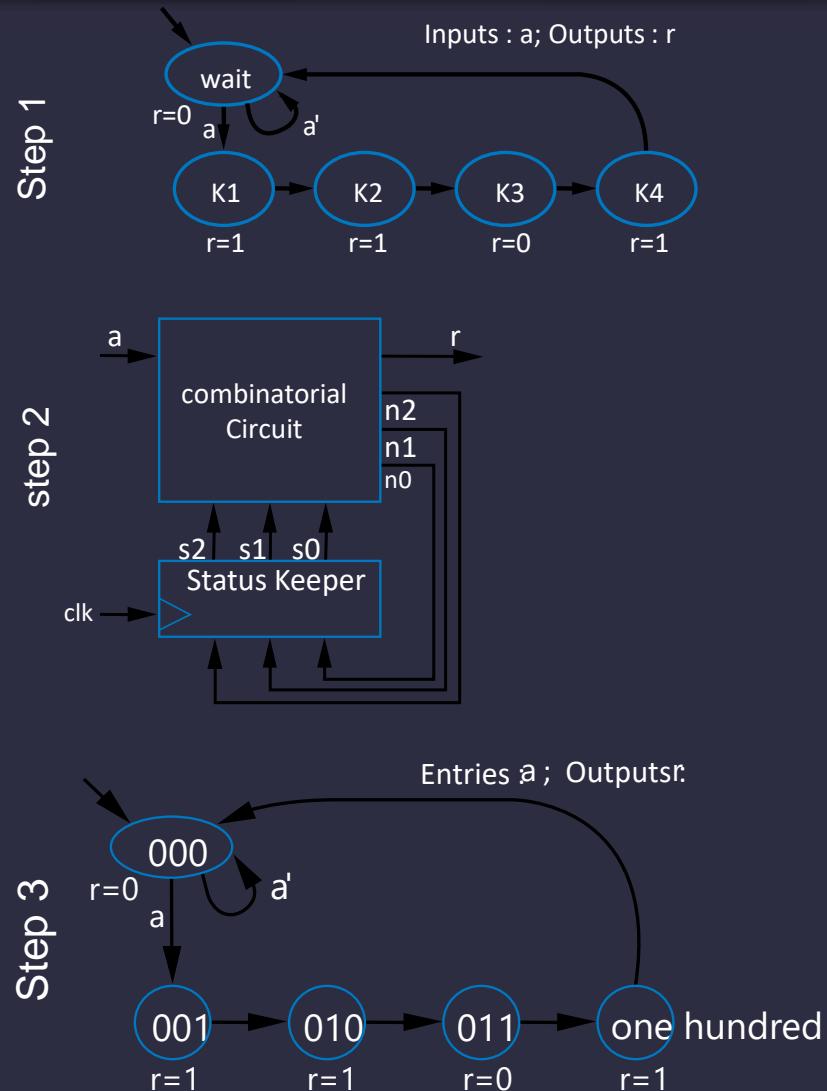


	Entries				Outputs			
	s2	s1	s0	a	r	n2	n1	n0
wait	0	0	0	0	0	0	0	0
	0	0	0	1	0	0	0	1
K1	0	0	1	0	1	0	1	0
	0	0	1	1	1	0	1	0
K2	0	1	0	0	1	0	1	1
	0	1	0	1	1	0	1	1
K3	0	1	1	0	0	1	0	0
	0	1	1	1	0	1	0	0
K4	1	0	0	0	1	0	0	0
	1	0	0	1	1	0	0	0
-	1	0	1	0	0	0	0	0
-	1	0	1	1	0	0	0	0
-	1	1	0	0	0	0	0	0
-	1	1	0	1	0	0	0	0
-	1	1	1	0	0	0	0	0
-	1	1	1	1	0	0	0	0

Step 4


Reverting to

What does this circuit do?

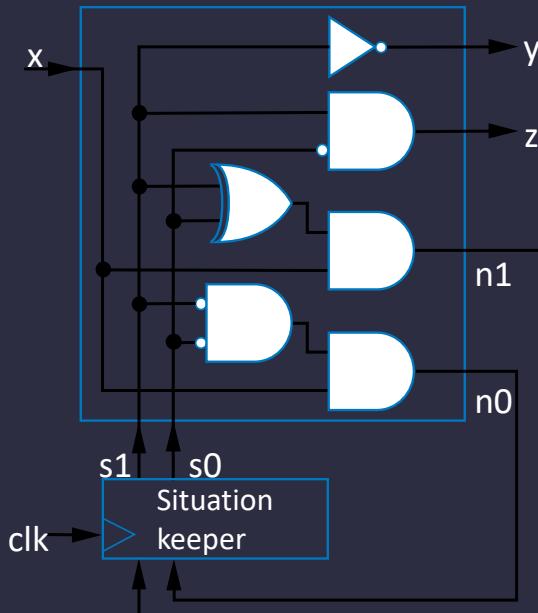


$$\begin{aligned}
 y &= s_1' \\
 z &= s_1 s_0' \\
 n_1 &= (s_1 x \text{ or } s_0) \\
)x \\
 n_0 &= (s_1' * s_0')x
 \end{aligned}$$

Entries			Outputs				
	s_1	s_0	x	n_1	n_0	y	z
A	0	0	0	0	0	1	0
	0	0	1	0	1	1	0
B	0	1	0	0	0	1	0
	0	1	1	1	0	1	0
C	1	0	0	0	0	0	1
	1	0	1	1	0	0	1
D	1	1	0	0	0	0	0
	1	1	1	0	0	0	0


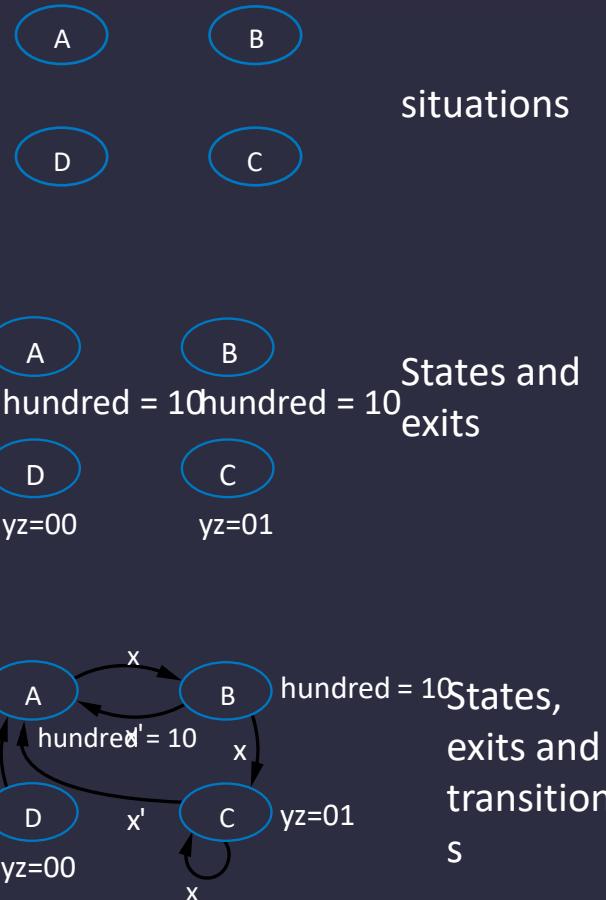


FSM Design Errors

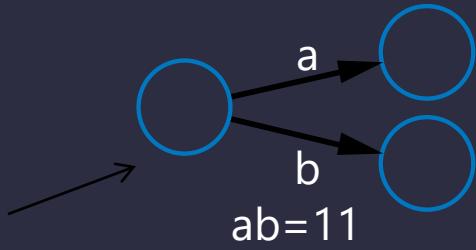- In conditions in transitions between states, only one transition condition must be true at a time*



What will be the next situation?

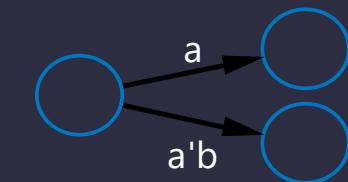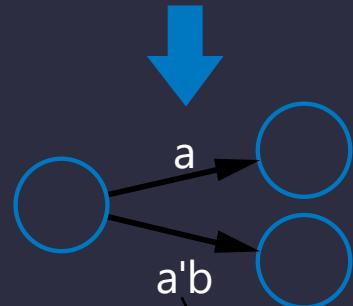

ab=00?
What will be the next situation?

