## **Electronic Circuits**

## Week 5: Parallel Circuit



Fenerbahçe University



#### Professor & TAs

Prof: Dr. Vecdi Emre Levent Office: 311 Email: emre.levent@fbu.edu.tr TA: Arş. Gör. Uğur Özbalkan Office: 311 Email: ugur.ozbalkan@fbu.edu.tr



## The Applied Voltage $V_A$ Is the Same Across Parallel Branches

Characteristics of a Parallel Circuit.

- Voltage is the same across each branch in a parallel circuit.
- The total current is equal to the sum of the individual branch currents.
- The equivalent resistance  $(R_{EQ})$  is less than the smallest branch resistance. The term equivalent resistance refers to a single resistance that would draw the same amount of current as all of the parallel connected branches.
- Total power is equal to the sum of the power dissipated by each branch resistance.



## The Applied Voltage $V_A$ Is the Same Across Parallel Branches

Example of a parallel circuit with two resistors. (a) Wiring diagram. (b) Schematic diagram.





## Each Branch / Equals $V_A / R$

• The current in a parallel circuit equals the voltage applied across the circuit divided by the resistance between the two points where the voltage is applied.

 $\frac{V}{R}$ 

• Each path for current in a parallel circuit is called a **branch**.

Each branch current equals

where V is the same

across all branches.



## Each Branch / Equals $V_A / R$

Parallel circuit.

(a) the current in each parallel branch equals the applied voltage  $V_A$  divided by each branch resistance R.





## Kirchhoff's Current Law (KCL)

- The pair of leads connecting all the branches to the voltage source terminals is the **main line**.
- All the current in the circuit must come from one side of the voltage source and return to the opposite side for a complete path.
- The amount of current in the main line is equal to the total of the branch currents.



## Kirchhoff's Current Law (KCL)



#### • The total current $I_T$ in the main line is equal to the sum of the branch currents.

- This is known as Kirchhoff's current law (KCL).
- It applies to any number of parallel branches, whether the resistances in those branches are equal or not.

#### $I_{T} = I_{1} + I_{2} + I_{3} + I_{4}$



• The combined equivalent resistance of a parallel circuit may be found by dividing the common voltage across all resistances by the total current of all the branches.

$$R_{EQ} = \frac{V_A}{I_T}$$



- The equivalent resistance of a parallel circuit must be less than the smallest branch resistance.
- Adding more branches to a parallel circuit reduces the equivalent resistance because more current is drawn from the same voltage source.



How adding parallel branches of resistors increases  $I_T$  but decreases  $R_{EQ}$ .

(a) One resistor. (b) Two branches. (c) Three branches. (d) Equivalent circuit of the three branches in (c).



# RSITES

#### **Resistance in Parallel**

Total Current and Reciprocal Resistance Formulas.

• In a parallel circuit, the total current equals the sum of the individual branch currents:

 $I_{\rm T} = I_1 + I_2 + I_3 + \ldots + {\rm etc.}$ 

• Total current is also equal to total voltage divided by equivalent resistance:

$$I_{\rm T} = \frac{V_{\rm T}}{R_{\rm EQ}}$$

# RSITES

### **Resistance in Parallel**

Total Current and Reciprocal Resistance Formulas.

• The equivalent resistance of a parallel circuit equals the reciprocal of the sum of the reciprocals:

$$R_{EQ} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \text{ etc.}}$$

Equivalent resistance also equals the applied voltage divided by the total current:

$$R_{EQ} = \frac{V_A}{I_T}$$



#### • Determining the Equivalent Resistance.



Two methods of combining parallel resistances to find R<sub>EQ</sub>. (a) Using the reciprocal

resistance formula to calculate  $R_{EQ}$  as  $4\Omega$ . (b) Using the total line current method with an for  $R_{EQ}$ . assumed line voltage of 20 V gives the same  $4\Omega$ 

# ALLER UNITERSITES

#### **Resistance in Parallel**

Special Case: Equal Value Resistors.

• If *R* is equal in all branches, divide one resistor's value by the number of resistors (N).



For the special case of all branches having the same resistance, just divide R by the

number of branches (N) to find R<sub>EQ</sub>. Here,  $R_{EQ} = \frac{60 \text{ k}\Omega}{3 = 20 \text{ k}\Omega}$ 



Special Case: Two Unequal Resistors.

• When there are only two branches in a parallel circuit and their resistances are unequal, use the formula:

$$R_{EQ} = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$R_{EQ} = \frac{24 \Omega}{40 \Omega}$$

$$R_{EQ} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{2400}{100}$$

For the special case of only two branch resistances, of any values, R<sub>EQ</sub> equals

their product divided by the sum. Here, 
$$R_{EQ} = \frac{2400}{100 = 24 \Omega}$$



• To find an unknown branch resistance, rewrite the formula as follows to solve for the unknown value.

$$R_{X} = \frac{R \times R_{EQ}}{R - R_{EQ}}$$

• These formulas may be used to simplify complex circuits.



## Total Power in Parallel Circuits

• Total power is equal to the sum of the power dissipated by the individual resistances of the parallel branches:

 $P_T = P_1 + P_2 + P_3 + \dots + \text{etc.}$ 

• Total power is equal to voltage times total current:

$$P_T = V_T I_T$$



## **Total Power in Parallel Circuits**

#### • Determining Power.



Check:  $P_T = V_T \times I_T = 10 V \times 3 A = 30 W$ 

The sum of the power values  $P_1$  and  $P_2$  used in each branch equals the total power  $P_T$  produced by the source.



Opens in Parallel Circuits.

- An open circuit in one branch results in no current through that branch.
- However, an open circuit in one branch has no effect on the other branches. This is because the other branches are still connected to the voltage source.
- An open in the main line prevents current from reaching any branch, so all branches are affected.



• Opens in Parallel Circuits.



In Figure (b) bulbs 2 and 3 still light. However, the total current is smaller. In (a) no bulbs light.



Shorts in a Parallel Circuit.

- A short circuit has zero resistance, resulting in excessive current in the shorted branch.
- A shorted branch shorts the entire circuit.
- Current does not flow in the branches that are not shorted. They are bypassed by the short circuit path that has zero resistance.



• A Short in a Parallel Circuit.



The other branches are shorted out. The total current is very high.



## Finding $R_{\tau}$ for Series-Parallel Resistances

Overview of Series-Parallel Circuits.

- A series-parallel circuit, or combination circuit, combines both series and parallel connections.
- Most electronic circuits fall into this category.
   Series-parallel circuits are typically used when different voltage and current values are required from the same voltage source.
- Series components form a series string.
- Parallel components form a parallel bank.



## Finding $R_T$ for Series-Parallel Resistances

• Overview of Series-Parallel Circuits.



There are three branches in this circuit; sections 1 and 2 are series strings.



## Finding $R_T$ for Series-Parallel Resistances

• Overview of Series-Parallel Circuits.



There are three series sections in this circuit; sections 1 and 2 are parallel banks.



## Finding $R_{\tau}$ for Series-Parallel Resistances

- To find  $R_{\tau}$  for a series-parallel circuit, add the series resistances and combine the parallel resistances.
- In this diagram, R<sub>1</sub> and R<sub>2</sub> are in series, and R<sub>3</sub> and R<sub>4</sub> are in parallel.
- However, R<sub>2</sub> is <u>not</u> in series with either R<sub>3</sub> or R<sub>4</sub>. Resistances in series have the same current, but the current in R<sub>2</sub> is equal to the <u>sum</u> of the branch currents I<sub>3</sub> and I<sub>4</sub>.



Schematic diagram of a series-parallel circuit.



#### Finding $R_T$ for Series-Parallel Resistances

• The series resistances are:

 $0.5k\Omega + 0.5k\Omega = 1k\Omega$ 

• The equivalent resistance of the parallel resistances is:

$$\frac{1 \text{ k}\Omega}{2} = 0.5 \text{ k}\Omega$$



#### **Resistance Strings in Parallel**



• In this figure, branch 1 has two resistances in series; branch 2 has only one resistance.



## **Resistance Strings in Parallel**

*V* is the same across each parallel branch.





## **Resistance Banks in Series**

- In this figure,  $R_2$  and  $R_3$  are parallel resistances in a bank. The parallel bank is in series with  $R_1$ .
- There may be more than two parallel resistances in a bank, and any number of banks in series.
- Ohm's Law is applied to the series and parallel components as seen previously.



Parallel bank of  $R_2$  and  $R_3$  in series with  $R_1$ 



### Resistance Banks in Series

• To find the total resistance of this type of circuit, combine the parallel resistances in each bank and add the series resistances.

$$R = \frac{V}{I}$$

$$6\Omega = \frac{10\Omega(\text{of } R_2 + R_3)}{2 \text{ branches}} + 1\Omega(R_1)$$

$$R = \frac{24V}{4A}$$

$$6\Omega = \frac{24V}{4A}$$

$$6\Omega = 5\Omega + 1\Omega$$



#### Resistance Banks and Strings in Series-Parallel 2

#### Example:

- Find all currents and voltages in Figure
  - Step 1: Find  $R_{T}$ .



Reducing a series-parallel circuit to an equivalent series circuit to find the  $R_{T}$ .

- (a) Actual circuit.
- (b) (b)  $R_3$  and  $R_4$  in parallel combined for the equivalent  $R_7$ .

Dr. V. E. Levent Electronic Circuits – COMP301

 $I_T = \frac{V_T}{R_T}.$ 



#### **Resistance Banks and Strings in Series-Parallel**



(c)  $R_7$  and  $R_6$  in series added for  $R_{13}$ . (d)  $R_{13}$  and  $R_5$  in parallel combined for  $R_{18}$ .



#### Resistance Banks and Strings in Series-Parallel 4



The  $R_{18}$ ,  $R_1$ , and  $R_2$  in series are added for the total resistance of 50  $\Omega$  for  $R_T$ .



In solving such circuits, apply the same principles as before:

- Reduce the circuit to its simplest possible form.
- Apply Ohm's Law.



#### Example:

• In Figure, we can find branch currents  $I_1$  and  $I_{2-3}$ , and  $I_7$ , and voltage drops  $V_1$ ,  $V_2$ , and  $V_3$ , without knowing the value of  $R_7$ .



Finding all the currents and voltages by calculating the branch currents first.



• Find  $I_1$ ,  $I_{2-3}$ , and  $I_T$ .





(parallel branches have the same voltage)

 $I_1 = 3A$ 



$$I_{2-3} = \frac{V}{R_{2-3}} \qquad I_T = I_1 + I_{2-3}$$
$$I_{2-3} = \frac{90V}{20\Omega + 25\Omega} \qquad I_T = 3A + 2A$$
$$I_{2-3} = \frac{90V}{45\Omega} \qquad I_T = 5A$$

 $I_{2-3} = 2A$ 



• Find voltage drops  $V_1$ ,  $V_2$ , and  $V_3$ :





	$V_1 = V_A$				
	$V_1 = 90$ V				
or					
	$V_1 = I_1 R_1$		$V_2 = I_{2-3}R_2$		$V_{3} =$
	$V_1 = 3A \times 3$	30Ω	$V_2 = 2A(20\Omega)$		$V_{3} =$
	$V_1 = 90V$		$V_2 = 40$ V		$V_{3} =$
Note	2:	$V_2 + V_3 = V$	r A		
40V + 50V = 90V					

Dr. V. E. Levent Electronic Circuits – COMP301

 $I_{2-3}R_3$ 

50V

 $2A(25\Omega)$ 



## wns

$$R_T = \frac{V_A}{I_T}$$
$$R_T = \frac{90V}{5A}$$

$$R_T = 18\Omega$$



- In series-parallel circuits, an open or short in one part of the circuit changes the values in the entire circuit.
- When troubleshooting series-parallel circuits, combine the techniques used when troubleshooting individual series and parallel circuits.



Effect of a Short in a Series-Parallel Circuit.

• The total current and total power increase.



Effect of a short circuit with series-parallel connections.

(a) Normal circuit with  $S_1$  open.

(b) Circuit with short between points A and B when  $S_1$  is closed; now  $R_2$  and  $R_3$  are short-circuited.



• Effect of a Short in a Series-Parallel Circuit.



The total current increases from 2A with  $S_1$  open to 10A with  $S_1$  closed.

With  $S_1$  closed,  $R_2$  and  $R_3$  are shorted out.



• Effect of an Open in a Series-Parallel Circuit.



Effect of an open path in a series-parallel circuit.

(a) Normal circuit with  $S_2$  closed.

(b) Series circuit with  $R_1$  and  $R_2$  when  $S_2$  is open. Now  $R_3$  in the open path has no current and zero *IR* voltage drop.

With  $S_2$  open,  $R_3$  is effectively removed from the circuit.



• Effect of an Open in a Series-Parallel Circuit.



With  $S_2$  open the voltage across points **C** and **D** equals the voltage across  $R_2$ , which is 89V. The voltage across  $R_3$  is zero.