

Embedded Systems

Week 8: State Machines



Dr. Vecdi Emre Levent

Instructors

Assist. Prof. Dr. Vecdi Emre Levent

Email : emre@levent.tc

emre.levent@marmara.edu.tr

Web: www.levent.tc



Course

- Finite State Machines

Determining the Behavior of the Sequential Circuit FSM



- Finite-State Machine (FSM)
 - It is a representation of the behavior of the sequential circuit according to the states.
 - Lists states and transitions between states
 - Example : Let there be an output signal named X and each clock change value in cycle
 - Two states : “Off” ($x=0$), and “On” ($x=1$)
 - There are transitions from the Off state to the On state and from the On state to the Off state.
 - The initial state is indicated by an arrow.

Output : x

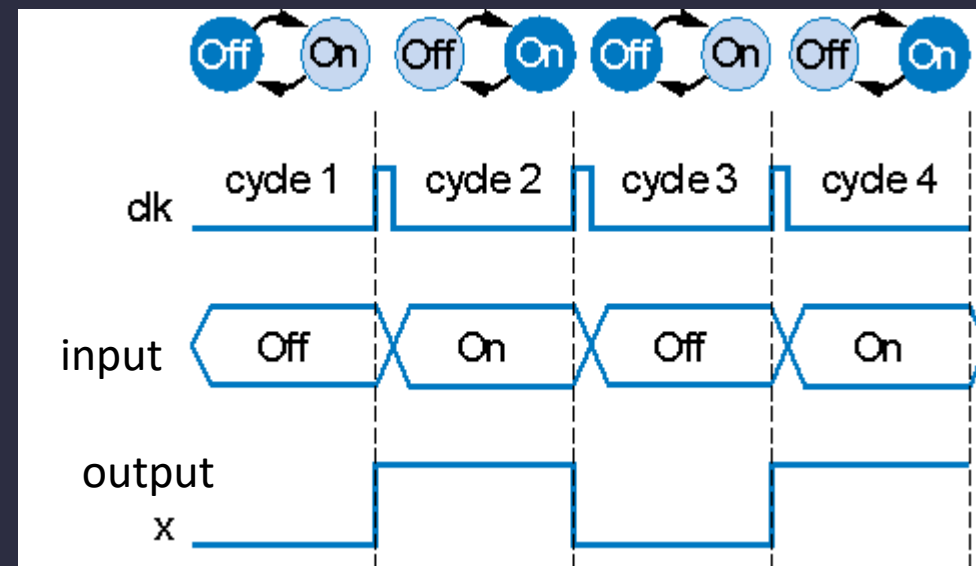 

FSM Example : 0,1,1,1, repetition

 
 
- In order 0, 1, 1, 1, 0, 1, 1, 1, ... A circuit that gives its outputs will be designed.
 - Each value is a clock It appears in the cycle .
- Can be designed with FSM
 - There are 4 states



FSM Example


take a one-bit input named b ,
Output pattern 101 and waits for
input b again.

Inputs : b ; Outputs : x

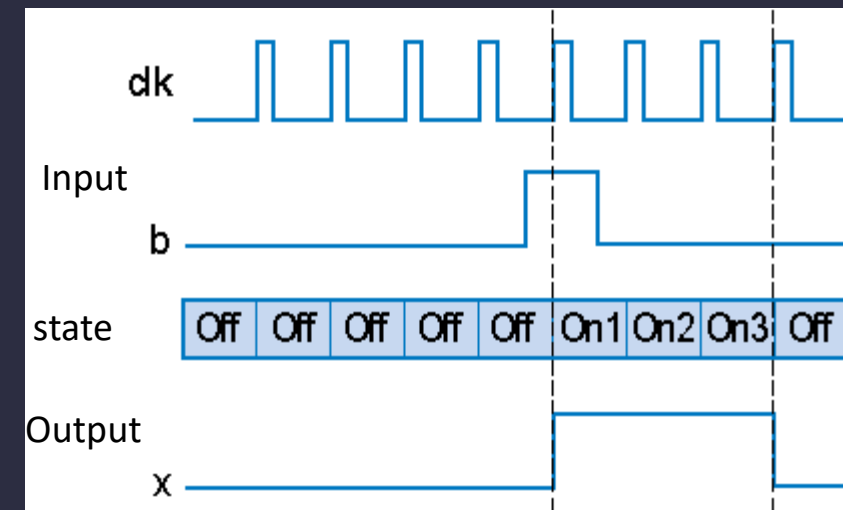 




FSM Example: Car Key

 - Car keys contain a chip that holds the key's identity.
 - When the key is inserted in the car, it asks the key for identification.
 - Sends key credential, if not correct the tool won't start
- FSM
 - Wait for request ($a=1$)
 - Send ID (For example , 1101)






FSM Example: Car Key

- FSM Timings

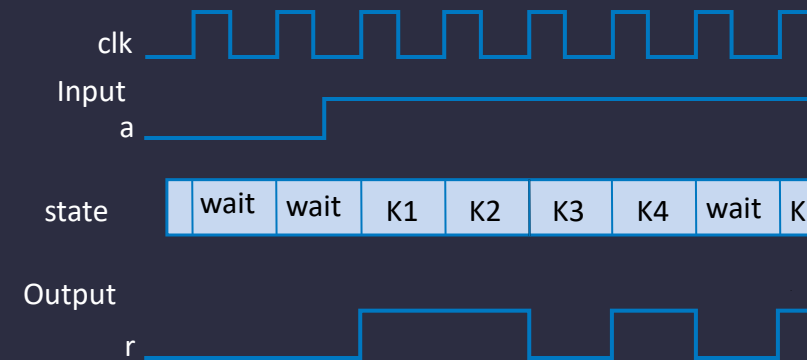  



FSM Architecture

   - How is FSM implemented as a sequential circuit ?
 - Status register - to keep the current state
 - Combinational circuit – to calculate output and next state



FSM Design Example

 
 
- Step 1: Analyze the requirements
- Step 2: Extract architecture
 - 2-bit state register (for 4 states)
 - Input b, output x
 - Next status signals n1, n0
- Step 3: Encode the states



FSM Design Example

- Step 4: Create a Truth Table


	Entries			Outputs		
	s1	s0	b	x	n1	n0
<i>Off</i>	0	0	0	0	0	0
	0	0	1	0	0	1
<i>On1</i>	0	1	0	1	1	0
	0	1	1	1	1	0
<i>On2</i>	1	0	0	1	1	1
	1	0	1	1	1	1
<i>On3</i>	1	1	0	1	0	0
	1	1	1	1	0	0

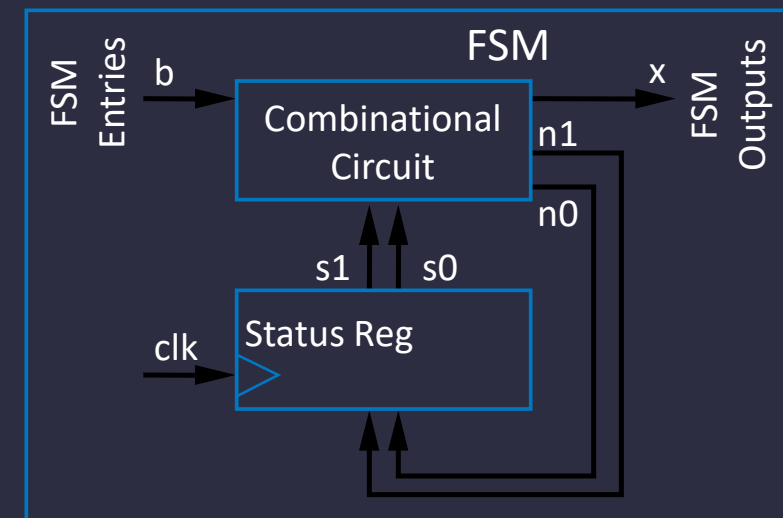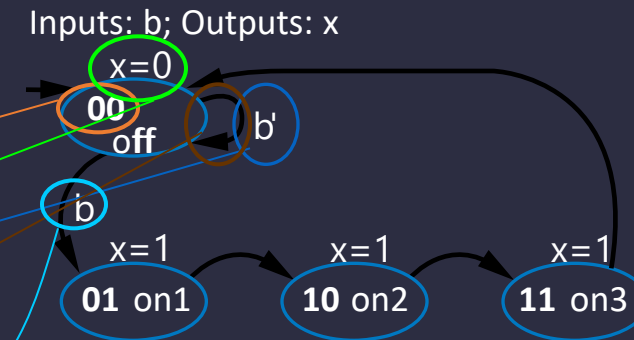

FSM Design Example

- Step 5: Combinational Circuit Implementation

	Entries			Outputs		
	s1	s0	b	x	n1	n0
<i>Off</i>	0	0	0	0	0	0
	0	0	1	0	0	1
<i>On1</i>	0	1	0	1	1	0
	0	1	1	1	1	0
<i>On2</i>	1	0	0	1	1	1
	1	0	1	1	1	1
<i>On3</i>	1	1	0	1	0	0
	1	1	1	1	0	0

 

$$x = s1 \mid s0$$

$$n1 = s1's0b' \mid s1's0b \mid s1s0'b' \mid s1s0'b$$

$$n1 = s1's0 \mid s1s0'$$

$$n0 = s1's0'b \mid s1s0'b' \mid s1s0'b$$

$$n0 = s1's0'b \mid s1s0'$$

FSM Design Example



- Step 5: Build the combinational circuit

	Entries			Outputs		
	s1	s0	b	x	n1	n0
<i>Off</i>	0	0	0	0	0	0
	0	0	1	0	0	1
<i>On1</i>	0	1	0	1	1	0
	0	1	1	1	1	0
<i>On2</i>	1	0	0	1	1	1
	1	0	1	1	1	1
<i>On3</i>	1	1	0	1	0	0
	1	1	1	1	0	0



$$x = s1 \mid s0$$

$$n1 = s1's0 \mid s1s0'$$

$$n0 = s1's0'b \mid s1s0'$$

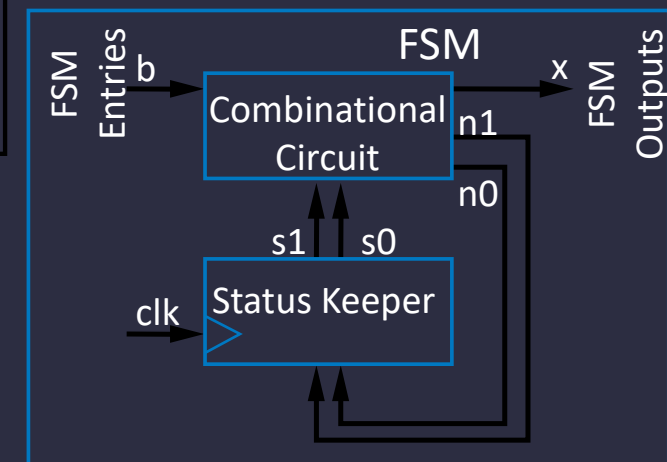 


Button Filter Module Example

  


- cycle when the button is pressed A design that produces a pulse is desired.


Button Filter Module Example

 

Step 1: FSM

 


Step 2: Build architecture

 

Step 3: State coding

Entries			Outputs		
s1	s0	bi	n1	n0	bo
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	0	0

Step 4: Status Chart

 

Step 5: Build Circuit




$$n1 = s1's0bi \mid s1s0bi$$

$$n0 = s1's0'bi$$


$$bo = s1's0bi' \mid s1's0bi = s1s0$$

FSM Design Errors

   - In conditions in transitions between states, only one transition condition must be true at a time*



 
$ab=00?$
What will be the next situation?



Course

- State Machines
 - State Machines Verilog Representations

Durum Makinaları

 

State Machines

Moore State Machine Examples

State Machines

```
module stateMachineTest (input clk, input in, output reg out)
```

```
  reg [1:0] state, stateNext;  
  reg outNext;
```


```
  initial begin  
    state = 0;  
    stateNext = 0;  
    out = 0;  
    outNext = 0;
```

```
  end
```

```
  always@(posedge clk) begin  
    state <= stateNext;  
    out <= outNext;
```

```
  end
```

Moore

 


State Machines

```

always@(*) begin
    stateNext = state;
    outNext = out;
    case(state)
        0: begin
            if(in == 0)begin
                stateNext = 1;
                outNext = 0;
            end
        end
    endcase
end
endmodule

```

Moore

 


State Machines

```

1: begin
    if(in == 1)begin
        stateNext = 2;
        outNext = 0;
    end
end
2: begin
    if(in == 1)begin
        stateNext = 3;
        outNext = 1;
    end else begin
        stateNext = 1;
        outNext = 0;
    end
end
3: begin
    if(in == 0)begin
        stateNext = 1;
        outNext = 0;
    end else begin
        stateNext = 0;
        outNext = 0;
    end
end
end
    
```

Moore

 

State Machines

```
module mooreMachine2 (input clk, input ResetN, input w, output reg z)
```

```
reg [1:0] state, stateNext;
```

```
reg zNext;
```

```
initial begin
```

```
    state = 0;
```

```
    stateNext = 0;
```

```
    z = 0;
```

```
    zNext = 0;
```


```
end
```

```
always@(posedge clk) begin
```

```
    state <= stateNext;
```

```
    z <= zNext;
```

```
end
```

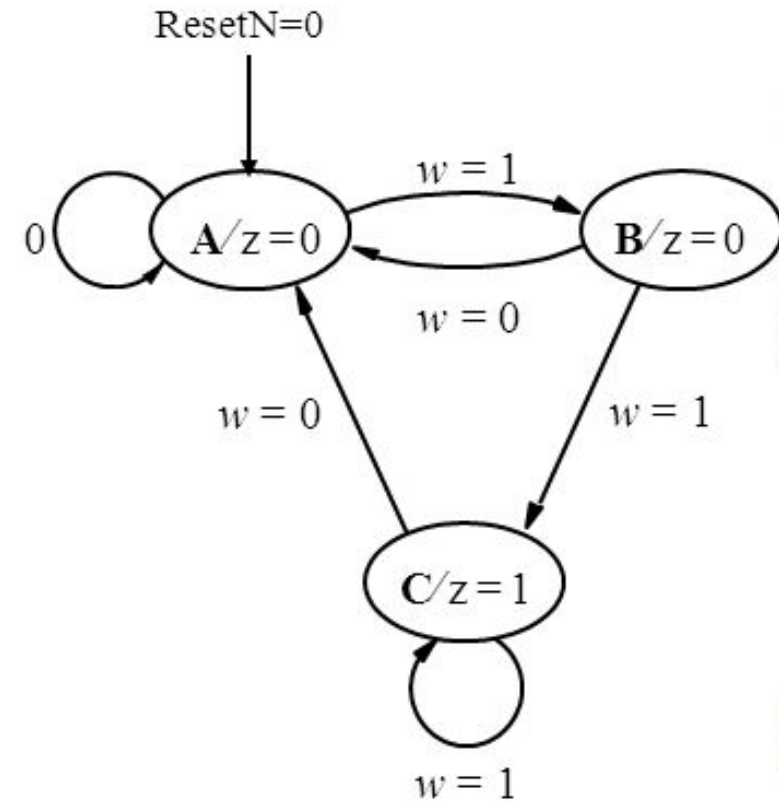


State Machines

```

always@(*) begin
    stateNext = state;
    zNext = z;
    if(ResetN) begin
        stateNext = 0;
        zNext = 0;
    end else begin
        case(state)
            0: begin
                if(w == 1)begin
                    stateNext = 1;
                    zNext = 0;
                end
            end
        endcase
    end
end
endmodule


```

 

State Machines

```

 1: begin
    if(w == 0)begin
        stateNext = 0;
        zNext = 0;
    end else begin
        stateNext = 2;
        zNext = 1;
    end
end
2: begin
    if(w == 0)begin
        stateNext = 0;
        zNext = 0;
    end
end
end
    
```



State Machines

Mealy State Machine Examples

State Machines

```
module mooreMachine1 (input clk, input in, output reg out)
```

```
reg [1:0] state, stateNext;
```

```
initial begin
```

```
    state = 0;
```

```
    stateNext = 0;
```


```
    out = 0;
```

```
end
```

```
always@(posedge clk) begin
```

```
    state <= stateNext;
```

```
end
```

 


State Machines

```

always@(*) begin
    stateNext = state;
    out = 0;
    case(state)
        0: begin
            if(in == 0)begin
                out = 0;
            end else begin
                out = 1;
                stateNext = 1;
            end
        end
    endcase
end


```

 

State Machines

```

 1: begin
    if(in == 0)begin
        out = 0;
        stateNext = 2;
    end else begin
        out = 0;
    end
end
2: begin
    if(in == 0)begin
        out = 0;
        stateNext = 3;
    end else begin
        out = 0;
        stateNext = 0;
    end
end
3: begin
    if(in == 0)begin
        out = 1;
        stateNext = 0;
    end else begin
        out = 0;
        stateNext = 1;
    end
end
end
    
```



State Machines

```
module mooreMachine2 (input clk, input in, output reg out)
```

```
  reg [1:0] state, stateNext;
```

```
  initial begin
```

```
    state = 0;
```

```
    stateNext = 0;
```


```
    out = 0;
```

```
  end
```

```
  always@(posedge clk) begin
```

```
    state <= stateNext;
```

```
  end
```

 


State Machines

```

always@(*) begin
    stateNext = state;
    out = 0;
    if(rst) begin
        stateNext = 0;
        out = 0;
    end else begin
        case(state)
            0: begin
                if(in == 0)begin
                    out = 0;
                end else if(in == 1) begin
                    out = 0;
                    stateNext = 1;
                end else if(in == 2) begin
                    out = 0;
                    stateNext = 2;
                end
            end
        endcase
    end
end
endmodule

```

 

State Machines

1: begin

```

if(in == 0)begin
    out = 0;
end else if(in == 1) begin
    out = 0;
    stateNext = 2;
end else if(in == 2) begin
    out = 2;
    stateNext = 2;
end

```

end

2: begin

```

if(in == 0)begin
    out = 0;
end else if(in == 1) begin
    out = 2;
    stateNext = 0;
end else if(in == 2) begin
    out = 3;
    stateNext = 0;
end

```

end

